
 



**PROGRAMMABLE  
LOGIC  
DEVICES**

 

(a) Programmable read-only memory (PROM)



(b) Programmable array logic (PAL)

 

(c) Programmable logic array (PLA)

Fig. 7-13 Basic Configuration of Three PLDs


 


Fig. 7-9 ROM Block Diagram

 
## Programmable logic devices


- Building circuits with decoders is so easy that **programmable logic devices** are often based around decoders.
- The diagram below shows a blank **read-only memory**, or **ROM**, device.
  - It's just a decoder whose outputs may be sent to several OR gates.
  - The connections between the decoder outputs and the OR gate inputs are "programmable," so different functions can be implemented.
- To program a ROM for some specific functions, you just have to make the right connections.



 
## ROM example

- Here are three functions V2, V1 and V0, implemented with our ROM.
- Blue crosses (X) indicate connections between decoder outputs and OR gates. Empty intersections are not connected.
- This is an **8 × 3 ROM** since there are 8 decoder outputs and 3 OR gates.



 

(a) Conventional symbol

 


(b) Array logic symbol

Fig. 7-1 Conventional and Array Logic Diagrams for OR Gate

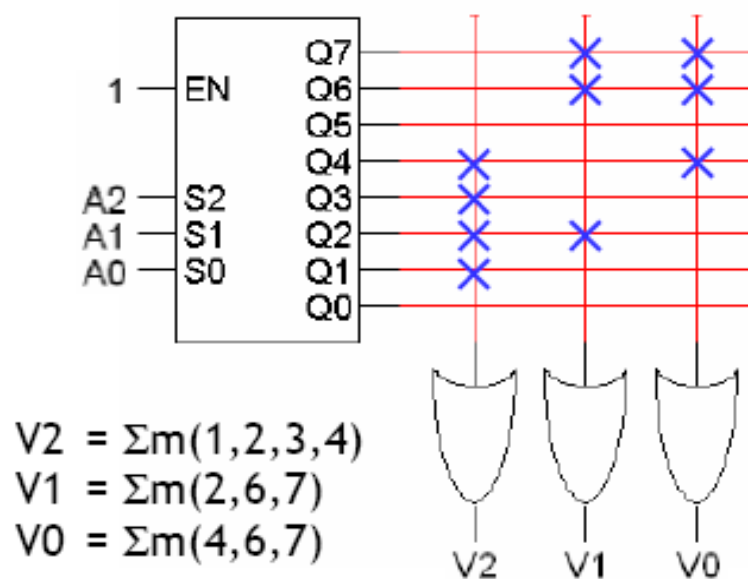
## The same example again

- Here is an alternative presentation of the same  $8 \times 3$  ROM, but with some simplified OR gates just to make the diagram neater.


 
## Why is this called a memory?

- You can think of this circuit as performing a computation on the inputs A2A1A0, to produce the outputs V2V1V0.
- Note that if the same inputs are chosen again, this circuit would perform the same calculation again, and produce the same output.
- In a sense, the circuit “remembers” the output for each possible input.




A2	A1	A0	V2	V1	V0
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	0	1	1



 
## Viewing circuits as memories

- So you can also think of this circuit as a memory.
  - It stores eight values of data, each consisting of three bits V2V1V0.
  - A2A1A0 form an **address** that refers to one of the eight stored values.
- This memory is **read-only** since you can't modify the data without going through the time-consuming process of re-programming the ROM.



Address			Data		
A2	A1	A0	V2	V1	V0
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	0	1	1
1	1	1	0	1	1

 

(a) Block diagram

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 7-12 ROM Implementation of Example 7-1


## Programmable logic arrays

---

- A ROM is potentially inefficient since it uses a decoder, which generates *all* possible minterms. No circuit minimization is done.
- Using a ROM to implement an  $n$ -input function requires many gates.
  - An  $n$ -to- $2^n$  decoder has  $n$  inverters and  $2^n$   $n$ -input AND gates.
  - We also need an OR gate with up to  $2^n$  inputs.
  - The number of gates roughly doubles for each additional ROM input.
- A **programmable logic array** or **PLA** makes the decoder part of the ROM programmable too. Instead of generating all possible minterms, you can choose which products (not necessarily minterms) to generate.
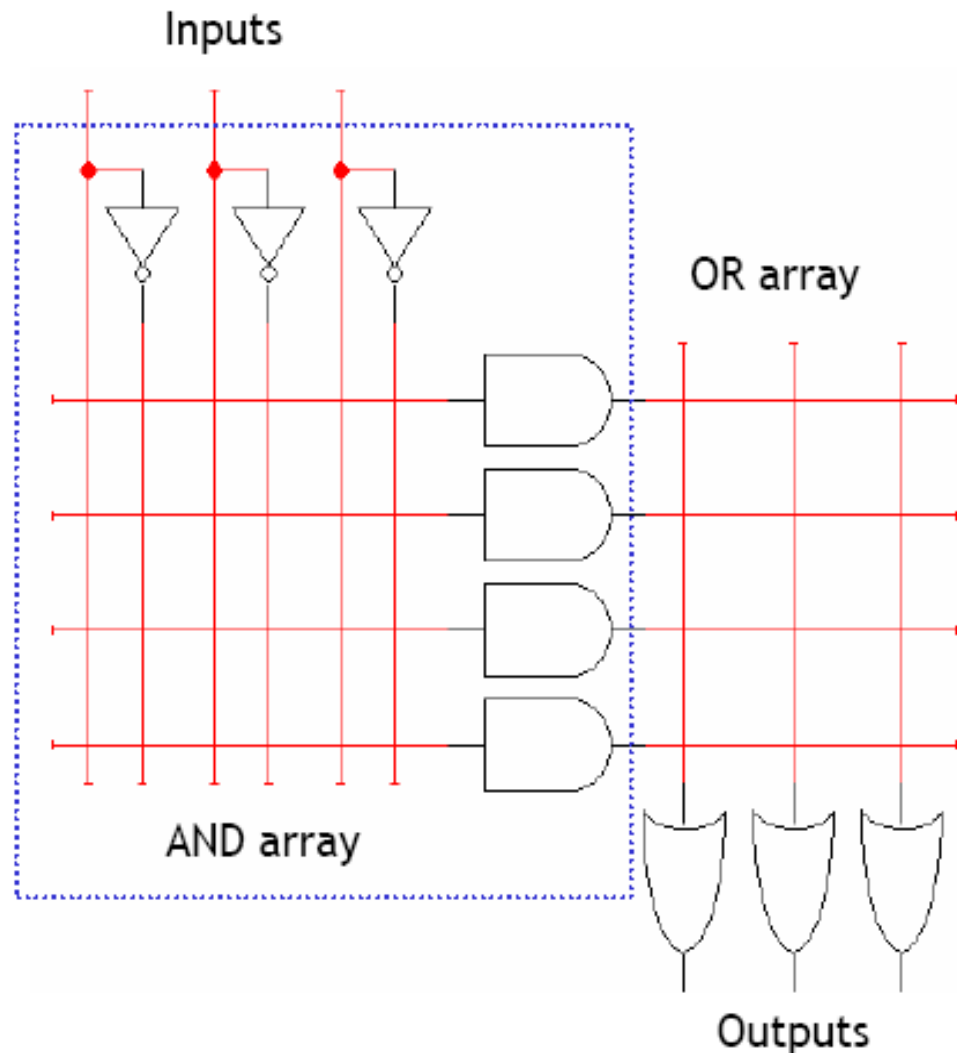
## A blank $3 \times 4 \times 3$ PLA

- This is a  $3 \times 4 \times 3$  PLA (3 inputs, up to 4 product terms, and 3 outputs), ready to be programmed.
- The left part of this diagram replaces the decoder used in a ROM.
- Connections are made within the **AND array** to produce four arbitrary products.
- Those products are then summed in the **OR array**.



## Regular K-map minimization

- The normal K-map approach is to minimize the number of product terms for each *individual* function.
- For our three sample functions, this would result in a total of six different product terms.

$$V2 = \Sigma m(1,2,3,4)$$

$$V1 = \Sigma m(2,6,7)$$

$$V0 = \Sigma m(4,6,7)$$

		Y			
		0	1	1	1
X	1	0	0	0	0
		Z			

$$V2 = xy'z' + x'z + x'y$$

				Y
	0	0	0	1
X	0	0	1	1
			Z	

$$V1 = yz' + xy$$

		Y			
		0	0	0	0
X	1	0	1	1	
		Z			

$$V0 = xz' + xy$$

## PLA minimization

- But for a PLA, what we really want is to minimize the number of product terms in *all* of the functions.
- We could express V2, V1 and V0 with just *four* total products instead.

$$V2 = \Sigma m(1,2,3,4)$$

$$V1 = \Sigma m(2,6,7)$$

$$V0 = \Sigma m(4,6,7)$$

		Y		
		0	1	1
X		1	0	0
	Z			

$$V2 = xy'z' + x'z + x'yz'$$

		Y		
		0	0	1
X		0	0	1
	Z			


$$V1 = x'yz' + xy$$

		Y		
		0	0	0
X		1	0	1
	Z			

$$V0 = xy'z' + xy$$
 
## PLA example

- So we can implement these three functions using a  $3 \times 4 \times 3$  PLA.



## PLA Example

Implement the two functions:

$$F1 = \Sigma(0,1,2,4)$$

$$F2 = \Sigma(0,5,6,7)$$

Using a PLA of size 3x4x2



		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
<i>A</i>	1	1	0	0	0
		<i>C</i>			

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
<i>A</i>	1	0	1	1	1
		<i>C</i>			

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

PLA programming table						
	Product term	Inputs				
		<i>A B C</i>			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	(C) <i>F</i> <sub>1</sub>	(T) <i>F</i> <sub>2</sub>
<i>AB</i>	1	1	1	–	1	1
<i>AC</i>	2	1	–	1	1	1
<i>BC</i>	3	–	1	1	1	–
<i>A'B'C'</i>	4	0	0	0	–	1

Fig. 7-15 Solution to Example 7-2

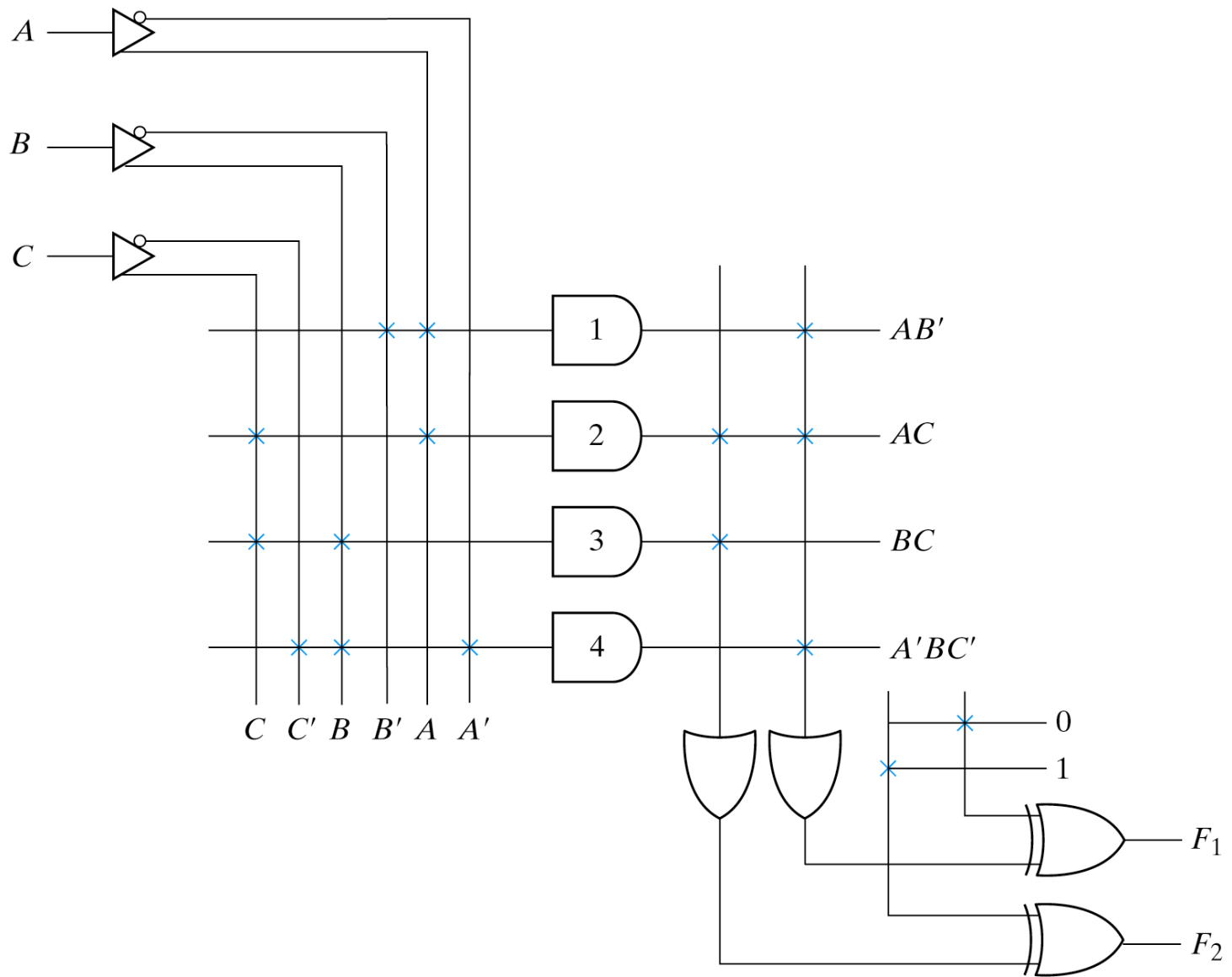


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

## PLA evaluation

---

- A  $k \times m \times n$  PLA can implement as many as  $n$  functions of  $k$  inputs, each of which must be expressible with no more than  $m$  product terms.
- Unlike ROMs, PLAs allow you to choose which products are generated.
  - This can significantly reduce the **fan-in** (number of inputs) of gates, as well as the total number of gates.
  - However, a PLA is less general than a ROM. Not every function may be expressible with the limited number of AND gates in a given PLA.
- You can think of PLAs as memories too.
  - A  $k \times m \times n$  PLA has  $k$  “address” lines, and each of those  $2^k$  addresses references an  $n$ -bit data value.
  - But again, not all possible data values can be stored.


**PROGRAMMABLE  
ARRAY  
LOGIC**

# Programmable Array Logic (PAL)

- OR plane (array) is fixed, AND plane can be programmed
- Less flexible than PLA
- # of product terms available per function (OR outputs) is limited


# PAL Example

Figure 4.15 A PAL

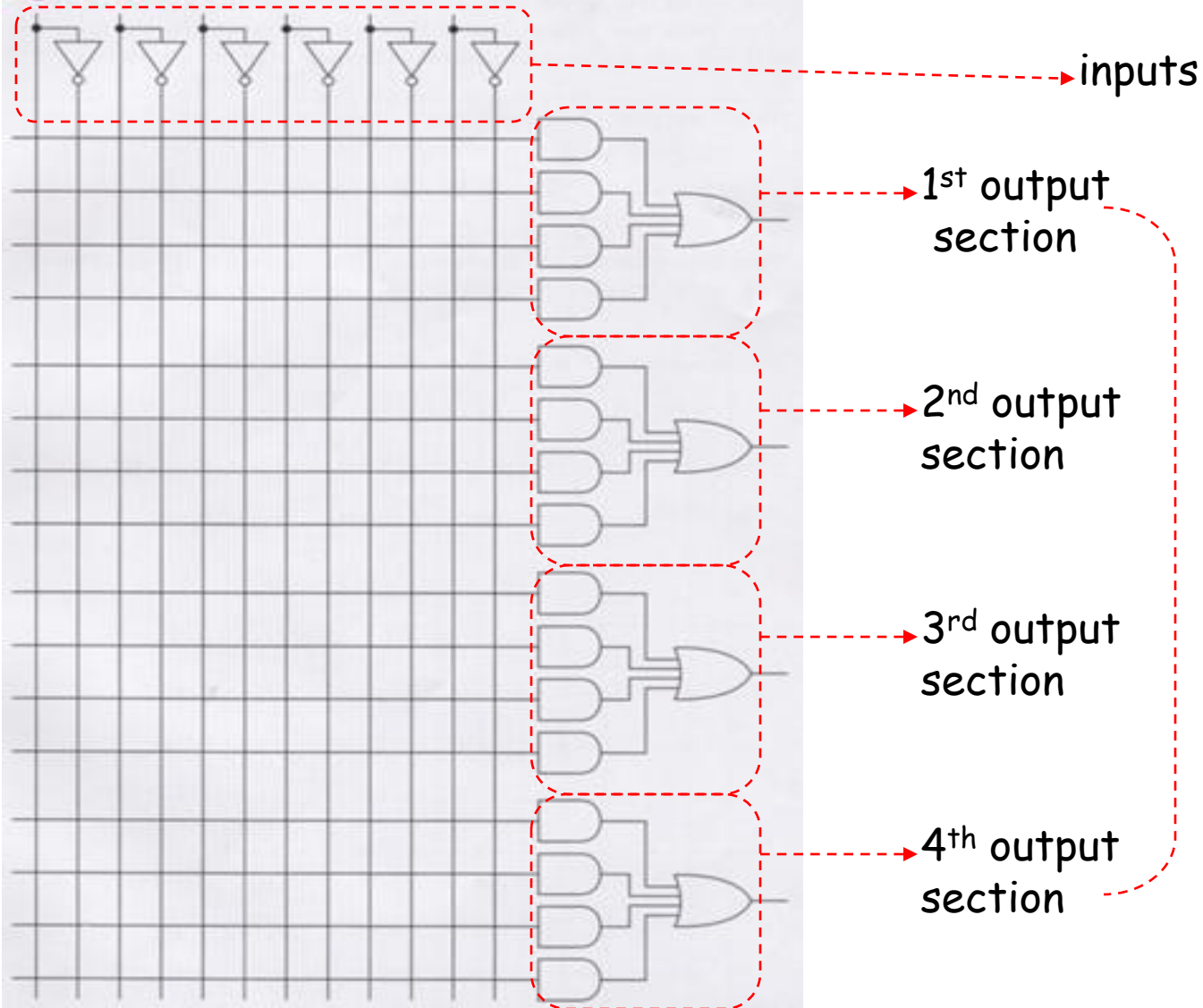

Only functions with  
at most four  
products can be  
implemented

# PAL-based circuit implementation

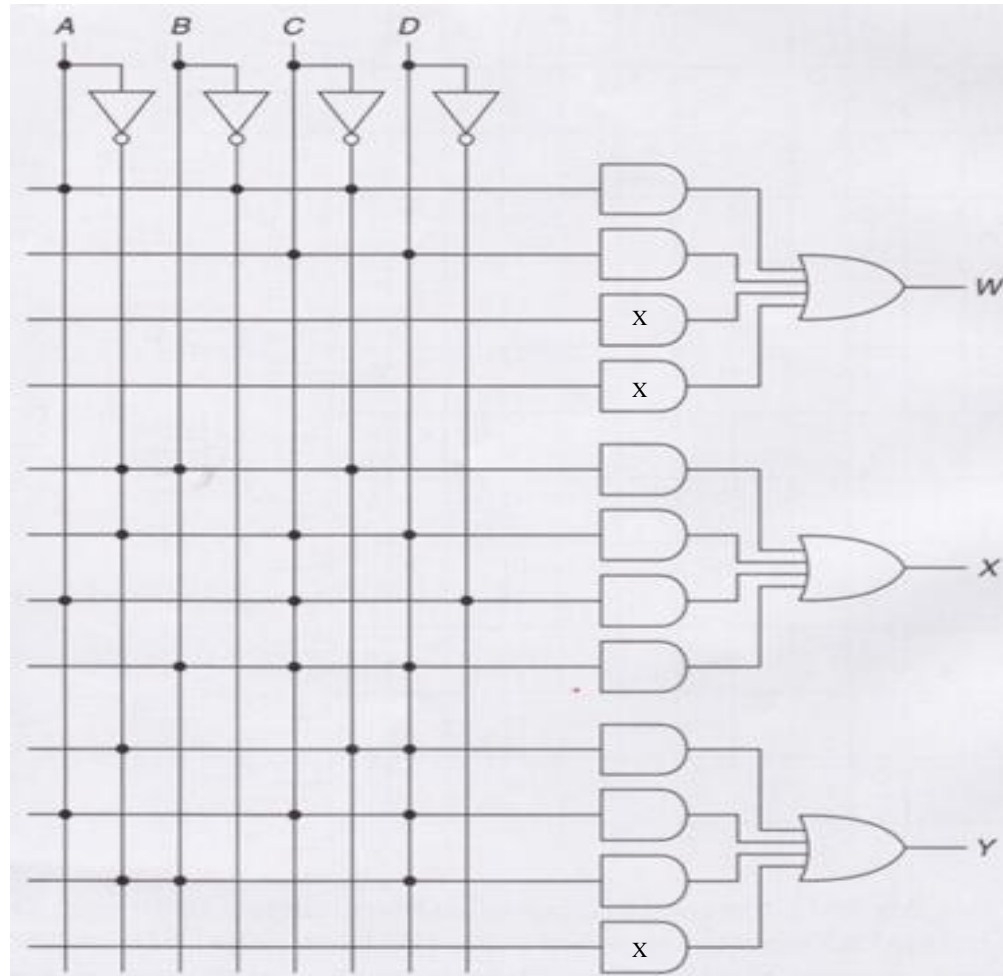


$$W = AB'C' + CD$$

$$X = A'BC' + A'CD + ACD' + BCD$$

$$Y = A'CD + ACD + A'BD$$
 
# Can we implement more complex functions using PALs?

- Yes, by allowing output lines to also serve as input lines in the AND plane.






# Example

- Implement the combinational circuit described by the following equations, using a PAL with 4 inputs, 4 outputs, and 3-wide AND-OR structure.
  - $W(A,B,C,D) = \sum m(2,12,13)$
  - $X(A,B,C,D) = \sum m(7,8,9,10,11,12,13,14,15)$
  - $Y(A,B,C,D) = \sum m(0,2,3,4,5,6,7,8,10,11,15)$
  - $Z(A,B,C,D) = \sum m(1,2,8,12,13)$

## Example (cont.)

- Use function simplification techniques to derive:
  - $W = ABC' + A'B'CD'$
  - $X = A + BCD$
  - $Y = A'B + CD + B'D'$
  - $Z = ABC' + A'B'CD' + AC'D' + A'B'C'D$   
 $= W + AC'D' + A'B'C'D$

# Example (cont.)

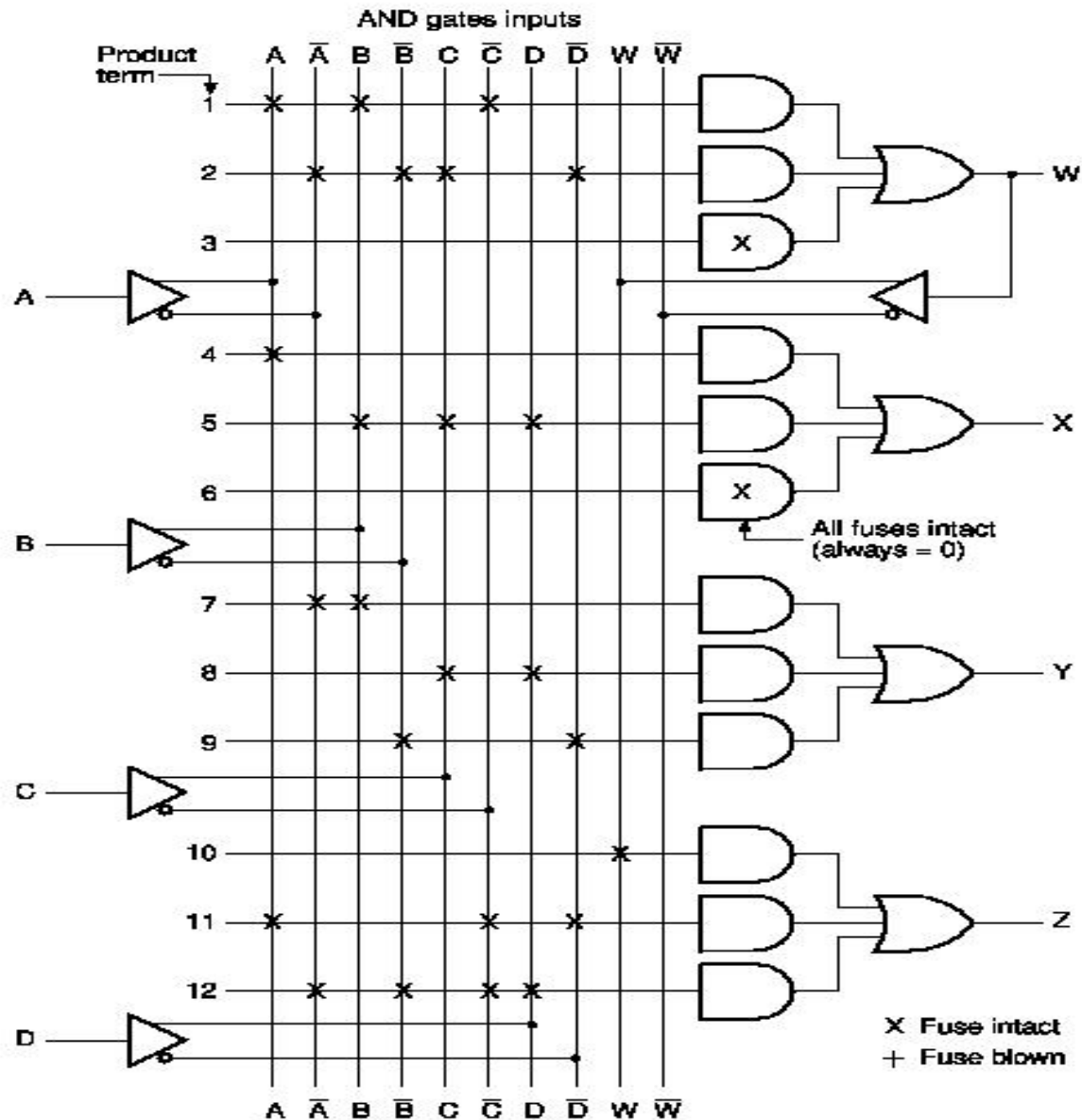

# Example (cont.)

Tabular Form Specification  
of interconnection programming

Product term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	—	—	$W = ABC\bar{C}$ $+ \bar{A}\bar{B}CD$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$X = A$ $+ BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$Y = \bar{A}B$ $+ CD$ $+ \bar{B}\bar{D}$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$Z = W$ $+ A\bar{C}\bar{D}$ $+ \bar{A}\bar{B}CD$
11	1	—	0	0	—	
12	0	0	0	1	—	

# Implement the functions given below Using a PLA

- $F1(a,b,c) = \sum(6,7)$
- $F2(a,b,c) = \sum(4,5,7)$
- $F3(a,b,c) = \sum(3,5)$
- $F4(a,b,c) = \sum(2,6)$