


Back to Combinational Logic Ckt design

COMPARATORS

MAGNITUDE COMPARATOR

- Given two n -bit magnitudes, A and B , a comparator indicates whether
 - $A = B$, $A > B$, or $A < B$

n -bit input magnitudes

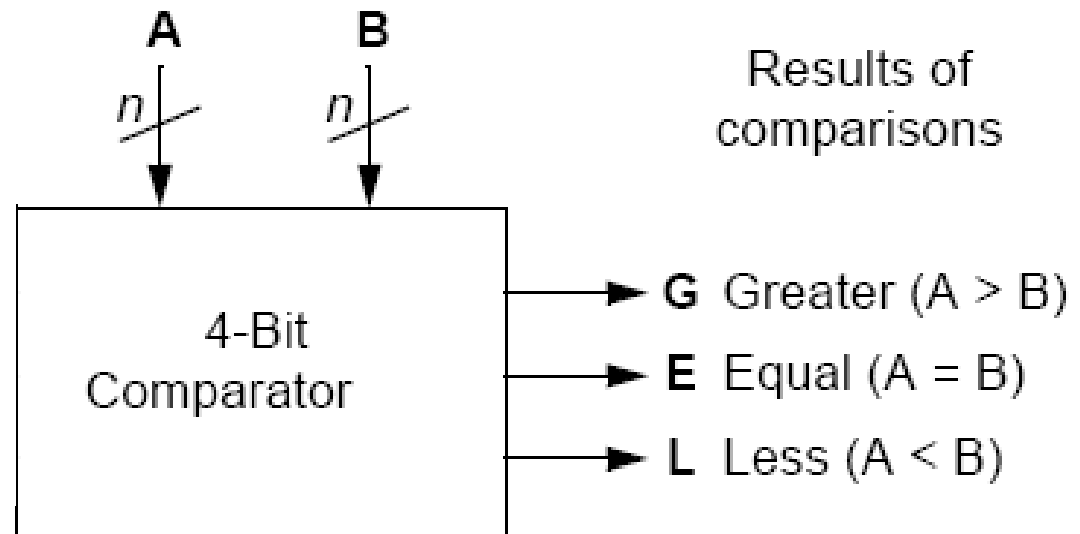

- The approach is to use the XNOR function (equivalence) on each of the n -bits as follows

$$x_i = \mathbf{A}_i \mathbf{B}_i + \overline{\mathbf{A}_i} \overline{\mathbf{B}_i} = \overline{\mathbf{A}_i \oplus \mathbf{B}_i}$$

- The Boolean functions for a 4-bit magnitude comparator is as follows
 - $(\mathbf{A} = \mathbf{B}) = x_3 x_2 x_1 x_0$
 - $(\mathbf{A} > \mathbf{B}) = \mathbf{A}_3 \overline{\mathbf{B}_3} + x_3 \mathbf{A}_2 \overline{\mathbf{B}_2} + x_3 x_2 \mathbf{A}_1 \overline{\mathbf{B}_1} + x_3 x_2 x_1 \mathbf{A}_0 \overline{\mathbf{B}_0}$
 - $(\mathbf{A} < \mathbf{B}) = \overline{\mathbf{A}_3} \mathbf{B}_3 + x_3 \overline{\mathbf{A}_2} \mathbf{B}_2 + x_3 x_2 \overline{\mathbf{A}_1} \mathbf{B}_1 + x_3 x_2 x_1 \overline{\mathbf{A}_0} \mathbf{B}_0$

Note: $\mathbf{A}_i \overline{\mathbf{B}_i}$ indicates whether $\mathbf{A}_i > \mathbf{B}_i$, $\overline{\mathbf{A}_i} \mathbf{B}_i$ indicates whether $\mathbf{A}_i < \mathbf{B}_i$, and x_i indicates whether $\mathbf{A}_i = \mathbf{B}_i$.


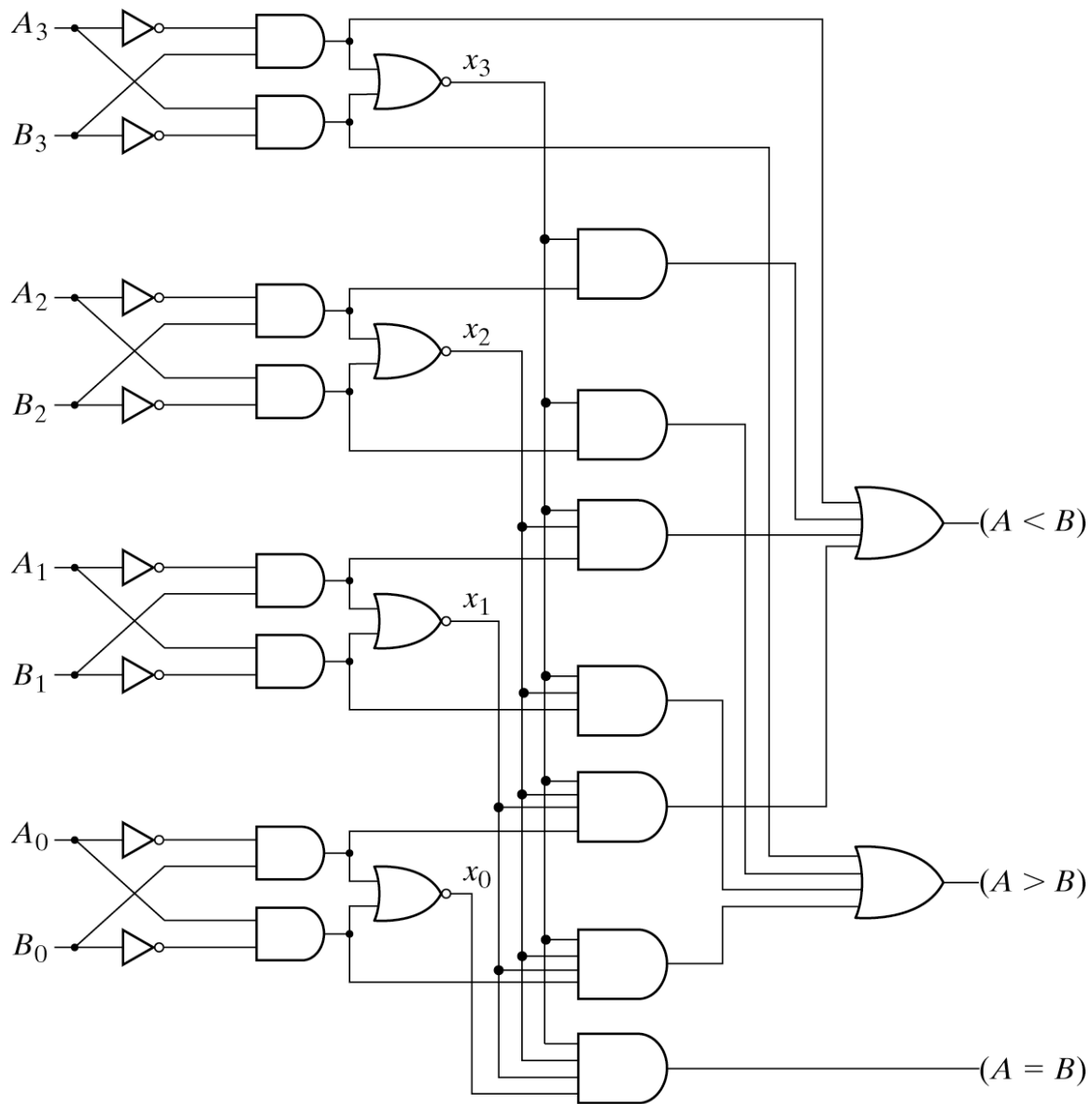


Fig. 4-17 4-Bit Magnitude Comparator

DECODERS

What a decoder does

 - A **n -to- 2^n decoder** uses its n -bit input to determine which of 2^n outputs will be uniquely activated.



S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- Here is a block diagram and truth table for a **2-to-4 decoder**.
 - The two-bit input is called **S1S0**, and the four outputs are **Q0-Q3**.
 - If the input is the binary number i , then output Q_i alone will be true.
- This circuit “decodes” a binary number into a “one-of-four” code.

Building a decoder

- We can use the truth table to derive minimal sum of products equations for each of the four outputs (Q0-Q3), based on the two inputs (S0-S1).

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- In this case there's not much to be simplified. Here are the equations:

$$Q0 = S1'S0'$$


$$Q1 = S1'S0$$

$$Q2 = S1S0'$$


$$Q3 = S1S0$$

Decoder circuit diagram

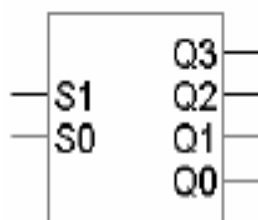- Here is an implementation of a 2-to-4 decoder.




S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

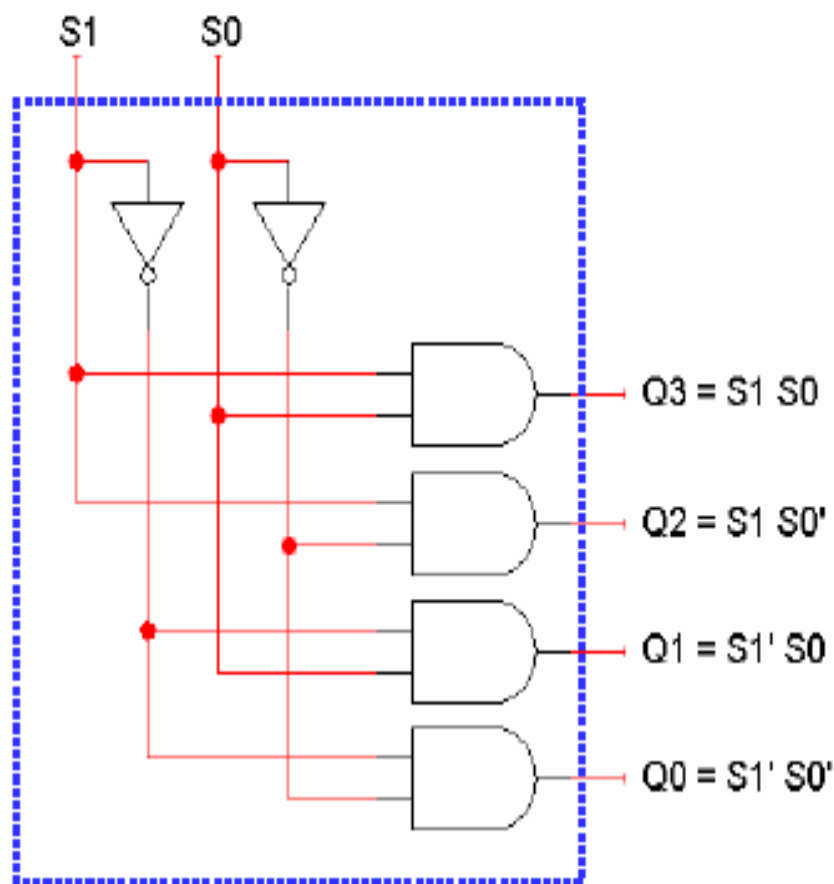

Enable inputs

decoders can include **enable inputs**.

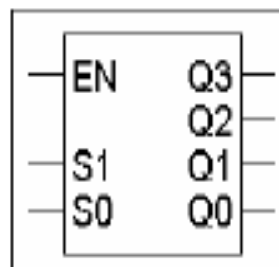
- **EN=0** disables the decoder, which by convention means that all of the decoder's outputs are 0.
- **EN=1** enables the decoder so that it behaves as specified earlier, with exactly one of the outputs being 1.



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

A 3-to-8 decoder

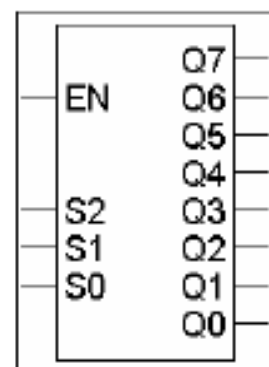- Larger decoders are similar. Here is a 3-to-8 decoder.
 - There are three selection inputs $S_2S_1S_0$, which activate one of eight outputs, Q_0 - Q_7 .
 - Again, only one output will be true for any input combination.
- A truth table and output equations for a 3-to-8 decoder (without EN) are given below.



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$Q_0 = S_2'S_1'S_0'$$

$$Q_1 = S_2'S_1'S_0$$

$$Q_2 = S_2'S_1S_0'$$

$$Q_3 = S_2'S_1S_0$$

$$Q_4 = S_2S_1'S_0'$$

$$Q_5 = S_2S_1'S_0$$

$$Q_6 = S_2S_1S_0'$$

$$Q_7 = S_2S_1S_0$$


Building a 3-to-8 decoder

- You could build a 3-to-8 decoder from the truth table and MSP equations below, just like we built the 2-to-4 decoder earlier.
- Another way to design a decoder is to break it into smaller pieces.
- Notice some patterns in the table below:
 - When $S_2 = 0$, outputs Q_0 - Q_3 are generated as in a 2-to-4 decoder.
 - When $S_2 = 1$, outputs Q_4 - Q_7 are generated as in a 2-to-4 decoder.

S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Decoder expansion

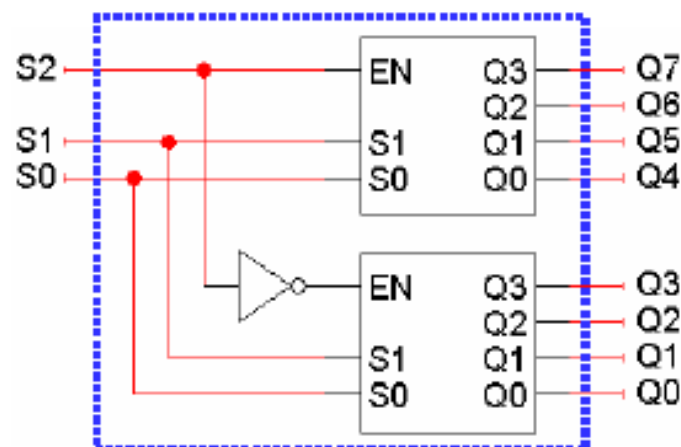
- Here's a 3-to-8 decoder built from two smaller 2-to-4 decoders.
- When $S2=0$, the bottom 2-to-4 decoder is enabled and generates a 1 for one of outputs $Q0$, $Q1$, $Q2$ or $Q3$.
- When $S2=1$, the top 2-to-4 decoder is enabled instead, and a 1 will be output for either $Q4$, $Q5$, $Q6$ or $Q7$.



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Modularity

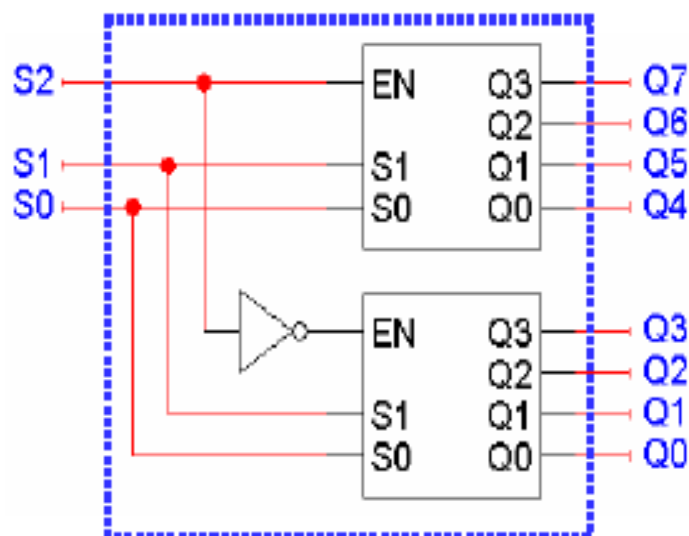- You could verify that this circuit is a 3-to-8 decoder, by using equations for the 2-to-4 decoders to derive equations for the 3-to-8.



So what good is a decoder?

- Do the truth table and equations look familiar?

S1	S0	Q0	Q1	Q2	Q3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$Q0 = S1'S0'$$

$$Q1 = S1'S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**.
 - For each input combination, exactly one output is true.
 - Each output equation contains all of the input variables.
- This means that you can easily use a decoder, or a minterm generator, to implement any sum of minterms expression.

Example: addition

- A truth table and sum of minterm equations for C and S are shown below.

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

- Today we'll implement these two functions using 3-to-8 decoders.


Implementing functions with decoders

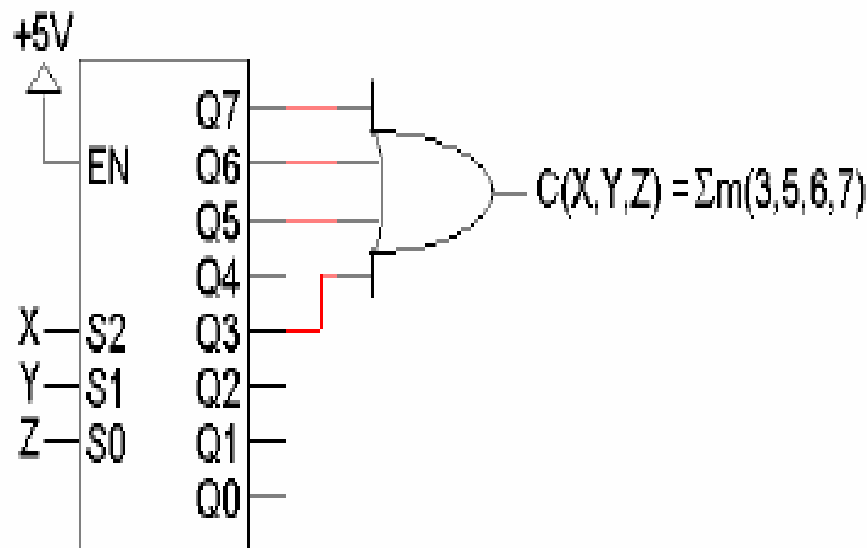- Here, a 3-to-8 decoder implements C as a sum of minterms.



- If XYZ is 011, 101, 110 or 111, then one of the decoder outputs Q3, Q5, Q6 or Q7 will be true, and the output $C(X,Y,Z)$ will also be true.

Verifying our adder

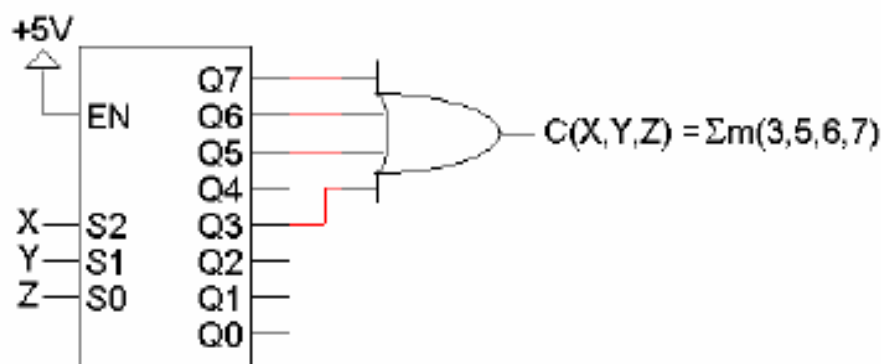

- C is the sum of decoder outputs Q3, Q5, Q6 and Q7.

$$C = Q3 + Q5 + Q6 + Q7$$


- We know how the decoder's outputs are generated from its inputs.

$$C = S2'S1S0 + S2S1'S0 + S2S1S0' + S2S1S0$$

- We can substitute XYZ for S2S1S0, resulting in a sum of minterms

$$C = X'YZ + XY'Z + XYZ' + XYZ$$

Decoder-based sum

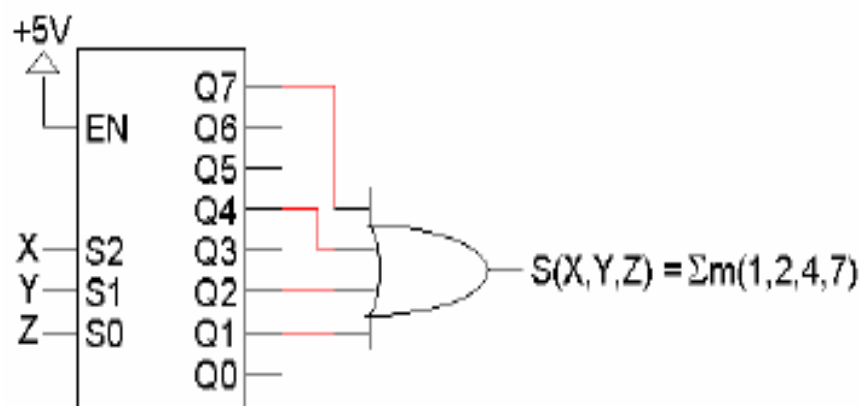


- If XYZ is 001, 010, 100 or 111, then one of decoder outputs Q1, Q2, Q4 or Q7 will be true, and $S(X,Y,Z)$ will be true as well.
- We can verify this circuit algebraically, just like before.

$$\begin{aligned} S(X,Y,Z) &= Q1 + Q2 + Q4 + Q7 \\ &= S2'S1'S0 + S2'S1S0' + S2S1'S0' + S2S1S0 \\ &= X'Y'Z + X'YZ' + XY'Z' + XYZ \\ &= m_1 + m_2 + m_4 + m_7 \end{aligned}$$

Using just one decoder

 
- Since the two functions C and S both have the same inputs, we could use just one decoder instead of two.



- Decoder output Q_0 is unused, while Q_7 is used multiple times. In general, you can always use circuit outputs as many or as few times as you need.


A variation of the standard decoder

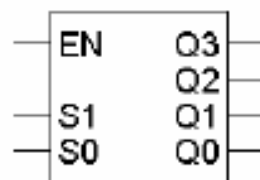- The decoders we've seen so far are **active-high** decoders.




EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

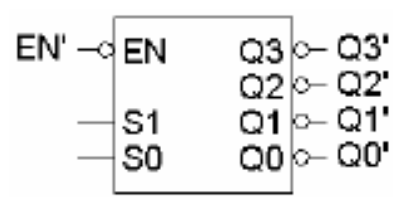- An **active-low decoder** is similar, but with an inverted EN input *and* inverted outputs—exactly one of the outputs will be *false*.




EN'	S1	S0	Q0'	Q1'	Q2'	Q3'
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

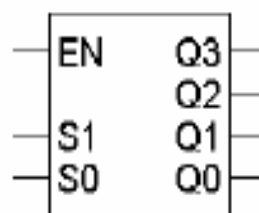- Active-high decoders generate minterms, as we've already seen.



$$\begin{aligned} Q3 &= S1 S0 \\ Q2 &= S1 S0' \\ Q1 &= S1' S0 \\ Q0 &= S1' S0' \end{aligned}$$

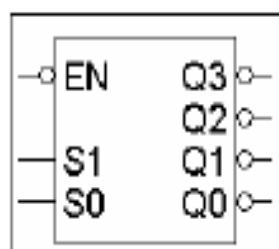- The output equations for an active-low decoder are mysteriously similar, yet somehow different.




$$\begin{aligned} Q3' &= (S1 S0)' = S1' + S0' \\ Q2' &= (S1 S0')' = S1' + S0 \\ Q1' &= (S1' S0)' = S1 + S0' \\ Q0' &= (S1' S0')' = S1 + S0 \end{aligned}$$

- It turns out that active-low decoders generate **maxterms**, so they can implement functions as sums of maxterms.

Active-low decoder example

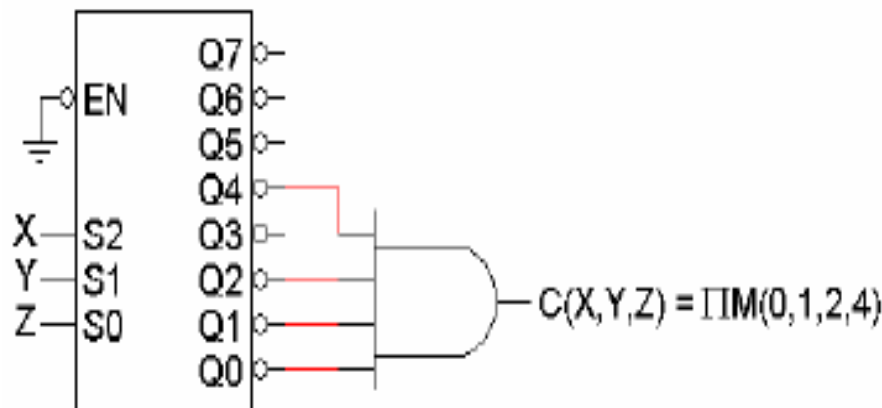- Here is the carry function C implemented with an active-low decoder.
 - Recall from our algebra lecture that $\Sigma m(3,5,6,7) = \Pi M(0,1,2,4)$.
 - We need an AND gate to generate a *product* of sums.




- The "ground" symbol connected to the EN input represents logical 0, so this decoder is always enabled.

Encoders

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has 2^n input lines and n output lines.
- The output lines generate the binary equivalent of the input line whose value is 1.

Encoders (cont.)

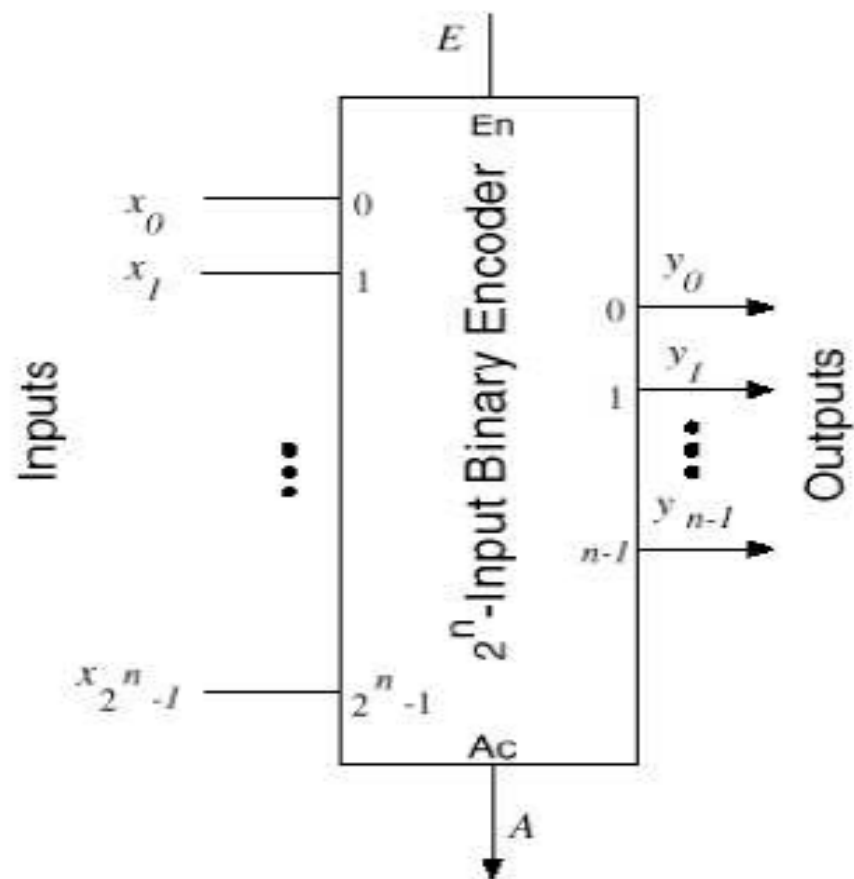

Encoder Example

- Example: 8-to-3 binary encoder (octal-to-binary)


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

Encoder Example (cont.)

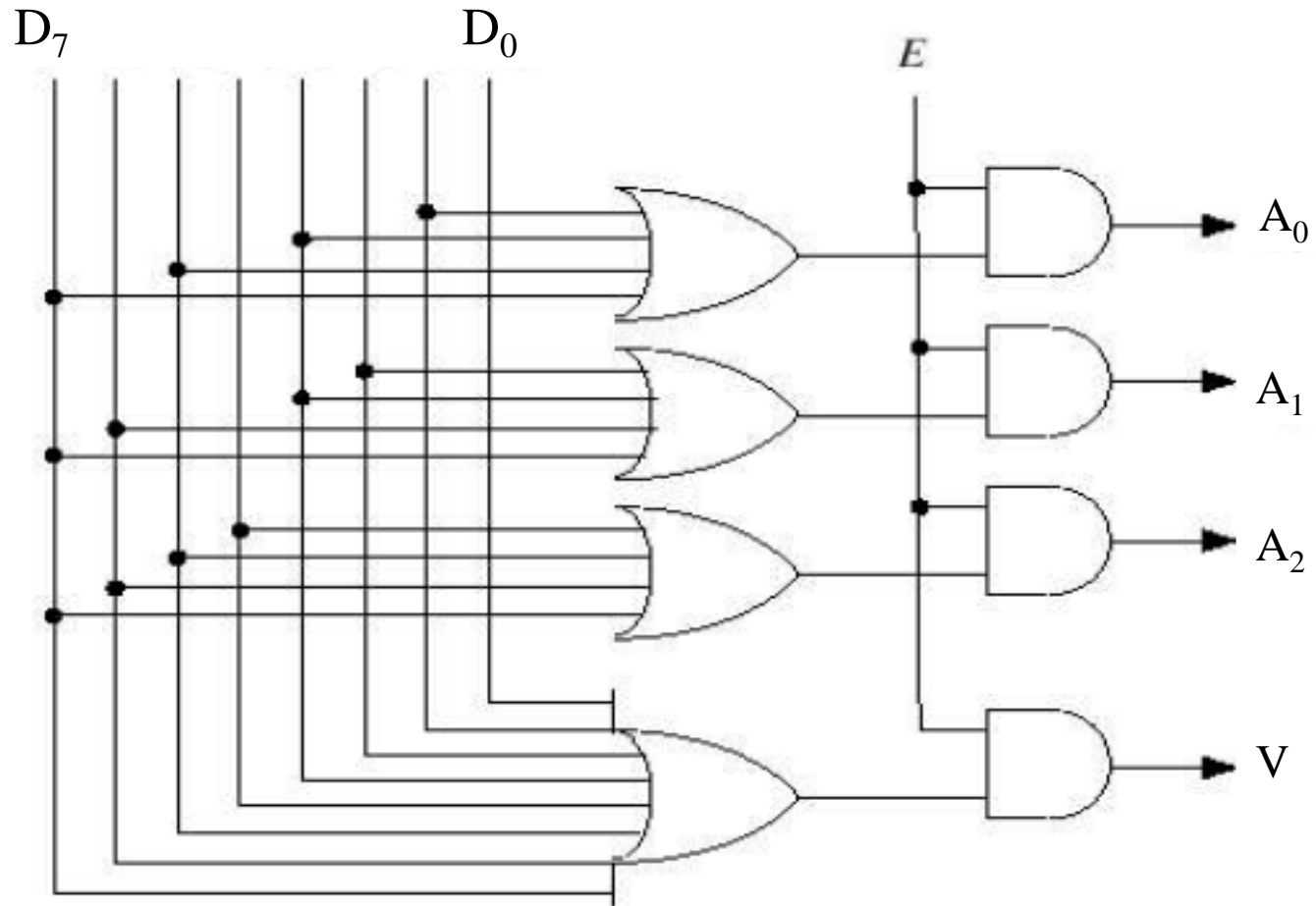

Encoder Design Issues

- There are two ambiguities associated with the design of a simple encoder:
 1. Only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination (for example, if D_3 and D_6 are 1 simultaneously, the output of the encoder will be 111).
 2. An output with all 0's can be generated when all the inputs are 0's, or when D_0 is equal to 1.

Priority Encoders

- Solves the ambiguities mentioned above.
- Multiple asserted inputs are allowed; one has priority over all others.
- Separate indication of no asserted inputs.



4-to-2 Priority Encoder (cont.)

- The operation of the priority encoder is such that:
- If two or more inputs are equal to 1 at the same time, the input in the highest-numbered position will take precedence.
- A *valid output indicator*, designated by V , is set to 1 only when one or more inputs are equal to 1. $V = D_3 + D_2 + D_1 + D_0$ by inspection.


Example: 4-to-2 Priority Encoder Truth Table

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Example: 4-to-2 Priority Encoder K-Maps

 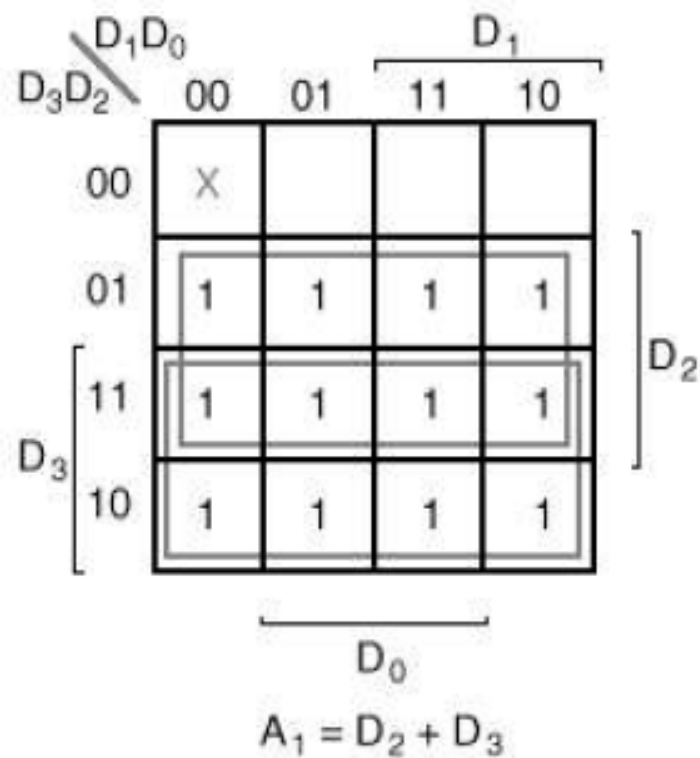

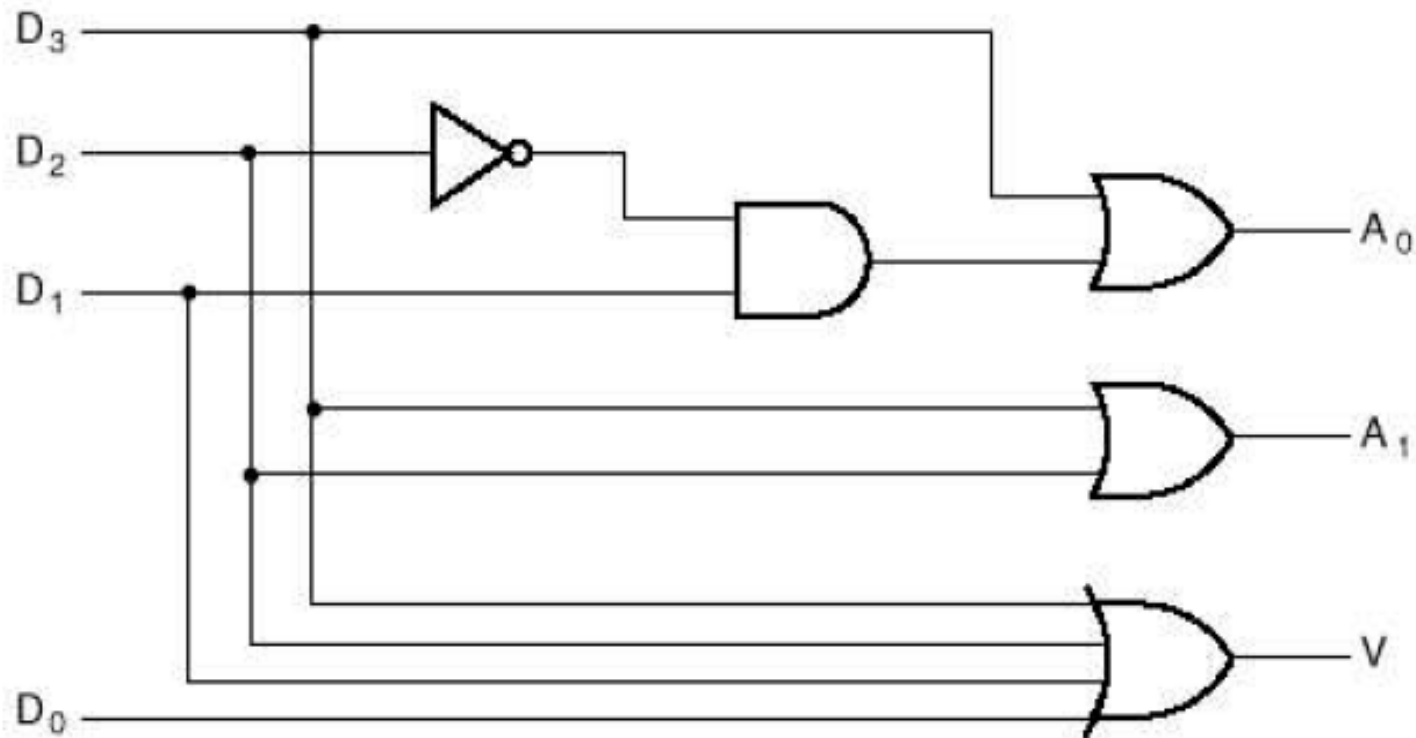Example: 4-to-2 Priority Encoder Logic Diagram




8-to-3 Priority Encoder


Table 4.6 A priority encoder.

[illegible]

Uses of binary Encoders

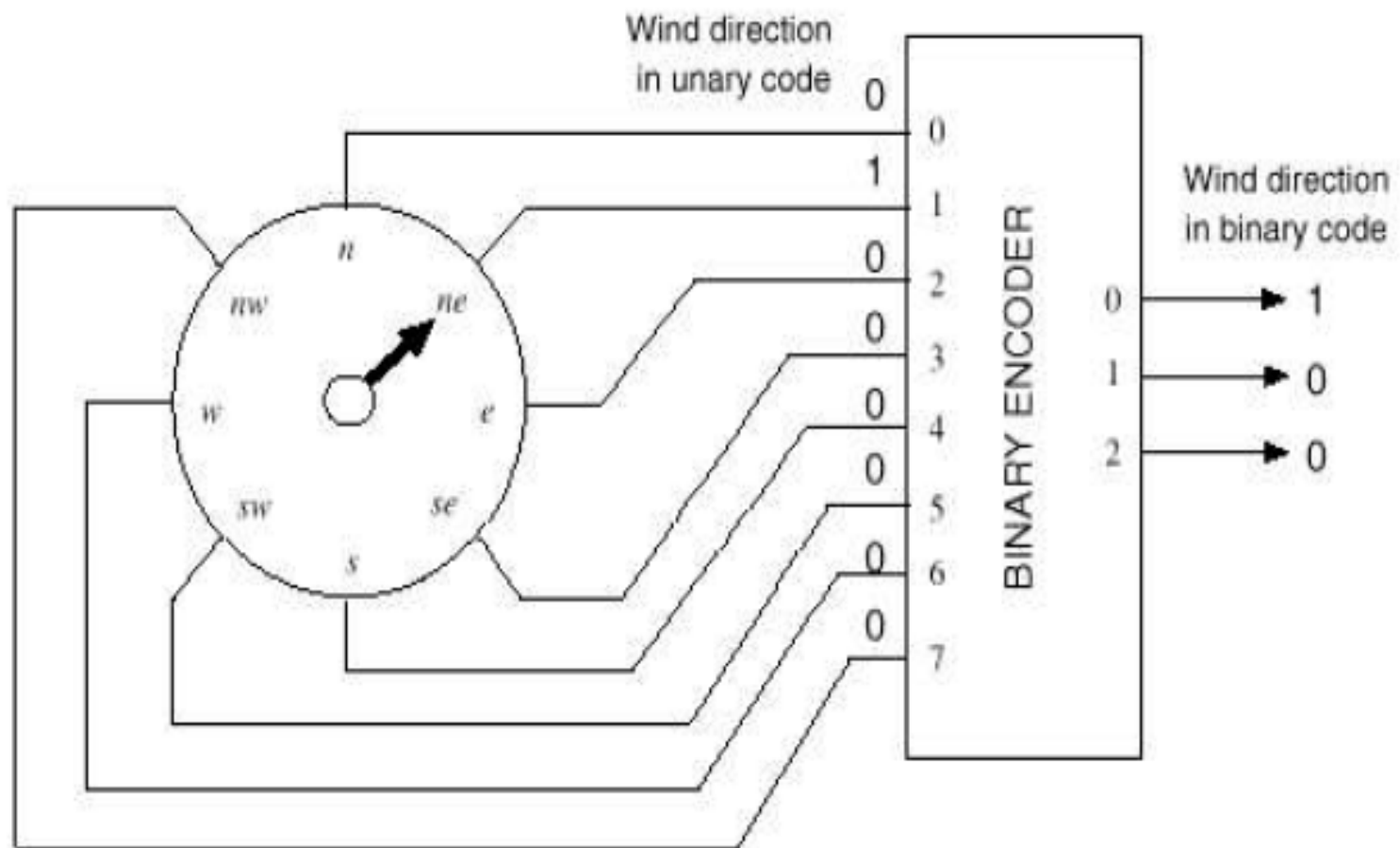


Uses of priority encoders (cont.)

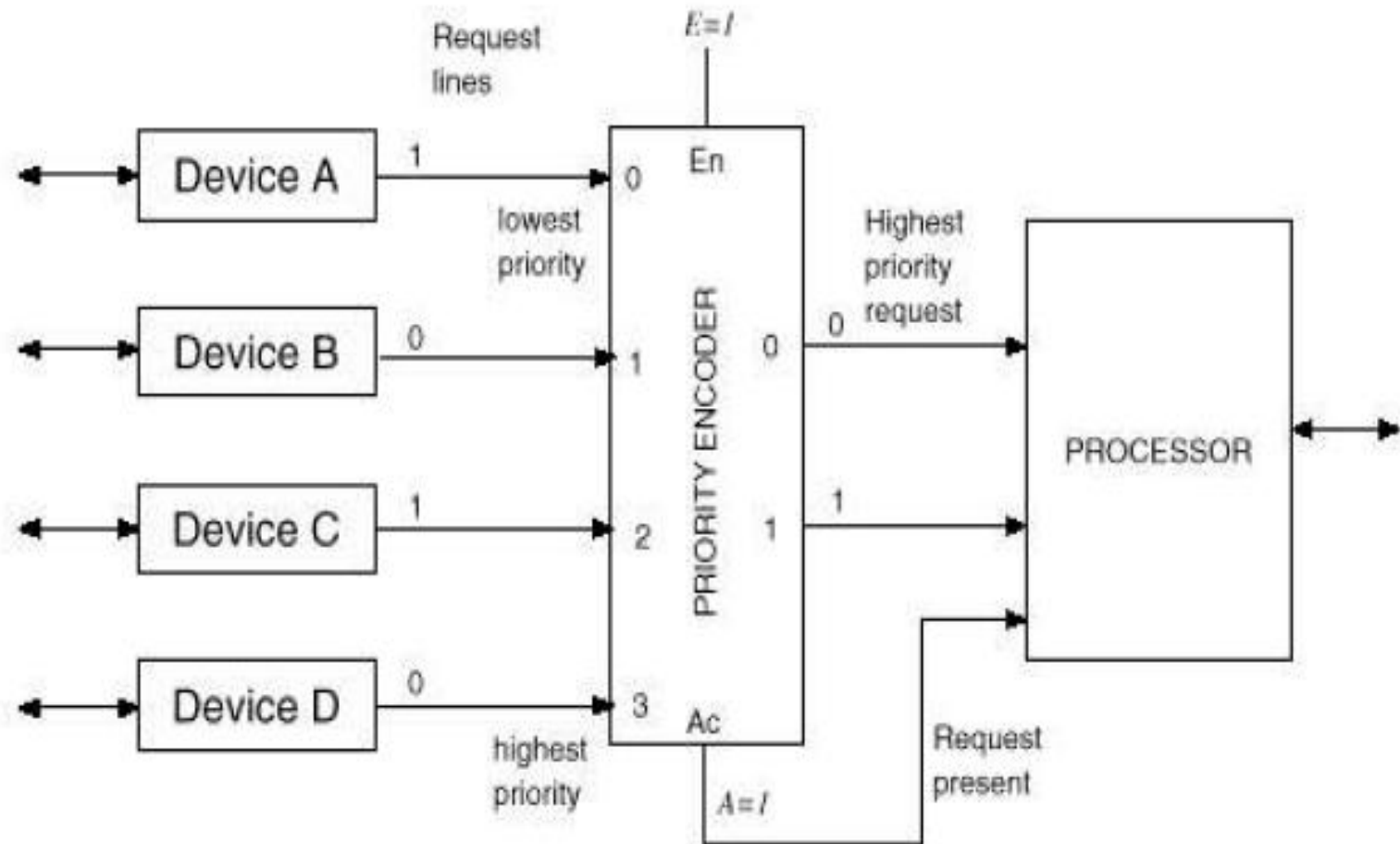

Multiplexers

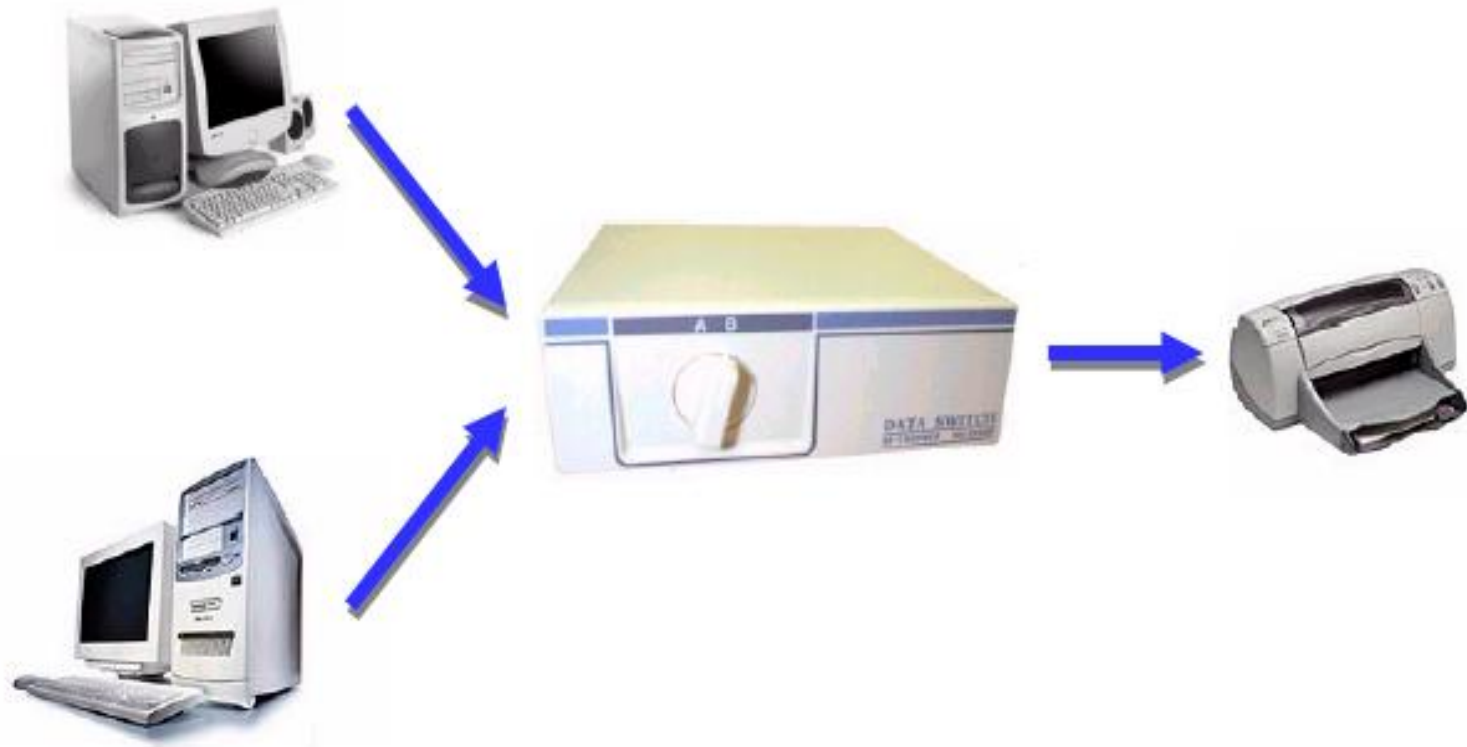
- Let's think about building another circuit, a **multiplexer**.
- In the old days, several machines could share an I/O device with a **switch**.



- The switch allows one computer's output to go to the printer's input.

A 2-to-1 multiplexer

 - Here is the circuit analog of that printer switch.



- This is a 2-to-1 multiplexer, or mux.
 - There are two data inputs D0 and D1, and a select input called S.
 - There is one output named Q.
- The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S.
 - If $S=0$, the output will be D0.
 - If $S=1$, the output will be D1.

Building a multiplexer

- Here is a truth table for the multiplexer, based on our description from the previous page:

The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S.


- If $S=0$, the output will be D0.
- If $S=1$, the output will be D1.

S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- You can then find an MSP for the mux output Q.


$$Q = S'D0 + S D1$$

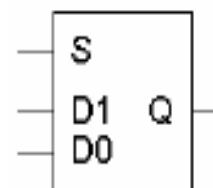- Note that this corresponds closely to our English specification above—sometimes you can derive an expression without first making a truth table.



Multiplexer circuit diagram

 - Here is an implementation of a 2-to-1 multiplexer.




$$Q = S'D0 + S D1$$

- Remember that a minimal sum of products expression leads to a minimal two-level circuit.

Enable inputs

- Many devices have an additional **enable input**, which “activates” or “deactivates” the device.
- We could design a 2-to-1 multiplexer with an enable input that’s used as follows.
 - EN=0 disables the multiplexer, which forces the output to be 0. (It does *not* turn off the multiplexer.)
 - EN=1 enables the multiplexer, and it works as specified earlier.
- Enable inputs are especially useful in combining smaller muxes together to make larger ones, as we’ll see later today.

 

EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1


A KVM switch

- This **KVM switch** allows four computers to share a single keyboard, video monitor, and mouse.



A 4-to-1 multiplexer

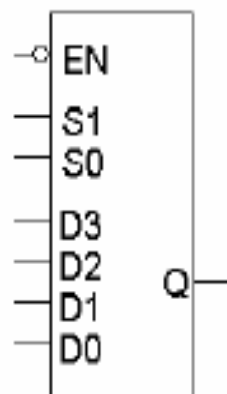- Here is a block diagram and abbreviated truth table for a 4-to-1 mux, which directs one of four different inputs to the single output line.
 - There are four data inputs, so we need *two* bits, **S1** and **S0**, for the mux selection input.




EN'	S1	S0	Q
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	x	x	1

$$Q = S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3$$

A 4-to-1 multiplexer implementation

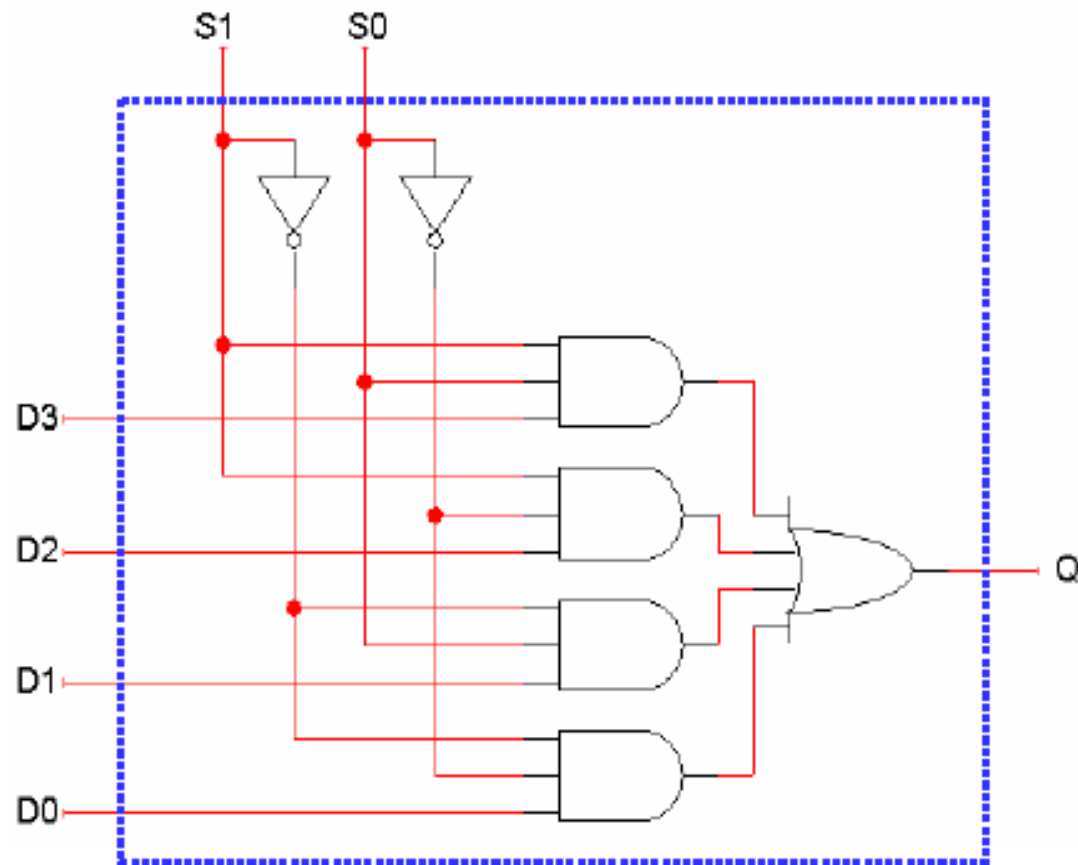
- Again we have a minimal sum of products expression, which leads to a minimal two-level circuit implementation.



$$Q = S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3$$

2^n -to-1 multiplexers

 - You can make even larger multiplexers, following the same pattern.
- A 2^n -to-1 multiplexer routes one of 2^n input lines to the output line.
 - There are 2^n data inputs, so there must also be n select inputs.
 - The output is a single bit.
- Here is an 8-to-1 multiplexer, probably the biggest we'll see in this class.



Example: addition

- Multiplexers can sometimes make circuit design easier.
- As an example, let's make a circuit to add three 1-bit inputs X , Y and Z .
- We'll need two bits to represent the total.
 - The bits will be called C and S , standing for "carry" and "sum."
 - These are two separate functions of the inputs X , Y and Z .
- A truth table and sum of minterm equations for C and S are shown below.


	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10 \rightarrow$	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11 \rightarrow$	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$
$$S(X,Y,Z) = \sum m(1,2,4,7)$$

Implementing functions with multiplexers

- We could implement a function of n variables with an n -to-1 multiplexer.
 - The mux select inputs correspond to the function's input variables, and are used to select one row of the truth table.
 - Each mux data input corresponds to one output from the truth table. We connect 1 to data input D_i for each function minterm m_i , and we connect 0 to the other data inputs.
- For example, here is the carry function, $C(X,Y,Z) = \Sigma m(3,5,6,7)$.

X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

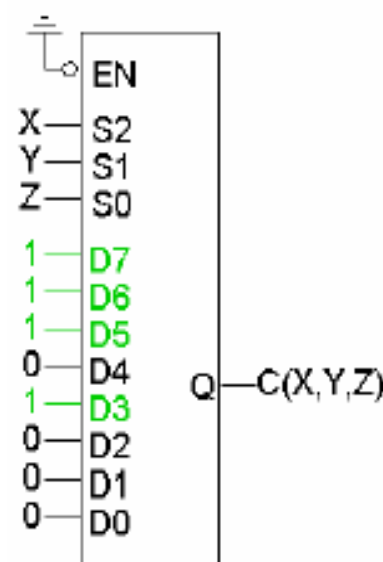

Partitioning the truth table

- We can actually implement $C(X,Y,Z) = \Sigma m(3,5,6,7)$ with just a 4-to-1 mux, instead of an 8-to-1.
 - Instead of using three variables to select one row of the truth table, we'll use two variables to pick a *pair* of rows in the table.
 - The multiplexer data inputs will be functions of the remaining variable, which distinguish between the rows in each pair.
- First, we can divide the rows of our truth table into pairs, as shown on the right. X and Y are constant within each pair of rows, so C is a function of Z only.
 - When $XY=00$, $C=0$
 - When $XY=01$, $C=Z$
 - When $XY=10$, $C=Z$
 - When $XY=11$, $C=1$

X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

A more efficient adder

- All that's left is setting the multiplexer inputs.
 - The two input variables X and Y will be connected to select inputs $S1$ and $S0$ of our 4-to-1 multiplexer.
 - The expressions for $C(Z)$ are then connected to the data inputs $D0$ - $D3$ of the multiplexer.


X	Y	Z	C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

When $XY=00$, $C=0$

When $XY=01$, $C=Z$

When $XY=10$, $C=Z$

When $XY=11$, $C=1$

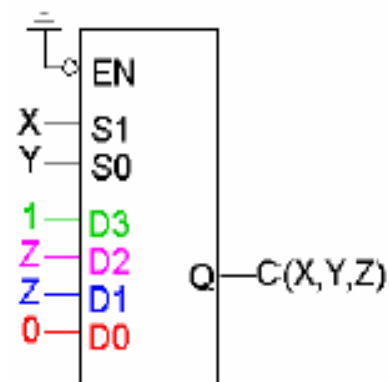


Verifying our adder

- Don't believe that this works? Start with the equation for a 4-to-1 multiplexer

$$Q = S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3$$

 - Then just plug in the actual inputs to our circuit, as shown again on the right: $S1S0 = XY$, $D3 = 1$, $D2 = Z$, $D1 = Z$, and $D0 = 0$.



$$\begin{aligned} C &= X'Y' \cdot 0 + X'YZ + XY'Z + XY \cdot 1 \\ &= X'YZ + XY'Z + XY \\ &= X'YZ + XY'Z + XY(Z' + Z) \\ &= X'YZ + XY'Z + XYZ' + XYZ \end{aligned}$$

- So the multiplexer output really is the carry function, $C(X,Y,Z) = \Sigma m(3,5,6,7)$.

Multiplexer-based sum

- Here's the same thing for the sum function, $S(X,Y,Z) = \Sigma m(1,2,4,7)$.


X	Y	Z	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

When $XY=00$, $S=Z$

When $XY=01$, $S=Z'$

When $XY=10$, $S=Z'$

When $XY=11$, $S=Z$

 


- Again, we can show that this is a correct implementation.

$$\begin{aligned} Q &= S1'S0'D0 + S1'S0 D1 + S1 S0'D2 + S1 S0 D3 \\ &= X'Y'Z + X'YZ' + XY'Z' + XYZ \\ &= \Sigma m(1,2,4,7) \end{aligned}$$

Dual multiplexers

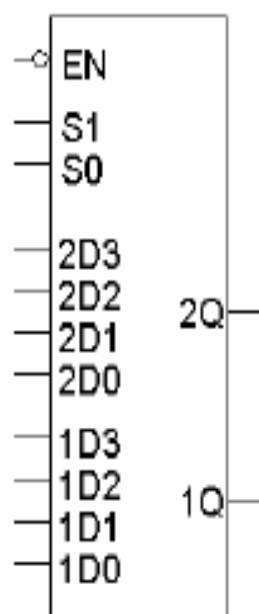
- A **dual 4-to-1 mux** allows you to select from one of four 2-bit data inputs.
 - The two output bits are 2Q 1Q, and S1-S0 select a *pair* of inputs.



EN'	S1	S0	2Q	1Q
0	0	0	2D0	1D0
0	0	1	2D1	1D1
0	1	0	2D2	1D2
0	1	1	2D3	1D3
1	x	x	1	1


Dual muxes in more detail

- You could build a dual 4-to-1 mux from its truth table and our familiar circuit design techniques.
- It's also possible to combine smaller muxes together to form larger ones.
- You can build the dual 4-to-1 mux just by using two 4-to-1 muxes.
 - The two 4-to-1 multiplexers share the same EN' , $S1$ and $S0$ signals.
 - Each smaller mux produces one bit of the two-bit output $2Q$ $1Q$.
- This kind of hierarchical design is very common in computer architecture.

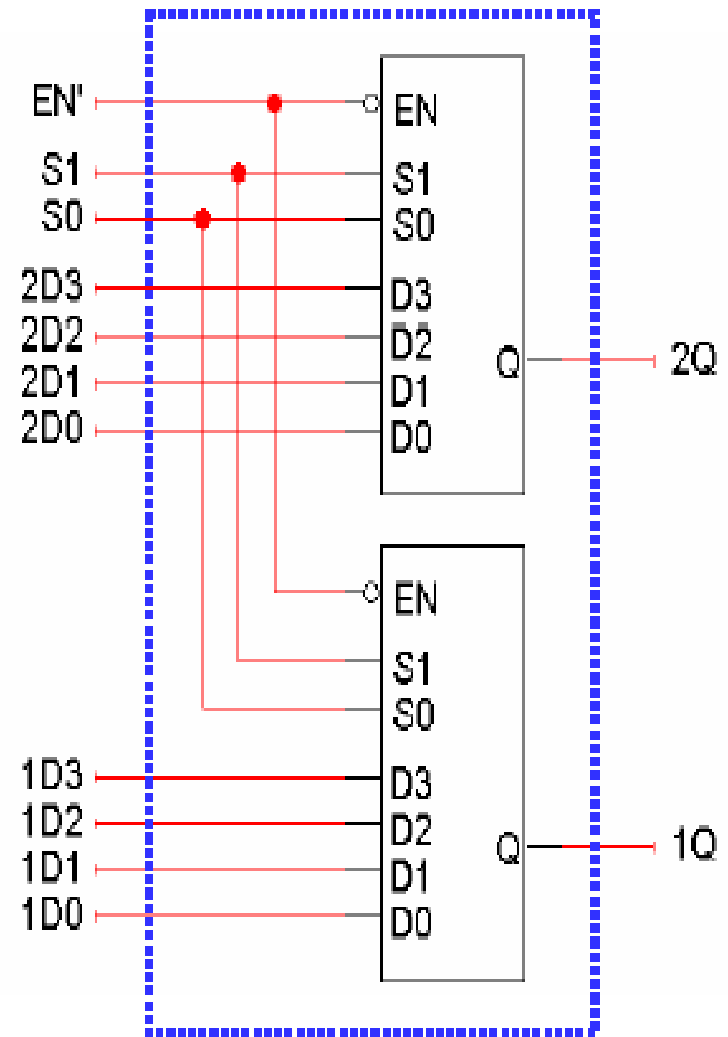

Dual multiplexer-based adder

 - We can use this dual 4-to-1 multiplexer to implement our adder, which produces a two-bit output consisting of C and S.



- That KVM switch from earlier is really a "tri 4-to-1 multiplexer," since it selects from four sets of three signals (keyboard, video and mouse).

De Multiplexers

A De-multiplexer is a logic circuit that transmit Information on a single line on one of 2^n output lines


Selection of output line depends on the value of n select lines

A Decoder with enable input can function as a De-multiplexer

Enable inputs

decoders can include **enable inputs**.

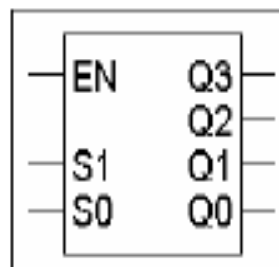- **EN=0** disables the decoder, which by convention means that all of the decoder's outputs are 0.
- **EN=1** enables the decoder so that it behaves as specified earlier, with exactly one of the outputs being 1.



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1