

BINARY MULTIPLIER

- ➔ To Multiply two unsigned binary numbers.**
- ➔ Sequential Multiplier**
- ➔ Uses one adder and a shift register.**

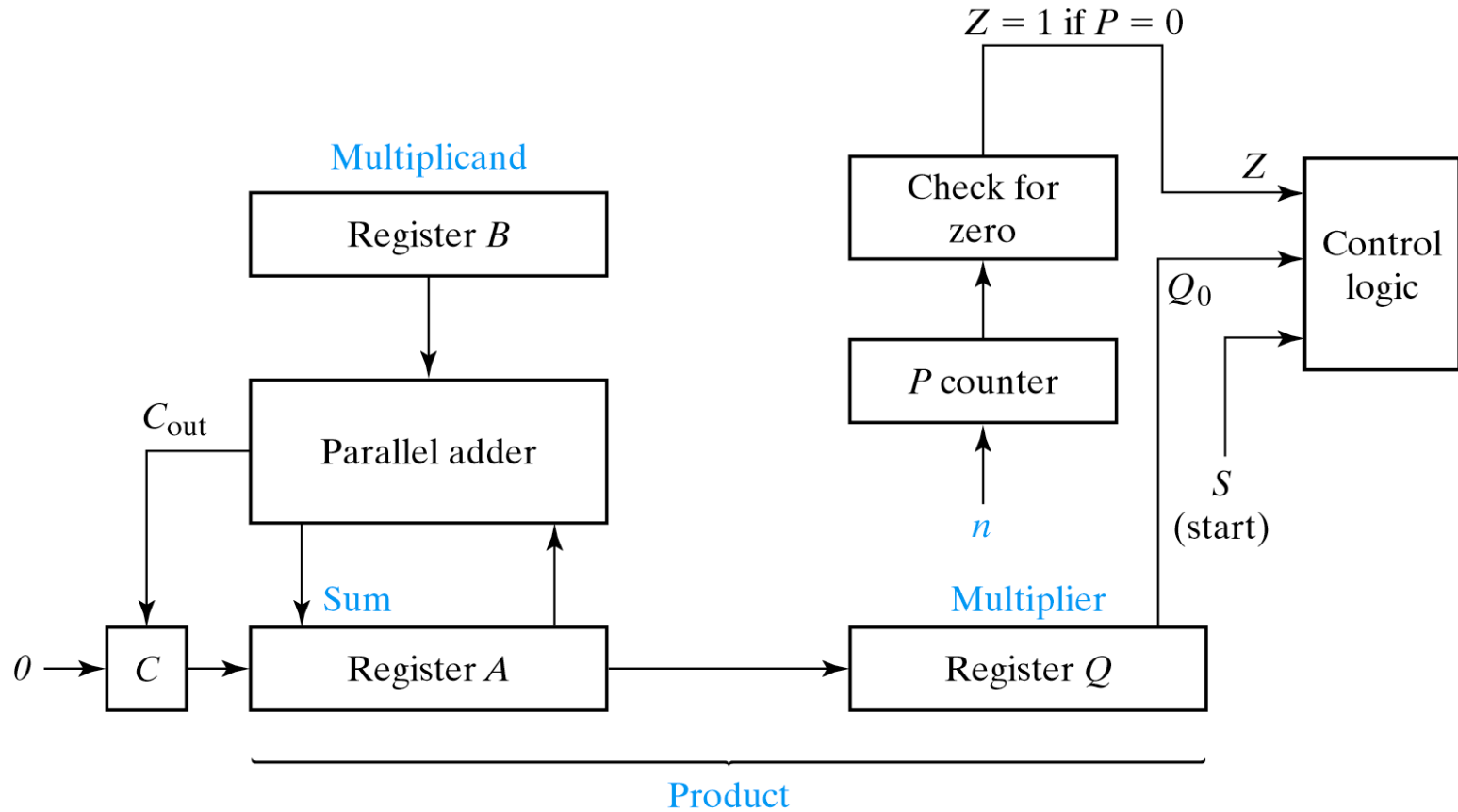


Fig. 8-13 Block Diagram of Binary Multiplier

- ➔ **Initially Multiplier in Q and Multiplicand in B**
- ➔ **With $S = 0$ no action and circuit is in state T0**
- ➔ **Multiplication process starts when $S = 1$ and control goes to T1.**
- ➔ **Register A and C set to 0 and counter P set to n, the number of bits in multiplier.**
- ➔ **System goes to T2.**

- ➔ Multiplier bit Q_0 is checked and if $= 1$, multiplicand B added to partial product A .
- ➔ Carry from addition transferred to C
- ➔ Partial product in A and C left unchanged if $Q_0 = 0$
- ➔ P decremented, next state is T_3 .
- ➔ Registers CAQ shifted once to right

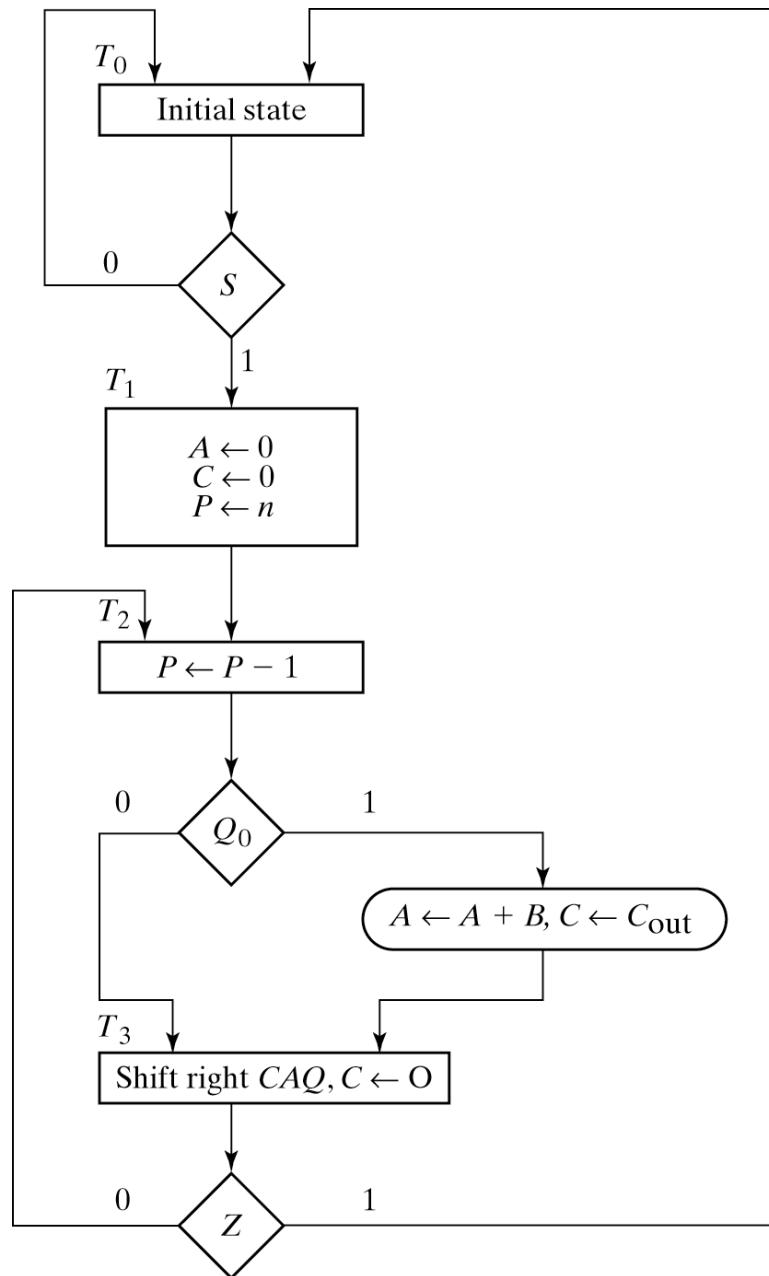



Fig. 8-14 ASM Chart for Binary Multiplier

Design steps:

- ➔ Design of register operations in the datapath**
- ➔ Design of control logic**

Diamond boxes determine the conditions for next state transition

 Register transfer operations come from State and Conditional boxes



(a) State diagram

T_0 : Initial state

T_1 : $A \leftarrow 0, C \leftarrow 0, P \leftarrow n$

T_2 : $P \leftarrow P - 1$

if $(Q_0) = 1$ then $(A \leftarrow A + B, C \leftarrow C_{\text{out}})$

T_3 : shift right $CAQ, C \leftarrow 0$

(b) Register transfer operations

Fig. 8-15 Control Specifications for Binary Multiplier

In the design of control logic:

➔ Establish required sequence of operations & provide signals to control register transfer operations.

➔ Sequence specified in state diagram

➔ Signals for controlling register operations:

T1 (for clearing A and C), T2 (for decrementing P)

T3(for shifting CAQ), Q0 to decide whether to add B or not

 


Fig. 8-16 Control Block Diagram

Inputs S and Z , outputs T_0 , T_1 , T_2 , T_3

$L = T_2Q_0$ to load sum into A if $Q_0 = 1$ while in T_2 .

State assignment for control

State	Binary	Gray code	One-Hot
T0	00	00	0001
T1	01	01	0010
T2	10	11	0100
T3	11	10	1000

Control logic design using sequence register and decoder

- ➔ An n bit sequence register is a circuit with n flip-flops**
- ➔ Multiplier having four states and two inputs needs two flip-flops for the register and a 2:4 decoder for outputs**

State Table:

Present state		Inputs		Next state		Outputs			
G1	G0	S	Z	G1	G0	T0	T1	T2	T3
0	0	0	X	0	0	1	0	0	0
0	0	1	X	0	1	1	0	0	0
0	1	X	X	1	0	0	1	0	0
1	0	X	X	1	1	0	0	1	0
1	1	X	0	1	0	0	0	0	1
1	1	X	1	0	0	0	0	0	1

- ➔ Input columns have don't care entries whenever the input variable is not used to determine the next state
- ➔ Outputs are functions of present state, generated with a Decoder with two inputs (G_1 G_0) and four outputs ($T_0 - T_3$)
- ➔ Next state of G_1 is equal to 1
 - when the present state is T_1 ,
 - when the present state is T_2 ,
 - when the present state is T_3 , provided $Z = 0$

So we write:

$$DG_1 = T_1 + T_2 + T_3Z'$$

Similarly:

$$DG_0 = T_0S + T_2.$$

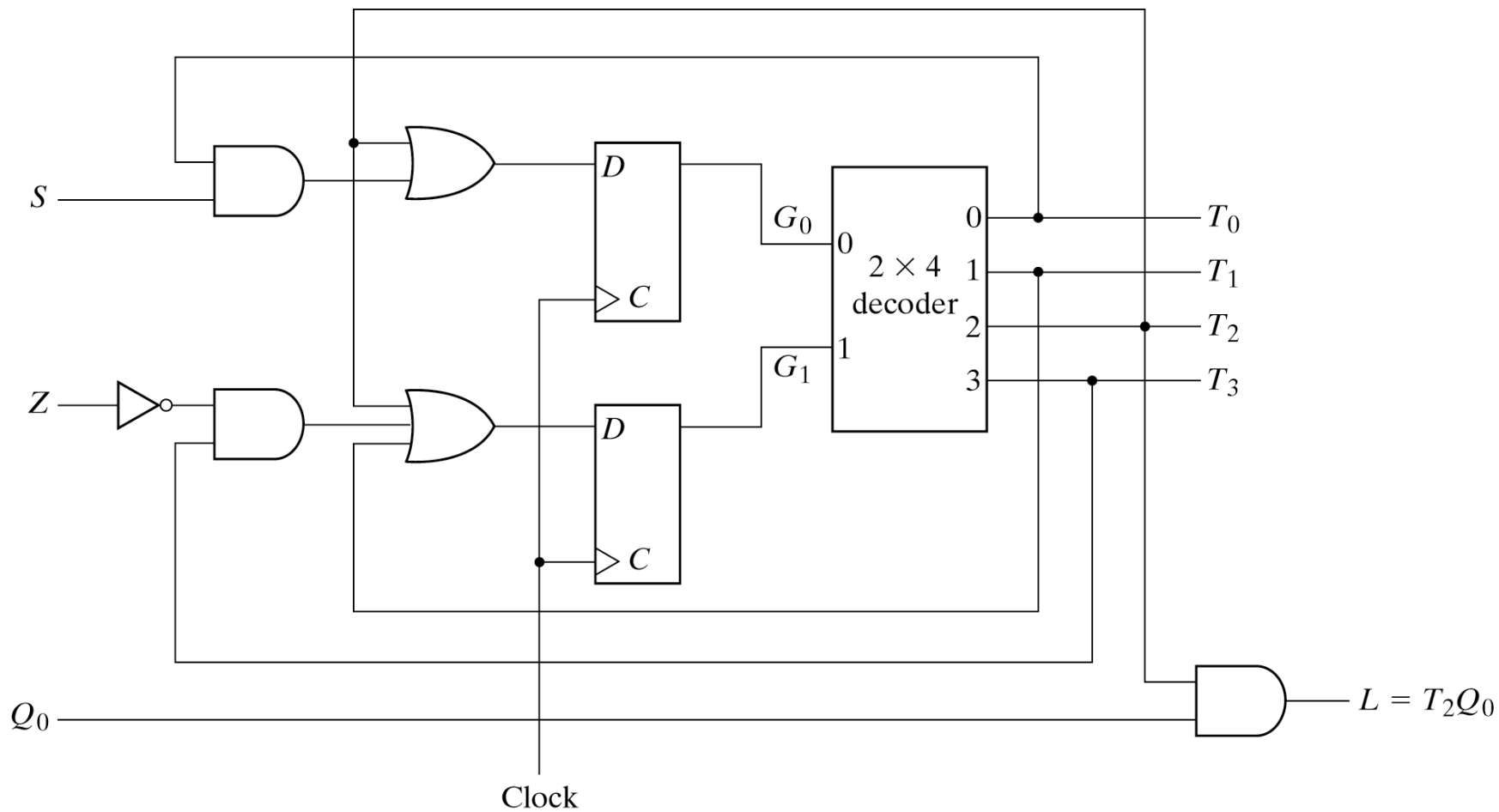


Fig. 8-17 Logic Diagram of Control for Binary Multiplier Using a Sequence Register and Decoder

Use of One Hot assignment which uses one Flip-flop per state

Single 1 propagates from one flip-flop to another under the control of decision logic.

$$\mathbf{DT0 = T0S' + T3Z}$$

$$\mathbf{DT1 = T0S}$$

$$\mathbf{DT2 = T1 + T3Z'}$$

$$\mathbf{DT3 = T2.}$$

 


Fig. 8-18 One Flip-Flop Per State Controller

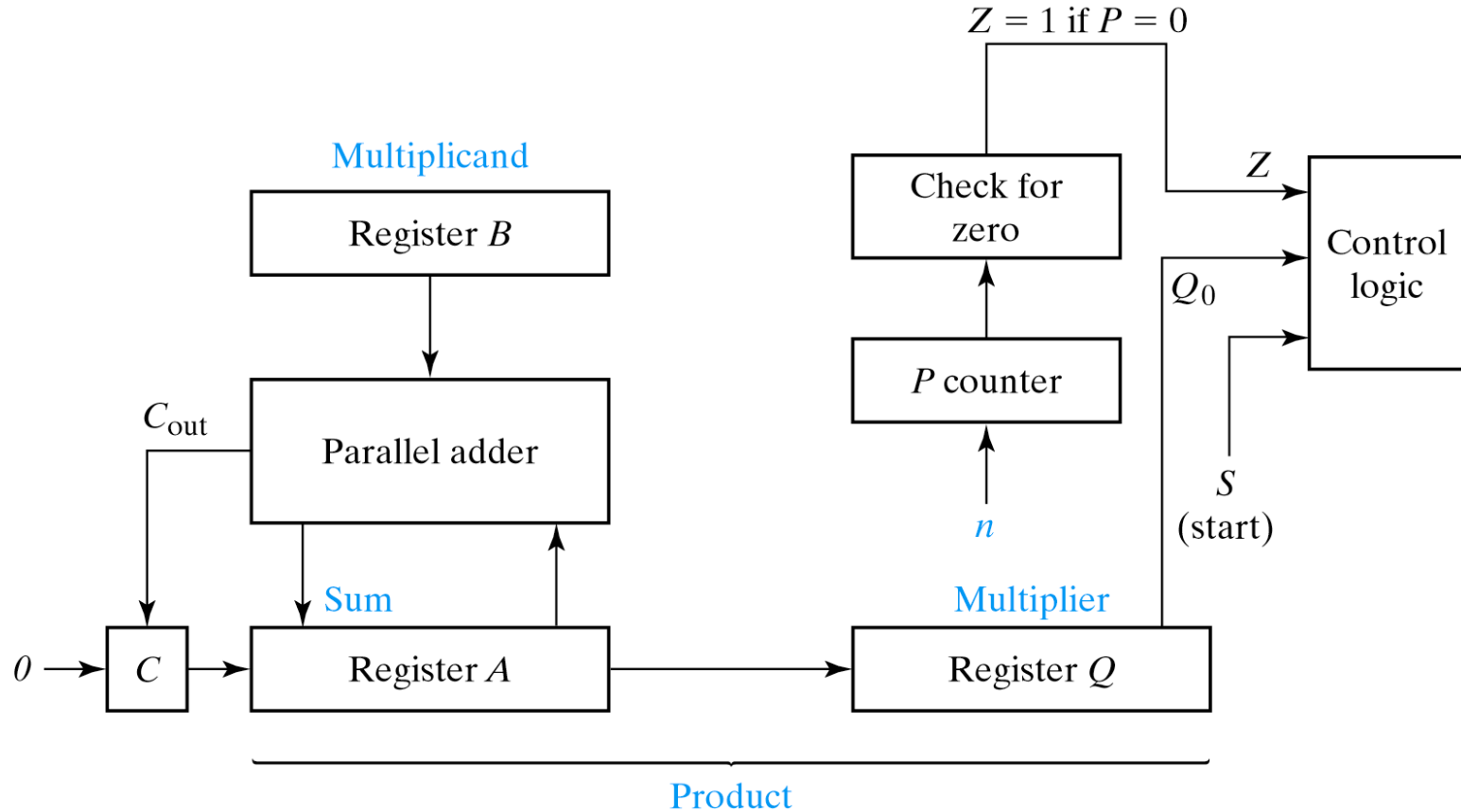


Fig. 8-13 Block Diagram of Binary Multiplier

**T1 (for clearing A ,C and load P), T2 (for decrementing P)
T3(for shifting CAQ), T2Q0 to decide whether to Load A or not**

Design with Multiplexers

- ➔ **Combinational circuit can be implemented with Multiplexers instead of gates.**
- ➔ **Results in regular pattern of three level of components.**
 - 1. Multiplexers that determine next state of register**
 - 2. Registers that hold the present state**
 - 3. Decoders that provide separate output for control state**

Predefined standard cell in many ICs.

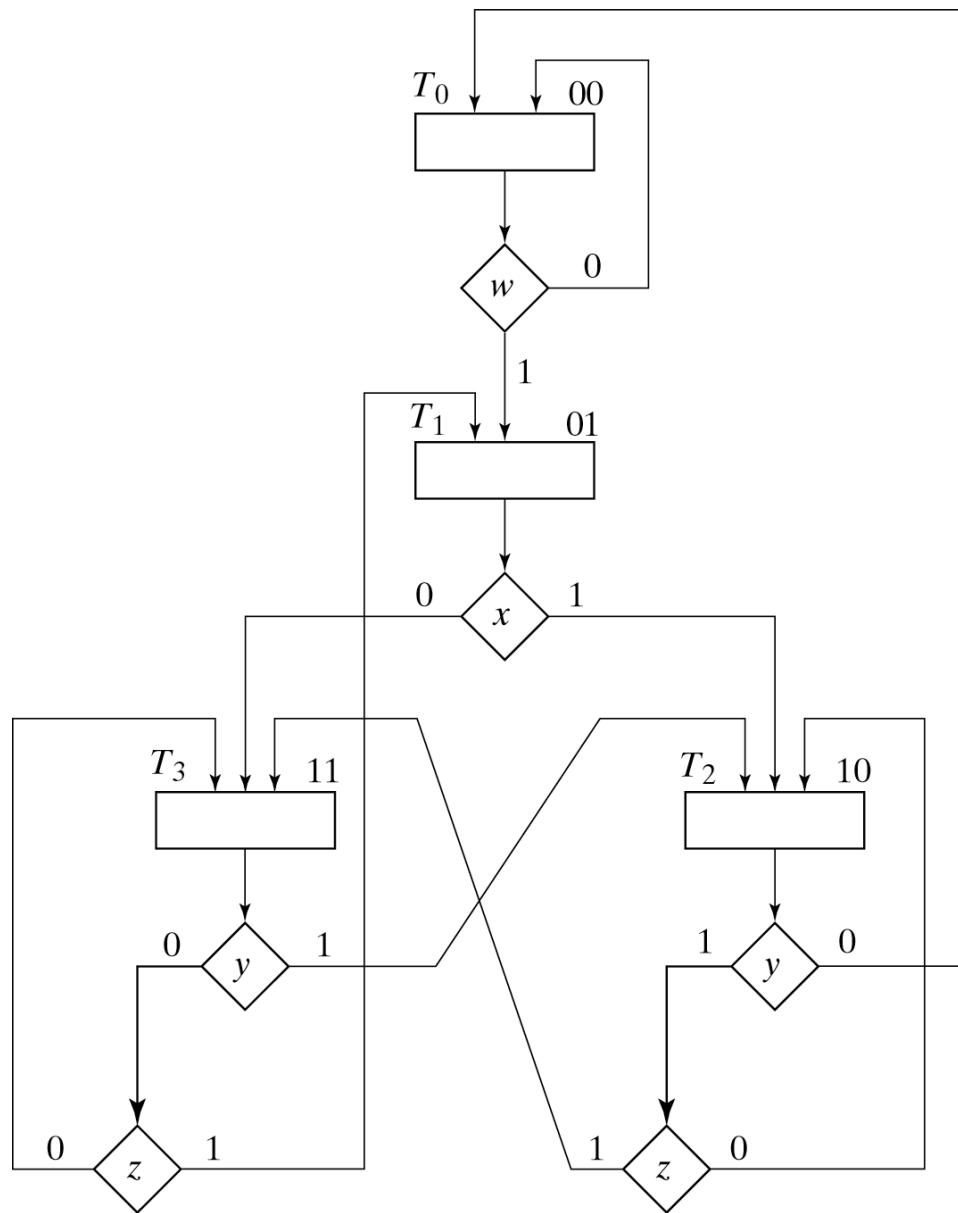


Fig. 8-19 Example of ASM Chart with Four Control Inputs

- ➔ **State boxes left empty as it is only to design Control sequence**
- ➔ **Binary assignments specified at upper right corner**
- ➔ **Decision boxes specify state transition as a function of four control inputs w, x, y, z**
- ➔ **Three level control implementation includes MUX, registers and decoders**

Multiplexer input conditions

Present state		Next state		Input conditions	Inputs	
G1	G0	G1	G0		MUX1	MUX2
0	0	0	0	w'		
0	0	0	1	w	0	w
0	1	1	0	x		
0	1	1	1	x'	1	x'
1	0	0	0	y'		
1	0	1	0	yz'	$yz' + yz = y$	yz
1	0	1	1	yz		
1	1	0	1	$y'z$		
1	1	1	0	y		
1	1	1	1	$y'z'$	$y + y'z' = y + z'$	$y'z + y'z' = y'$

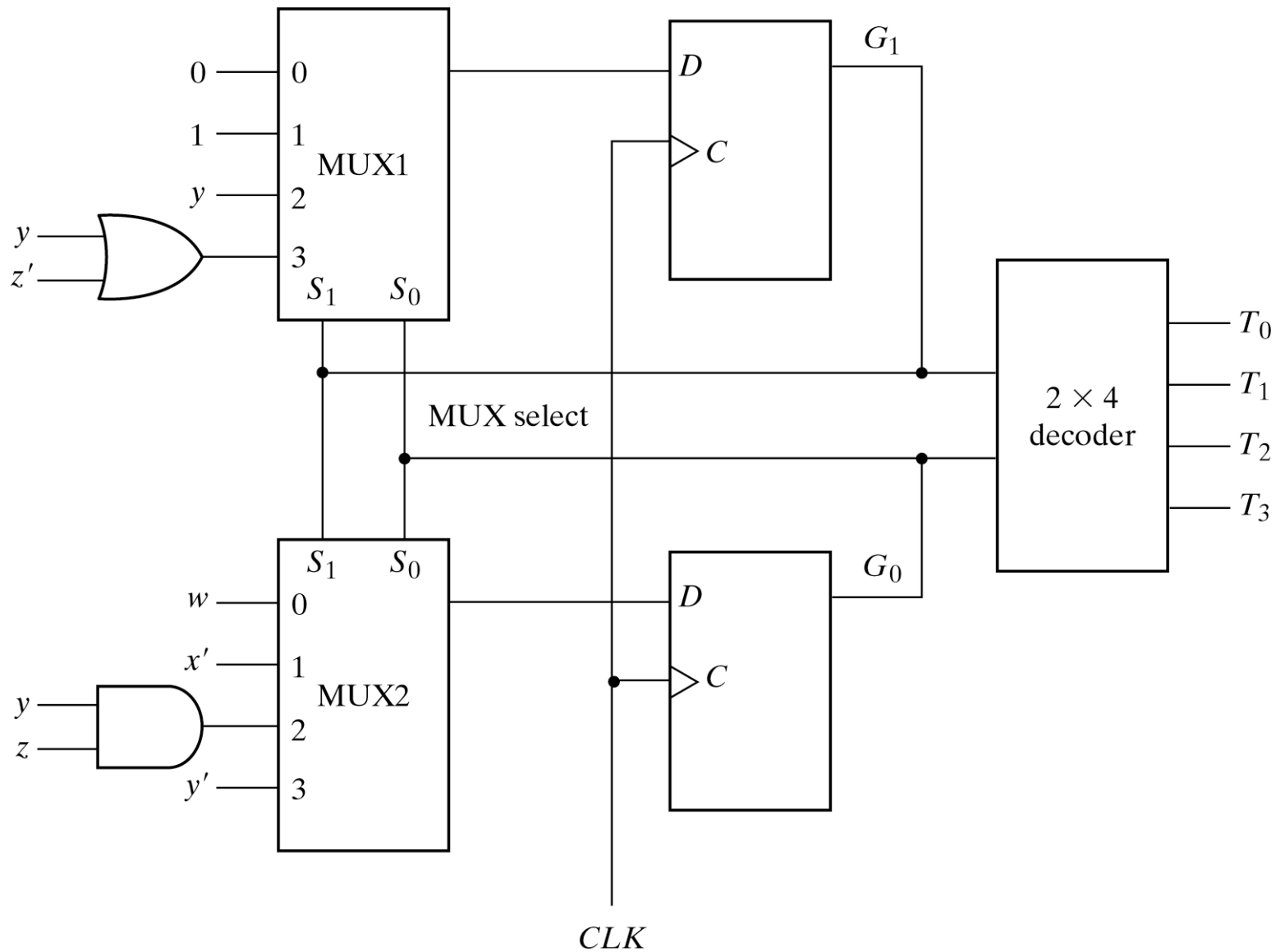


Fig. 8-20 Control Implementation with Multiplexers

Design Example:

Count number of 1's in a register

Two registers R1 and R2 and Flip-flop E

- System counts number of 1's in R1 and sets R2 to that number.**
- Done by shifting each bit in R1 one at a time into E, E checked by control and if 1 R2 is incremented.**
- Control uses external input S to start and uses status input E and Z from datapath.
Z = 1 when R1 = 0**

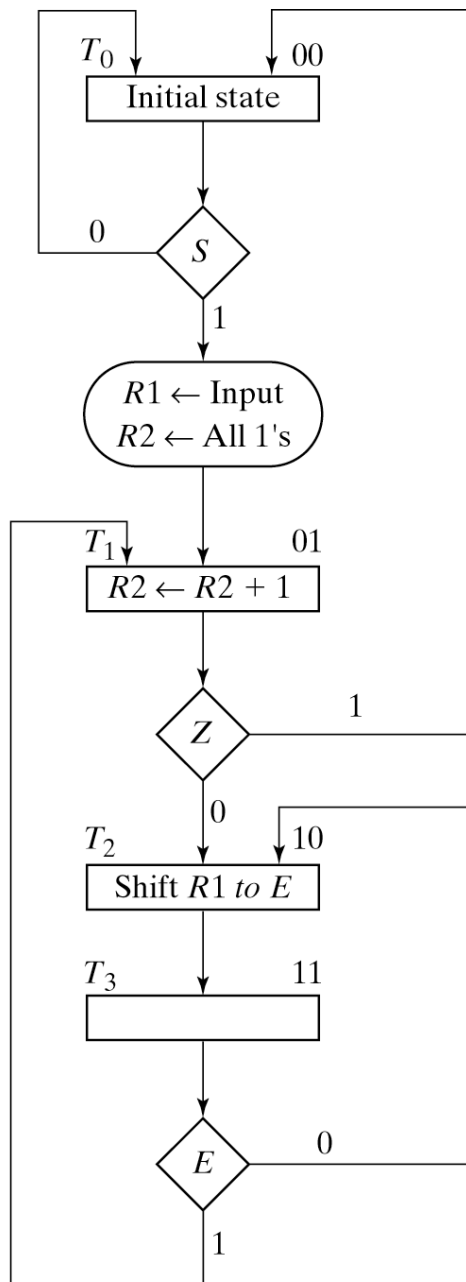


Fig. 8-21 ASM Chart for Count-of-Ones Circuit

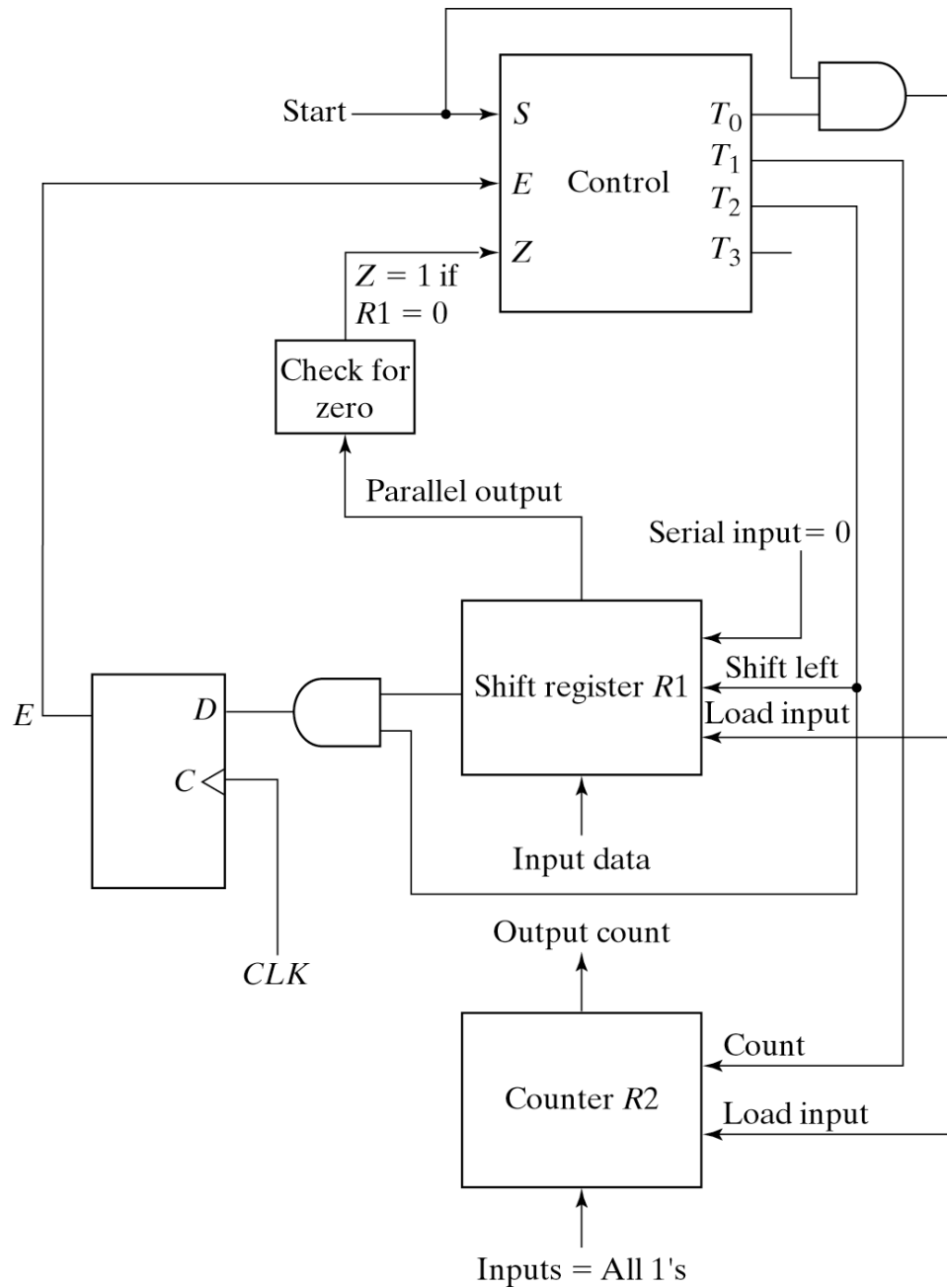


Fig. 8-22 Block Diagram for Count-of-Ones

Multiplexer input conditions

Present state		Next state		Input	Inputs	
G1	G0	G1	G0	conditions	MUX1	MUX2
0	0	0	0	S'		
0	0	0	1	S	0	S
0	1	0	0	Z		
0	1	1	0	Z'	Z'	0
1	0	1	1	None	1	1
1	1	1	0	E'		
1	1	0	1	E	E'	E

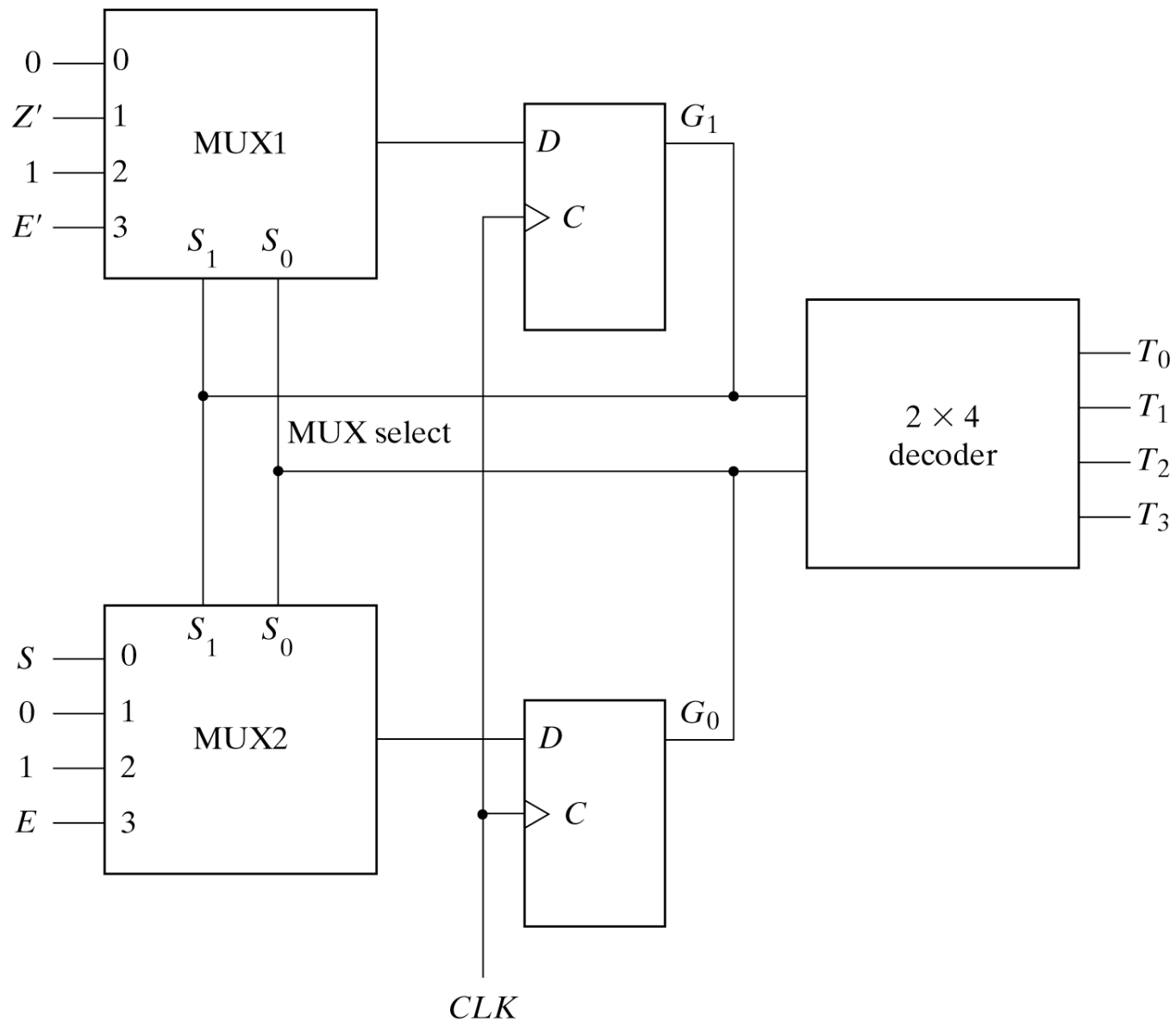


Fig. 8-23 Control Implementation for Count-of-Ones Circuit