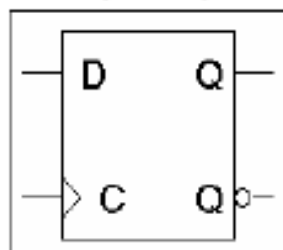


ANALYSIS OF SEQUENTIAL CIRCUITS

Flip-flop review

Flip-flops




Characteristic tables

| D | Q(t+1) | Operation |
|---|--------|-----------|
| 0 | 0 | Reset |
| 1 | 1 | Set |


Characteristic equations

$$Q(t+1) = D$$

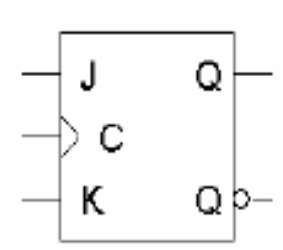

| J | K | Q(t+1) | Operation |
|---|---|--------|------------|
| 0 | 0 | Q(t) | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | Q'(t) | Complement |

$$Q(t+1) = K'Q(t) + JQ'(t)$$


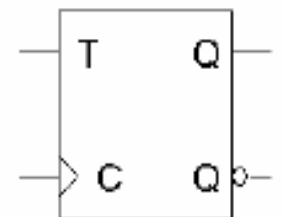


| T | Q(t+1) | Operation |
|---|--------|------------|
| 0 | Q(t) | No change |
| 1 | Q'(t) | Complement |

$$Q(t+1) = T \oplus Q(t)$$

What do sequential circuits look like?

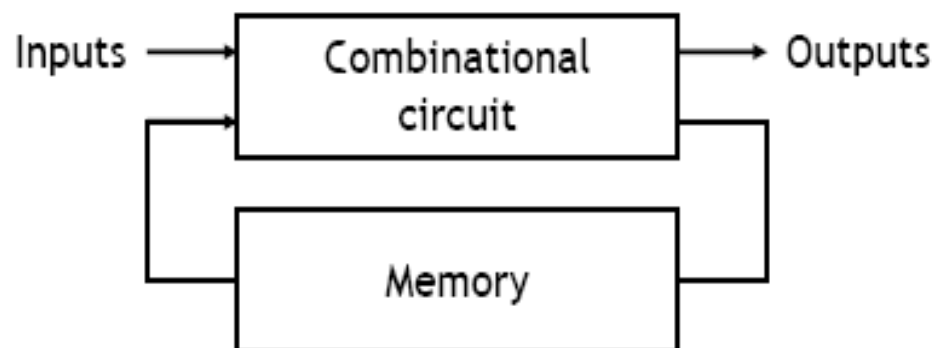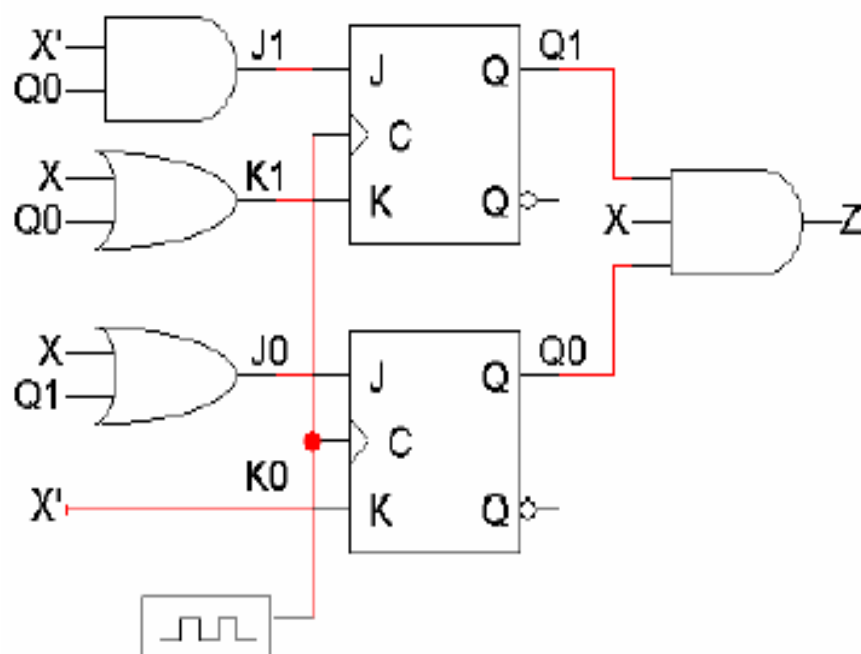- Here is a sequential circuit with two JK flip-flops. There is one input X and one output Z .
- The values of the flip-flops (Q_1Q_0) form the **state**, or the memory, of the circuit.
- The flip-flop outputs also go back into the primitive gates on the left. This matches the abstract sequential circuit diagram at the bottom.




How do you analyze a sequential circuit?

- We can analyze a combinational circuit by deriving a truth table, which shows how the circuit outputs are generated from its inputs.
- But in a sequential circuit, the outputs are dependent upon not only the inputs, but also the current state of the flip-flops. So to understand how a sequential circuit works, we have to know how the memory changes.
- A **state table** is the sequential analog of a truth table. It shows inputs *and* current states on the left, and outputs *and* next states on the right.

How do you analyze a sequential circuit?


- We can analyze a combinational circuit by deriving a truth table, which shows how the circuit outputs are generated from its inputs.
- But in a sequential circuit, the outputs are dependent upon not only the inputs, but also the current state of the flip-flops. So to understand how a sequential circuit works, we have to know how the memory changes.
- A **state table** is the sequential analog of a truth table. It shows inputs *and* current states on the left, and outputs *and* next states on the right.

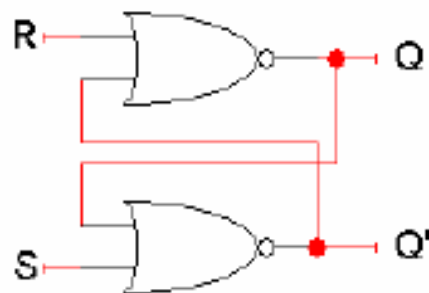

| Inputs | | Current | | Next | |
|--------|---|---------|----|------|----|
| S | R | Q | Q' | Q | Q' |
| 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |

Analyzing our example circuit

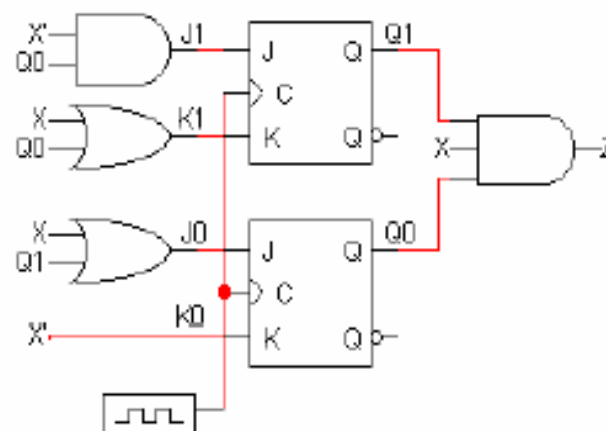- A state table for our example circuit is shown below.
- The present state Q_1Q_0 and the input X will determine the next state Q_1Q_0 and the output Z .




| Present State | | Inputs X | Next State | | Outputs Z |
|---------------|-------|---------------|------------|-------|----------------|
| Q_1 | Q_0 | | Q_1 | Q_0 | |
| 0 | 0 | 0 | | | |
| 0 | 0 | 1 | | | |
| 0 | 1 | 0 | | | |
| 0 | 1 | 1 | | | |
| 1 | 0 | 0 | | | |
| 1 | 0 | 1 | | | |
| 1 | 1 | 0 | | | |
| 1 | 1 | 1 | | | |

The outputs are easy

- From the diagram, you can see that

$$Z = Q_1 Q_0 X$$

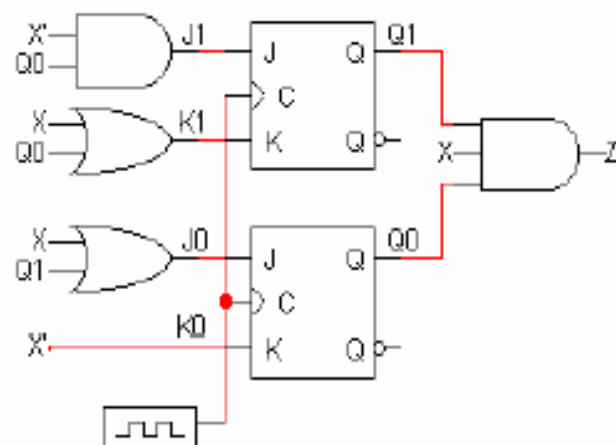- This is an example of a **Mealy machine**, where the output depends on both the present state ($Q_1 Q_0$) and the input (X).



| Present State | | Inputs | Next State | | Outputs |
|---------------|-------|--------|------------|-------|---------|
| Q_1 | Q_0 | X | Q_1 | Q_0 | Z |
| 0 | 0 | 0 | | | 0 |
| 0 | 0 | 1 | | | 0 |
| 0 | 1 | 0 | | | 0 |
| 0 | 1 | 1 | | | 0 |
| 1 | 0 | 0 | | | 0 |
| 1 | 0 | 1 | | | 0 |
| 1 | 1 | 0 | | | 0 |
| 1 | 1 | 1 | | | 1 |

Flip-flop input equations

- Finding the next states is harder. To do this, we have to figure out how the flip-flops are changing.
 1. Find Boolean expressions for the flip-flop inputs.
 2. Use these expressions to find the actual flip-flop input values for each possible combination of present states and inputs.
 3. Use flip-flop characteristic tables or equations to find the next states, based on the flip-flop input values and the present states.

Step 1: Flip-flop input equations


- For our example, the **flip-flop input equations** are:

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

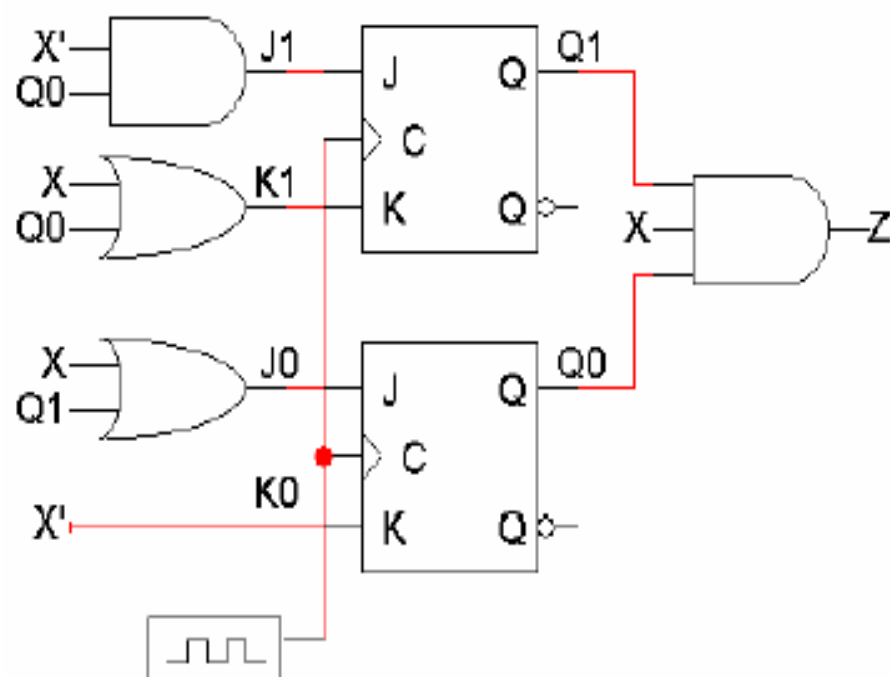

Step 2: Flip-flop input values

- With these equations, we can make a table showing J_1 , K_1 , J_0 and K_0 for the different combinations of present state Q_1Q_0 and input X .

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

| Present State | | Inputs X | Flip-flop Inputs | | | |
|---------------|-------|---------------|------------------|-------|-------|-------|
| Q_1 | Q_0 | | J_1 | K_1 | J_0 | K_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 |

Step 3: Find the next states

- Finally, use the JK flip-flop characteristic tables or equations to find the next state of *each* flip-flop, based on its present state and inputs.
- The general JK flip-flop characteristic equation was given earlier today.

$$Q(t+1) = K'Q(t) + JQ'(t)$$

- In our example circuit, we have two JK flip-flops, so we have to apply this equation to *each* of them.

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

Step 3 concluded

- Finally, here are the next states for Q_1 and Q_0 , using these equations.

$$Q_1(t+1) = K_1'Q_1(t) + J_1Q_1'(t)$$

$$Q_0(t+1) = K_0'Q_0(t) + J_0Q_0'(t)$$

| Present State | | Inputs X | Flip-flop Inputs | | | | Next State | |
|---------------|-------|-------------|------------------|-------|-------|-------|------------|-------|
| Q_1 | Q_0 | | J_1 | K_1 | J_0 | K_0 | Q_1 | Q_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |

Getting the state table columns straight

- The table starts with **Present State** and **Inputs**.
 - **Present State** and **Inputs** yield **FF Inputs**.
 - **Present State** and **FF Inputs** yield **Next State**, based on the flip-flop characteristic tables.
 - **Present State** and **Inputs** yield **Output**.
- We really only care about **FF Inputs** in order to find **Next State**.

| Present State | | Inputs | Flip-flop Inputs | | | | Next State | | Output |
|---------------|-------|--------|------------------|-------|-------|-------|------------|-------|--------|
| Q_1 | Q_0 | X | J_1 | K_1 | J_0 | K_0 | Q_1 | Q_0 | Z |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |


State diagrams

- We can also represent the state table graphically with a **state diagram**.
 - The diagram has one **node** for each possible state.
 - **Arrows** in the diagram connect present states to next states, and are labelled with “input/output.”

State diagrams

- We can also represent the state table graphically with a **state diagram**.
 - The diagram has one **node** for each possible state.
 - **Arrows** in the diagram connect present states to next states, and are labelled with “input/output.”
- A diagram corresponding to our example state table is shown below.


| Present State | | Inputs | Next State | | Output |
|---------------|-------|--------|------------|-------|--------|
| Q_1 | Q_0 | | Q_1 | Q_0 | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 |

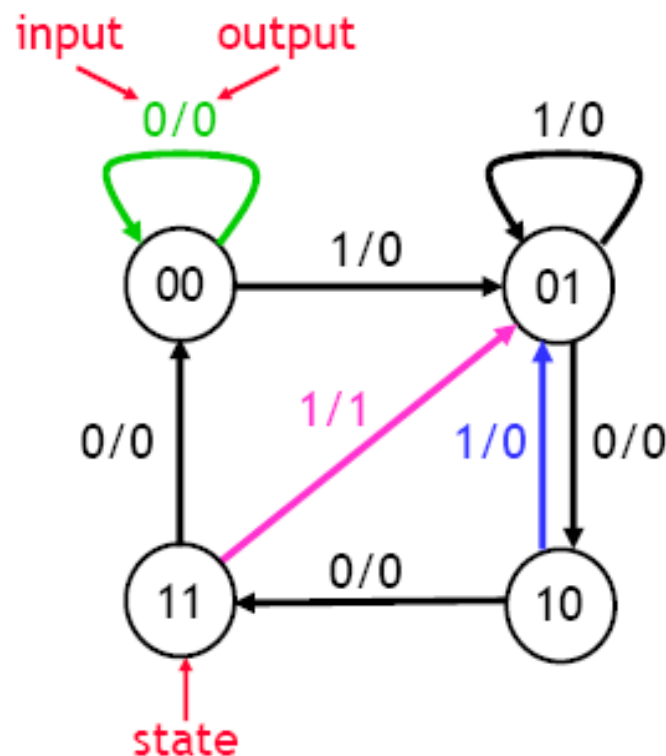

Size of the state diagram


- Always check the size of your state diagrams.
 - If there are n flip-flops, there should be 2^n nodes in the diagram.
 - If there are m inputs, then each node will have 2^m outgoing arrows.
- Our example circuit has two flip-flops and one input, so the state diagram should have four nodes, each with two outgoing arrows.

| Present State | | Inputs X | Next State | | Output Z |
|---------------|-------|---------------|------------|-------|---------------|
| Q_1 | Q_0 | | Q_1 | Q_0 | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 |

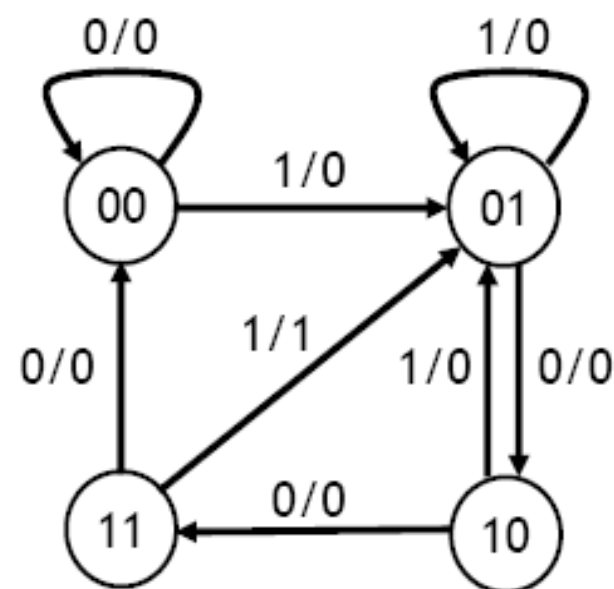

A D flip-flop example

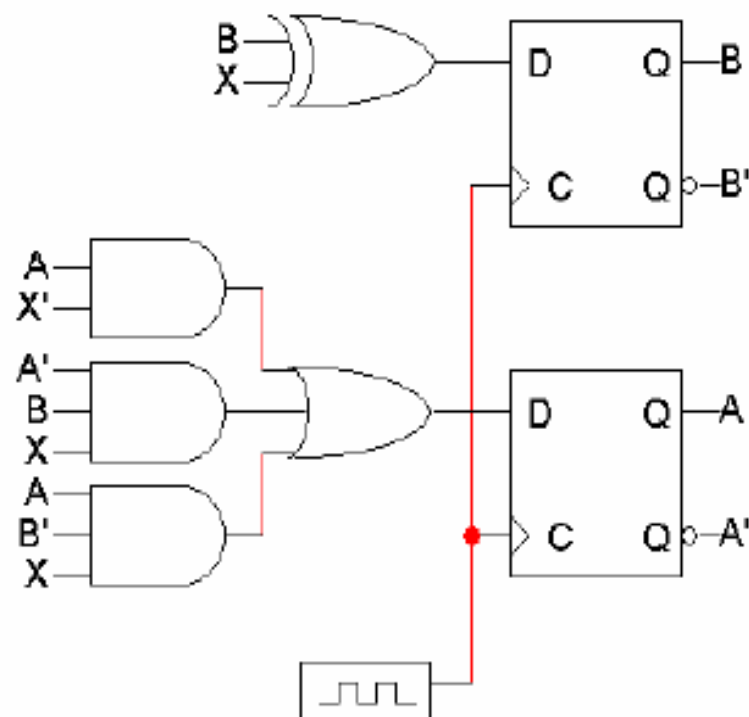
- Here are two D flip-flops, with values labelled **A** and **B**.
- There is one input, **X**.
- There are no explicit outputs.
 - In this case, the outputs are assumed to be the flip-flop values **A** and **B** themselves.
 - This is an example of a **Moore machine**, where the outputs depend on only the present state.



Analyzing the example circuit

- The basic state table is below.
- Again, you can see that the present states are being used to generate the next states.
- For this example, remember that the present state also serves as the output.

| Present State | | Inputs | Next State | |
|---------------|---|--------|------------|---|
| A | B | X | A | B |
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

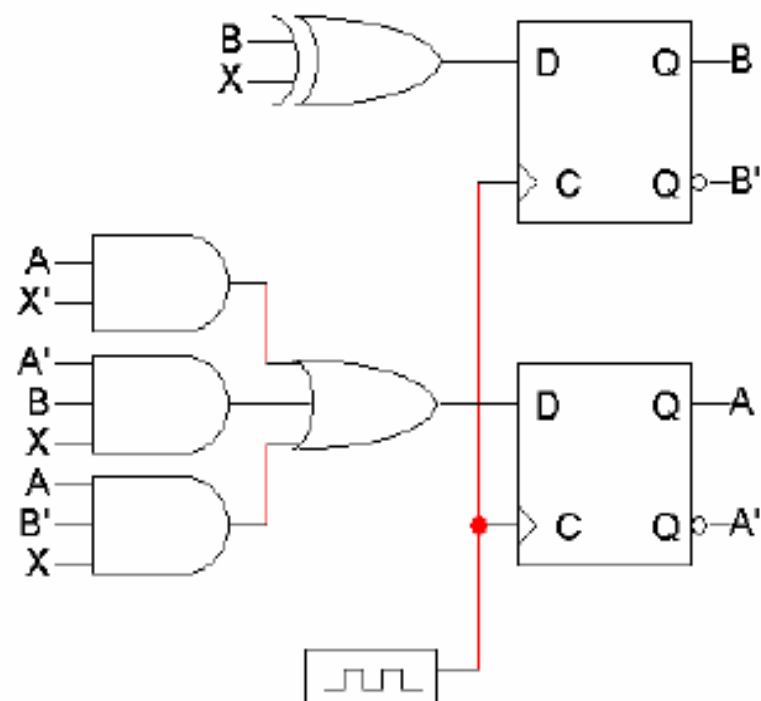


Step 1: Flip-flop input equations

- There are two input equations, one for each flip-flop.

$$D_A = AX' + A'BX + AB'X$$

$$D_B = B \oplus X$$

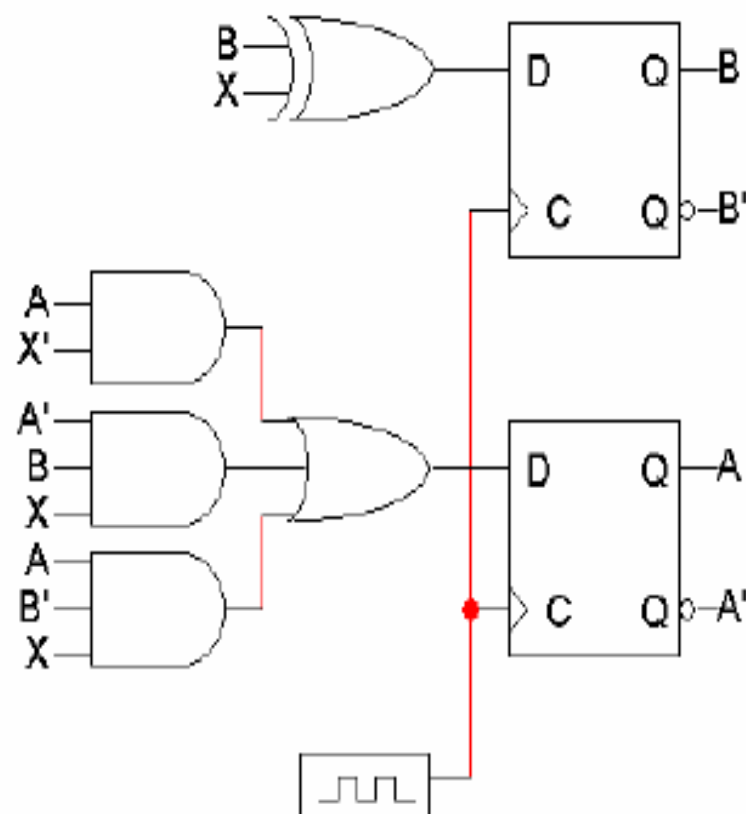- "D_A" indicates a D-type flip-flop, whose output is A.



Step 2: Flip-flop input values

- Now that we have the equations for D_A and D_B , we can fill in actual values for each combination of present state and inputs.

$$D_A = AX' + A'BX + AB'X$$

$$D_B = B \oplus X$$

| Present State | | Inputs | Flip-flop Inputs | |
|---------------|---|--------|------------------|-------|
| A | B | X | D_A | D_B |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

Step 3: Find the next states

- Finally, use the D flip-flop characteristic equation to find the next state of each flip-flop, based on its present state and its inputs.
- D flip-flops are simple because the next state is the same as the D input, *regardless* of the present state.

$$Q(t+1) = D$$


- People often don't even bother writing the "Flip-flop Inputs" columns.

| Present State | | Inputs | Flip-flop Inputs | | Next State | |
|---------------|---|--------|------------------|----------------|------------|---|
| A | B | X | D _A | D _B | A | B |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

So what does this circuit do?

- When $X = 0$, the next state is the same as the present state.
- When $X = 1$, the next state is "one more" than the present state.
- This is a basic two-bit **counter** with an enable input, X . It's also called a modulo-4 counter, since it counts from 0 to 3 repeatedly.

| Present State | | Inputs X | Next State | |
|---------------|---|---------------|------------|---|
| A | B | | A | B |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

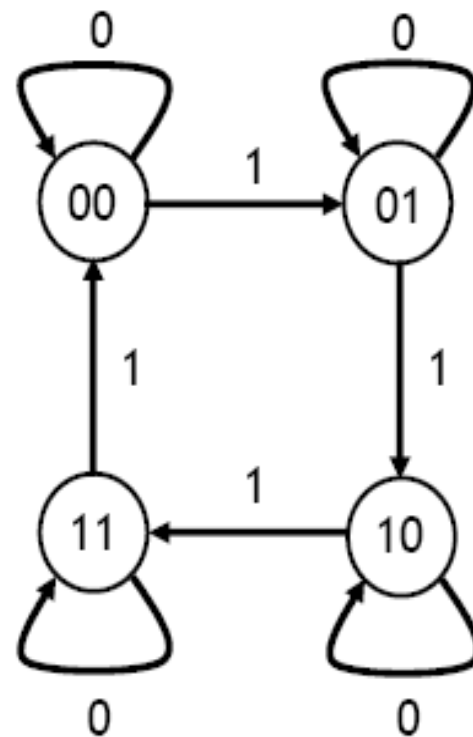

Summary

- To analyze sequential circuits, you have to understand how the flip-flops change on each clock cycle, according to their current values and inputs.
- A **state table** show all the possible ways that the outputs and state of a sequential circuit can change, based on the its inputs and present state.
- **State diagrams** are an alternative way of showing the same information.
- Next time we'll look at designing sequential circuits. This is the opposite process—you make a state table and/or diagram first, and then turn that into a sequential circuit.