

Function with Don't care inputs

- Don't cares included while computing Prime implicants
- In the Selection of Essential Prime implicants don't cares not used.

Simplify Using QM Method

$$F(A,B,C,D) = \Sigma(6,7,14)$$

$$d(A,B,C,D) = \Sigma(0,8,15)$$

EX-OR Function

$$x \oplus y = xy' + x'y$$

EX-NOR Function

$$(x \oplus y)' = xy + x'y'$$

Interesting XOR properties

- There are several fascinating properties of XOR that you can prove using Boolean algebra, starting from the definition $x \oplus y = x'y + xy'$

$$x \oplus 0 = x \quad x \oplus 1 = x'$$

$$x \oplus x = 0 \quad x \oplus x' = 1$$

$$x \oplus (y \oplus z) = (x \oplus y) \oplus z \quad \text{Associative}$$

$$x \oplus y = y \oplus x \quad \text{Commutative}$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

3-input EX-OR

$$\begin{aligned}
 Y &= A \oplus B \oplus C \\
 &= A'B'C + A'BC' \\
 &\quad AB'C' + ABC \\
 &= \Sigma (1,2,4,7)
 \end{aligned}$$

- ODD Function

	1		1
1		1	


Odd Function

$$F = A \oplus B \oplus C$$


1		1	
	1		1

Even Function

$$F = (A \oplus B \oplus C)'$$

 

(a) 3-input odd function

 

(b) 3-input even function

Fig. 3-34 Logic Diagram of Odd and Even Functions

	1		1
1		1	
	1		1
1		1	

$$F = A \oplus B \oplus C \oplus D$$

- ODD FUNCTION

1		1	
	1		1
1		1	
	1		1

$$F = (A \oplus B \oplus C \oplus D)'$$

- EVEN FUNCTION

Parity Generation and Checking:

Useful in error detection and correction

Parity bit- extra bit included with
binary message


Parity Generator

Parity checker

- A parity generator/checker can detect a 1-bit error in a message.


To generate an even parity bit

$$P = X \oplus Y \oplus Z$$

 

To check a even parity bit

$$C = X \oplus Y \oplus Z \oplus P$$

 

Message			Even	
X	Y	Z	Parity Bit, P	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0

If no errors detected, $C = 0$

COMBINATIONAL LOGIC

 


Fig. 4-1 Block Diagram of Combinational Circuit

BCD-to-Excess-3 Code Converter

- Design a circuit that converts a binary-coded-decimal (BCD) codeword to its corresponding excess-3 codeword.
- Excess-3 code: Given a decimal digit n , its corresponding excess-3 codeword $(n+3)_2$
Example:
 $n=5 \rightarrow n+3=8 \rightarrow 1000_{\text{excess-3}}$
 $n=0 \rightarrow n+3=3 \rightarrow 0011_{\text{excess-3}}$
- We need 4 input variables (A, B, C, D) and 4 output functions $W(A, B, C, D)$, $X(A, B, C, D)$, $Y(A, B, C, D)$, and $Z(A, B, C, D)$.





BCD-to-Excess-3 Converter (cont.)

- The truth table relating the input and output variables is shown below.
- Note that the outputs for inputs 1010 through 1111 are *don't cares* (not shown here).


Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

Maps for BCD-to-Excess-3 Code Converter

    The K-maps for are constructed using the don't care terms




BCD-to-Excess-3 Converter (cont.)

 

Binary addition by hand

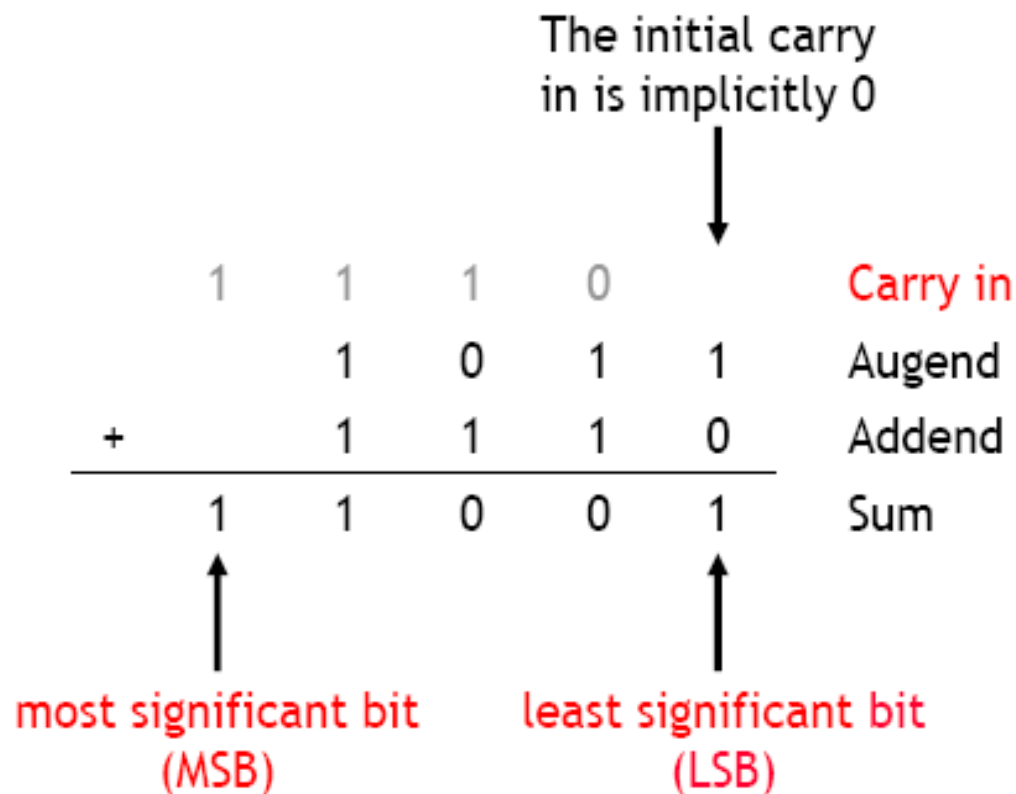- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example, $1 + 1 = 10$ and you have to carry!





HALF ADDER

Adding two bits

- We'll make a hardware adder based on our human addition algorithm.
- We start with a **half adder**, which adds two bits X and Y and produces a two-bit result: a **sum** S (the right bit) and a **carry out** C (the left bit).
- Here are truth tables, equations, circuit and block symbol.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
  
$$\begin{aligned}C &= XY \\S &= X'Y + XY' \\&= X \oplus Y\end{aligned}$$



FULL ADDER

Adding three bits

- But what we really need to do is add *three* bits: the augend and addend bits, *and* the carry in from the right.
- A **full adder** circuit takes three inputs X , Y and C_{in} , and produces a two-bit output consisting of a sum S and a carry out C_{out} .

$$\begin{array}{r} 1 \quad 1 \quad 1 \quad 0 \\ \quad 1 \quad 0 \quad 1 \quad 1 \\ + \quad 1 \quad 1 \quad 1 \quad 0 \\ \hline 1 \quad 1 \quad 0 \quad 0 \quad 1 \end{array}$$

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full adder equations

- Using Boolean algebra, we can simplify S and C_{out} as shown here.

X	Y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$\begin{aligned}S &= \Sigma m(1,2,4,7) \\&= X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in} \\&= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in}) \\&= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' \\&= X \oplus Y \oplus C_{in}\end{aligned}$$

$$\begin{aligned}C_{out} &= \Sigma m(3,5,6,7) \\&= X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} \\&= (X'Y + XY')C_{in} + XY(C_{in}' + C_{in}) \\&= (X \oplus Y)C_{in} + XY\end{aligned}$$


Full adder circuit

- We write the equations this way to highlight the hierarchical nature of adder circuits—you can build a full adder by combining two half adders!

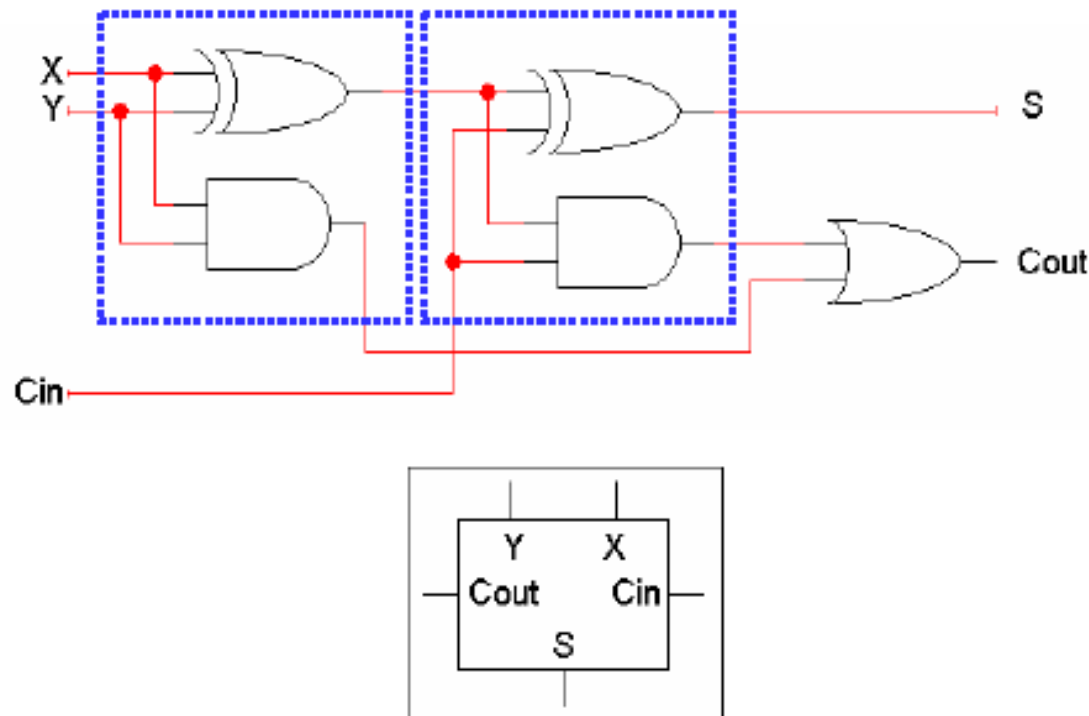
$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = (X \oplus Y) C_{in} + XY$$



A four-bit adder

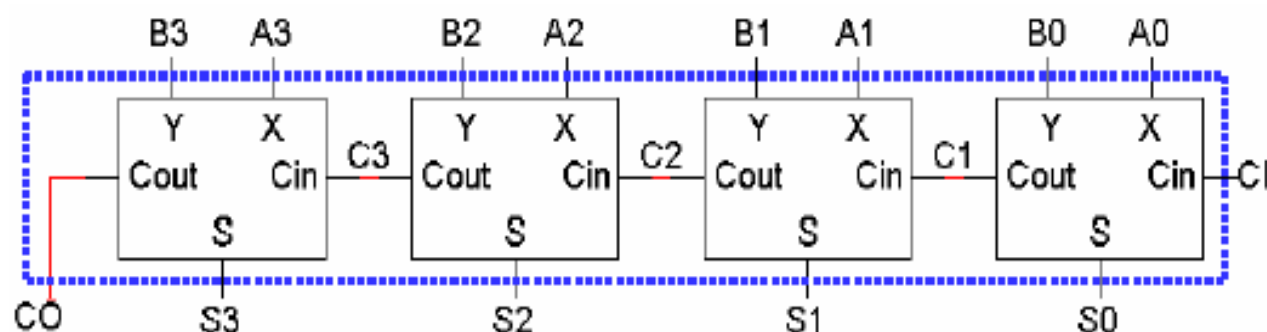


 - Similarly, we can cascade four full adders to build a four-bit adder.
 - The inputs are two four-bit numbers ($A_3A_2A_1A_0$ and $B_3B_2B_1B_0$) and a carry in CI .
 - The two outputs are a four-bit sum $S_3S_2S_1S_0$ and the carry out CO .
- If you designed this adder without taking advantage of the hierarchical structure, you'd end up with a 512-row truth table with five outputs!



An example of 4-bit addition

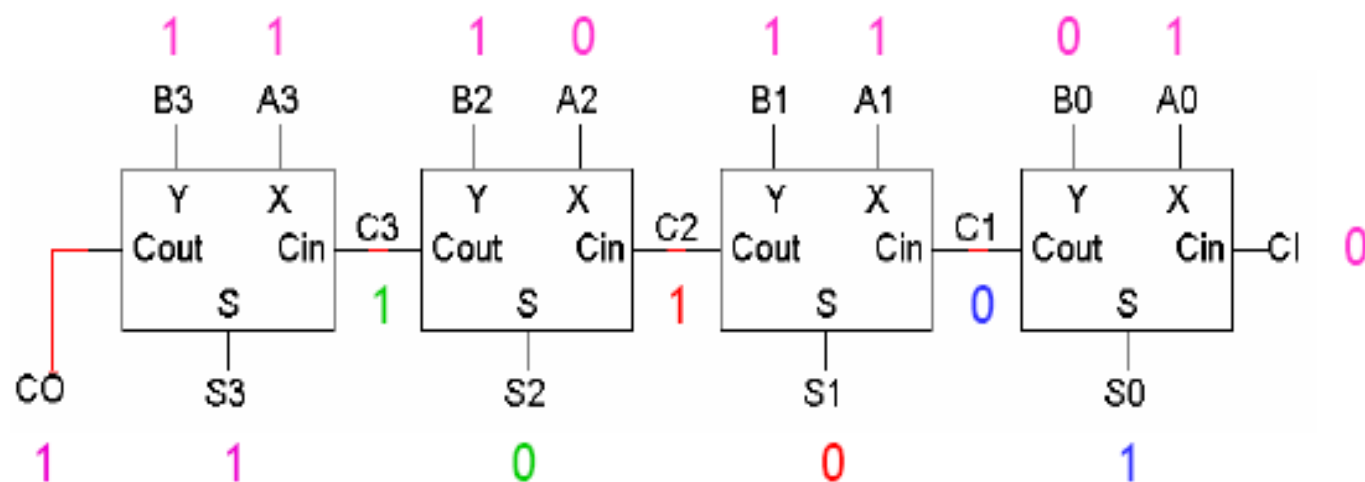- Let's put our initial example into this circuit, with $A=1011$ and $B=1110$.




1. Fill in all the inputs, including $C0=0$
2. The circuit produces $C1$ and $S0$ ($1 + 0 + 0 = 01$)
3. Use $C1$ to find $C2$ and $S1$ ($1 + 1 + 0 = 10$)
4. Use $C2$ to compute $C3$ and $S2$ ($0 + 1 + 1 = 10$)
5. Use $C3$ to compute $C4$ and $S3$ ($1 + 1 + 1 = 11$)

Binary Adder/Subtractors

- The subtraction $A-B$ can be performed by taking the 2's complement of B and adding to A .
- The 2's complement of B can be obtained by complementing B and adding one to the result.

$$\begin{aligned}A-B &= A + 2C(B) \\ &= A + 1C(B) + 1 \\ &= A + B' + 1\end{aligned}$$

4-bit Binary Adder/Subtractor

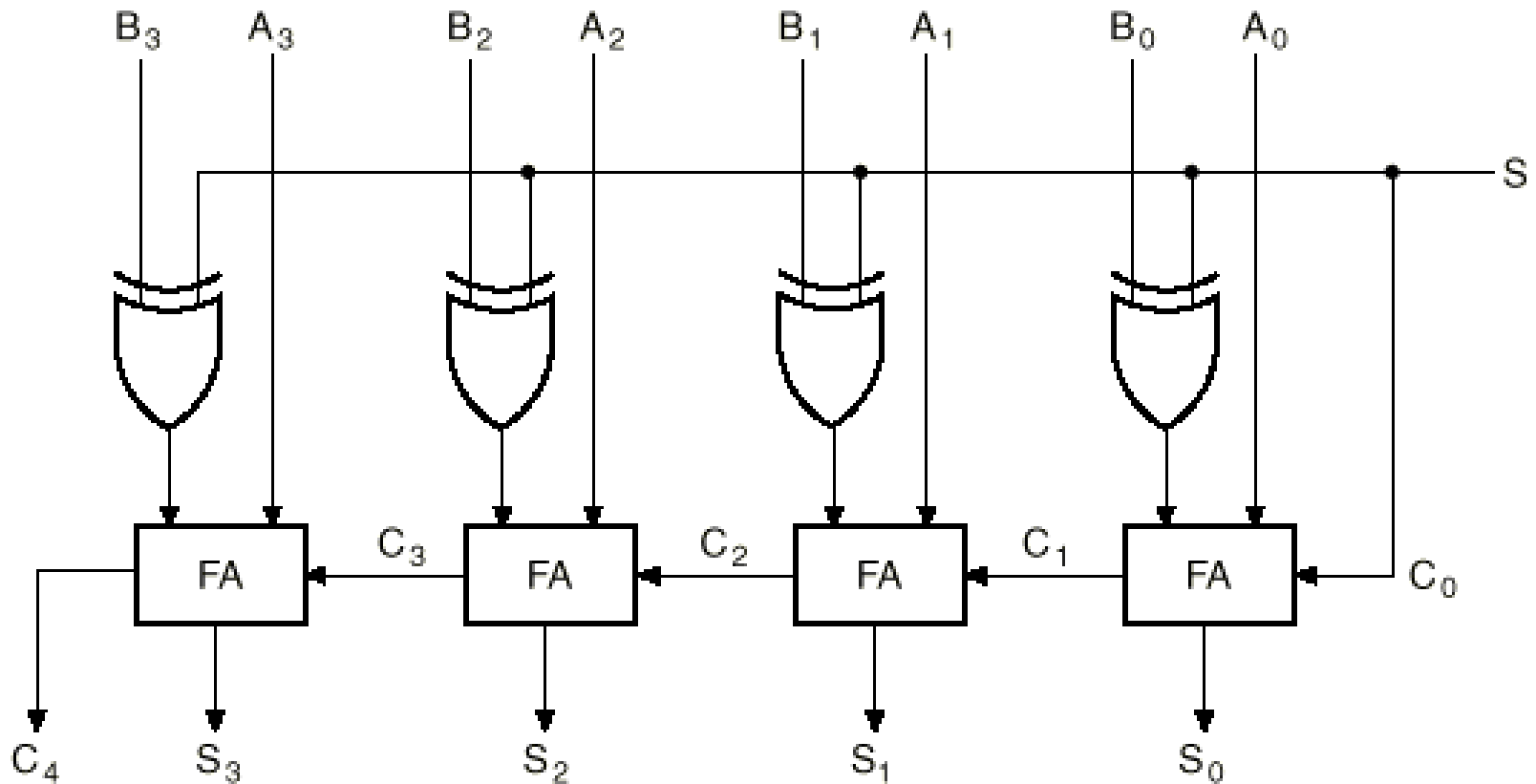


-XOR gates act as programmable inverters

4-bit Binary Adder/Subtractor (cont.)


- When $S=0$, the circuit performs $A + B$. The carry in is 0, and the XOR gates simply pass B untouched.
- When $S=1$, the carry into the least significant bit (LSB) is 1, and B is complemented (1's complement) prior to the addition; hence, the circuit adds to A the 1's complement of B plus 1 (from the carry into the LSB).

4-bit Binary Adder/Subtractor (cont.)

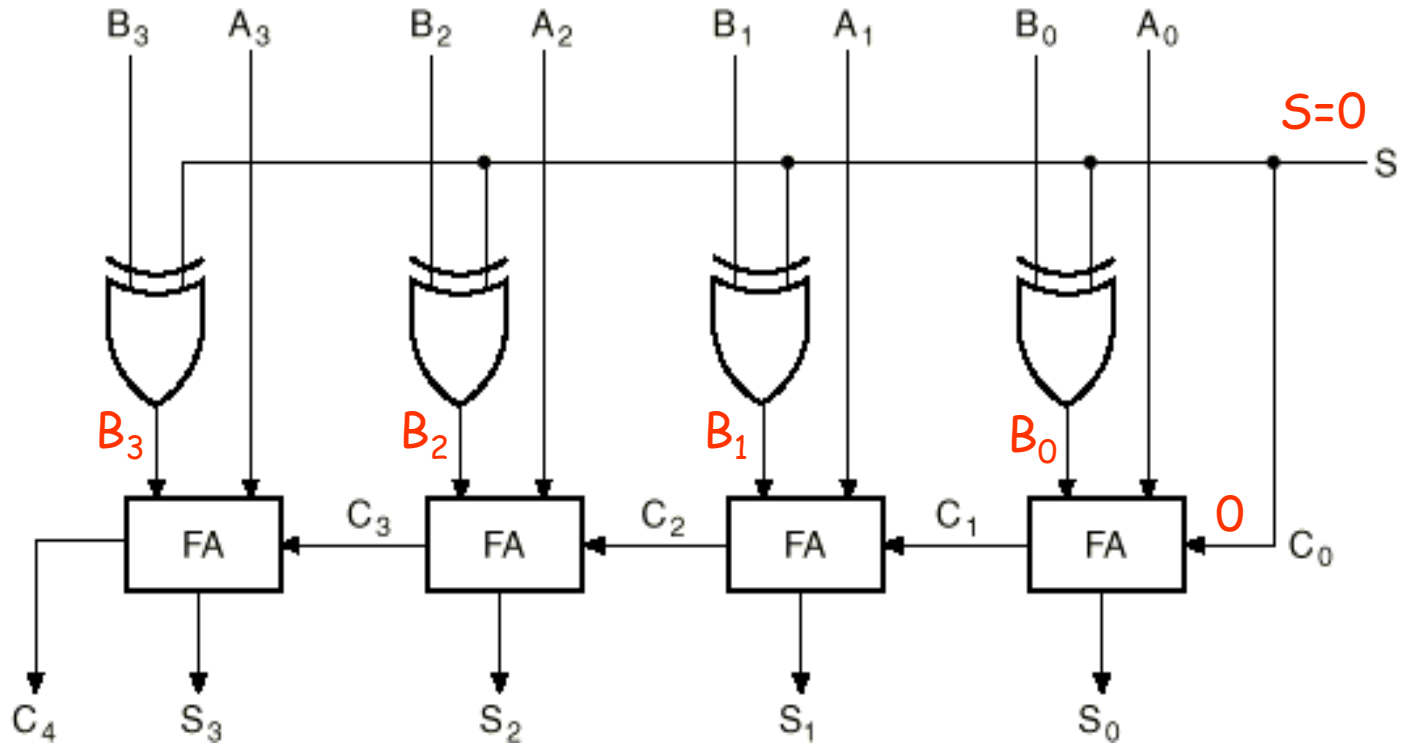

$S=0$ selects addition

4-bit Binary Adder/Subtractor (cont.)

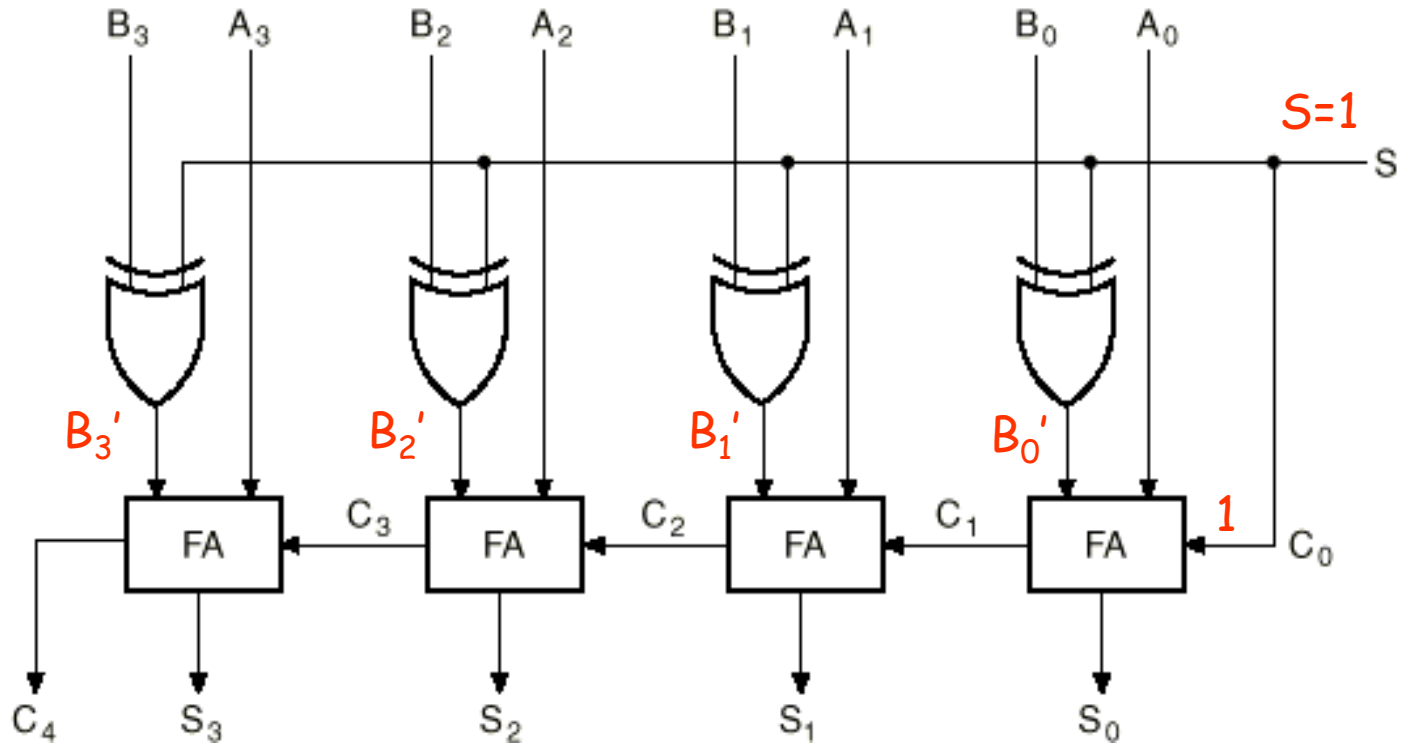

S=1 selects subtraction

Decimal Adders

- Is Binary sum less than or equal to 1001**
- For binary sum more than 1001 add 0110**
- Circuit needs modification**


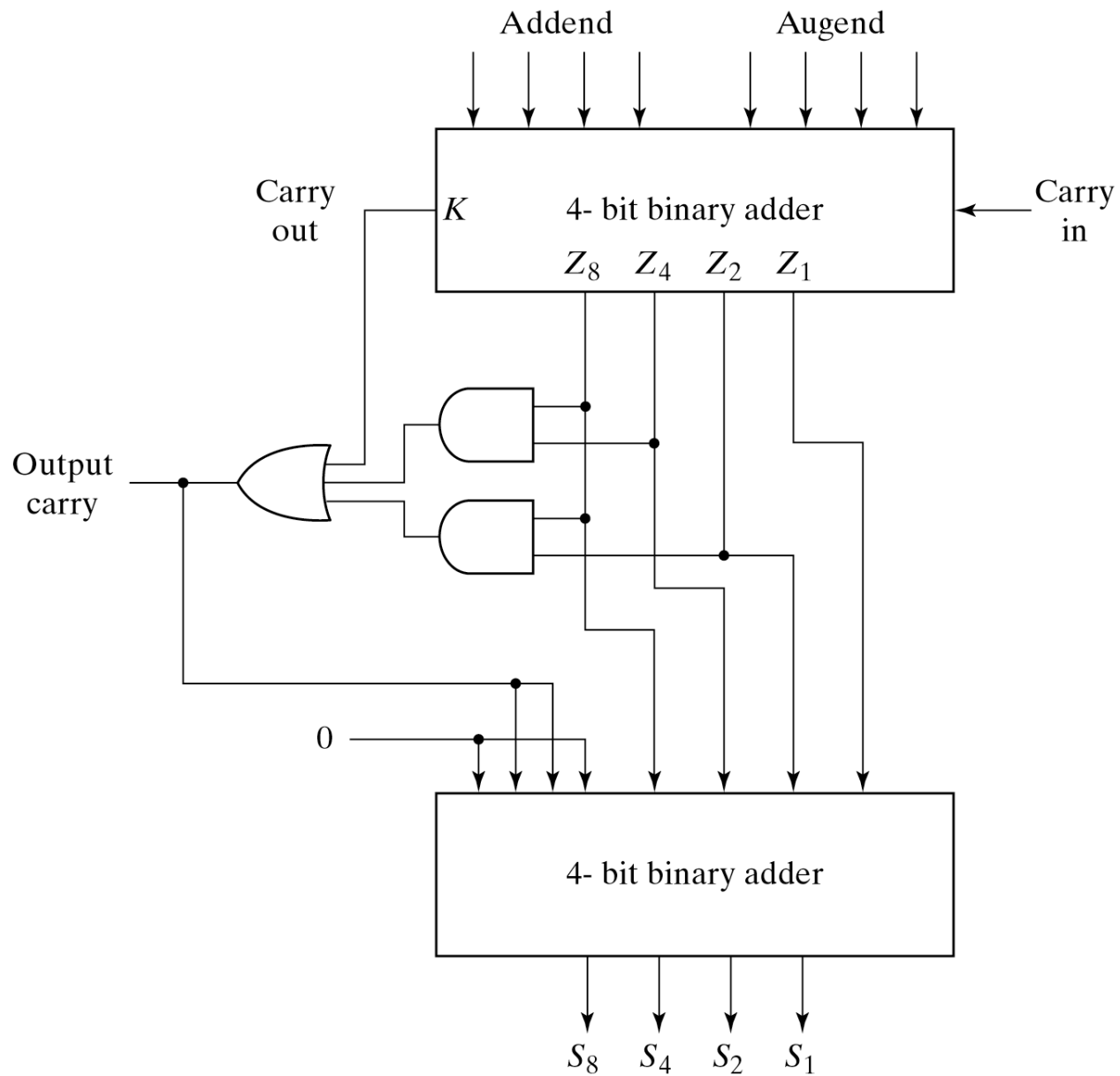


Fig. 4-14 Block Diagram of a BCD Adder

Hierarchical adder design

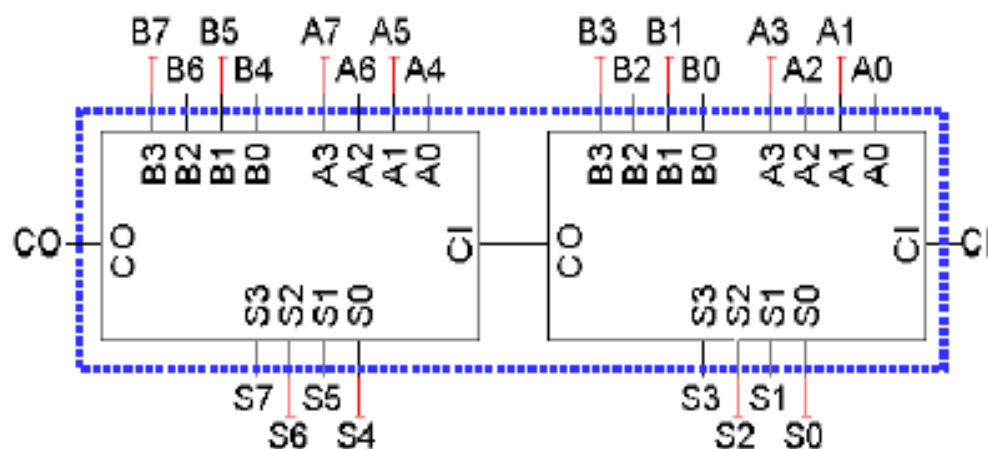
- When you add two 4-bit numbers the carry in is always 0, so why does the four-bit adder have a CI input?
- We can use CI to combine four-bit adders together to make even larger adders, just like we combined half adders and full adders earlier.
- Here is one way to build an eight-bit adder, for example.



- CI is also useful for subtraction,

Ripple carry delays

- The diagram below shows our four-bit adder completely drawn out.
- This is called a **ripple carry adder**, because the inputs A0, B0 and C1 “ripple” leftwards until CO and S3 are produced.
- Ripple carry adders are slow!
 - There is a very long path from A0, B0 and C1 to CO and S3.
 - For an n -bit ripple carry adder, the longest path has $2n+1$ gates.
 - The longest path in a 64-bit adder would include 129 gates!

 

A faster way to compute carry outs

- Instead of waiting for the carry out from each previous stage, we can minimize the delay by computing it directly with a two-level circuit.
- First we'll define two functions.
 - The "generate" function G_i produces 1 when there *must* be a carry out from position i (i.e., when A_i and B_i are both 1).


$$G_i = A_i B_i$$

- The "propagate" function P_i is true when an incoming carry is propagated (i.e, when $A_i=1$ or $B_i=1$, but not both).

$$P_i = A_i \oplus B_i$$

- Then we can rewrite the carry out function.

$$C_{i+1} = G_i + P_i C_i$$

 

A_i	B_i	C_i	C_{i+1}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Let's look at the carry out equations for specific bits, using the general equation from the previous page $C_{i+1} = G_i + P_i C_i$.

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

- These expressions are all sums of products, so we can use them to make a circuit with only a two-level delay.

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator


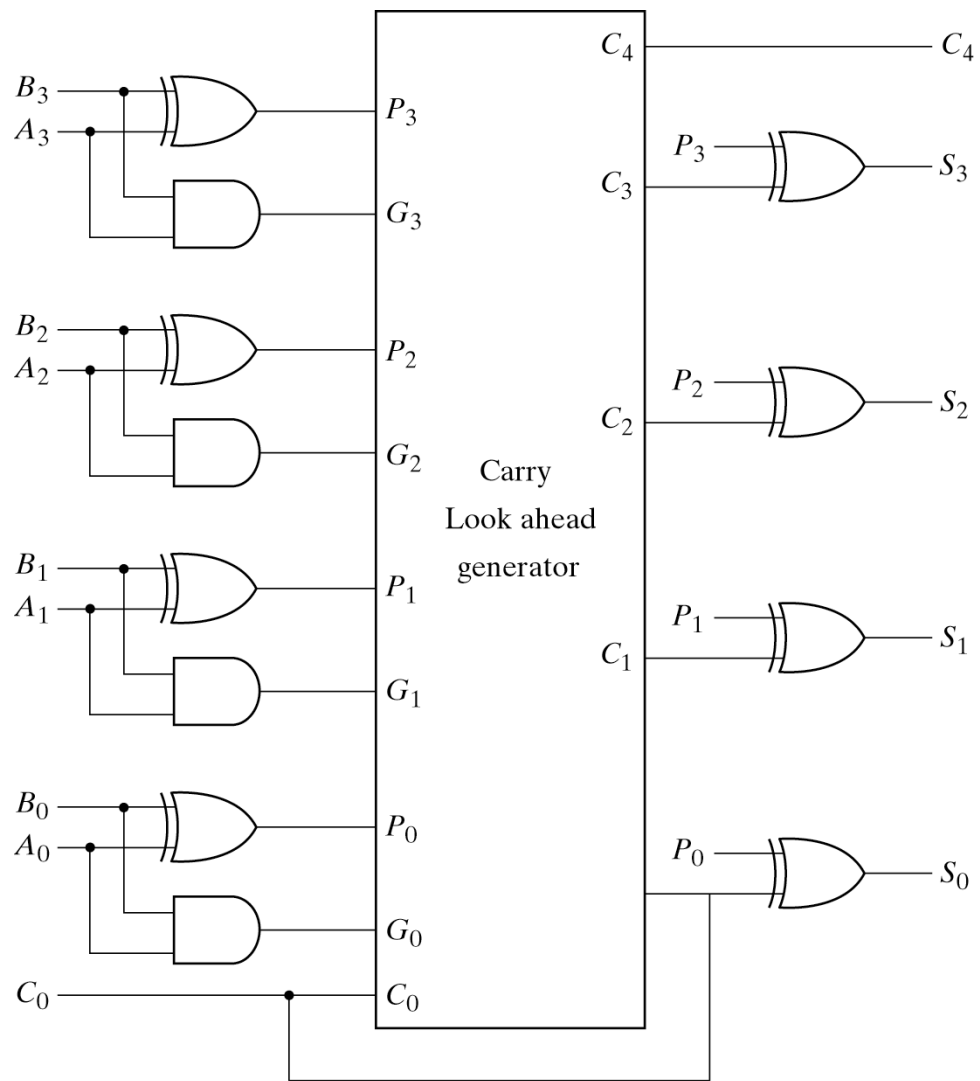


Fig. 4-12 4-Bit Adder with Carry Lookahead

A faster four-bit adder

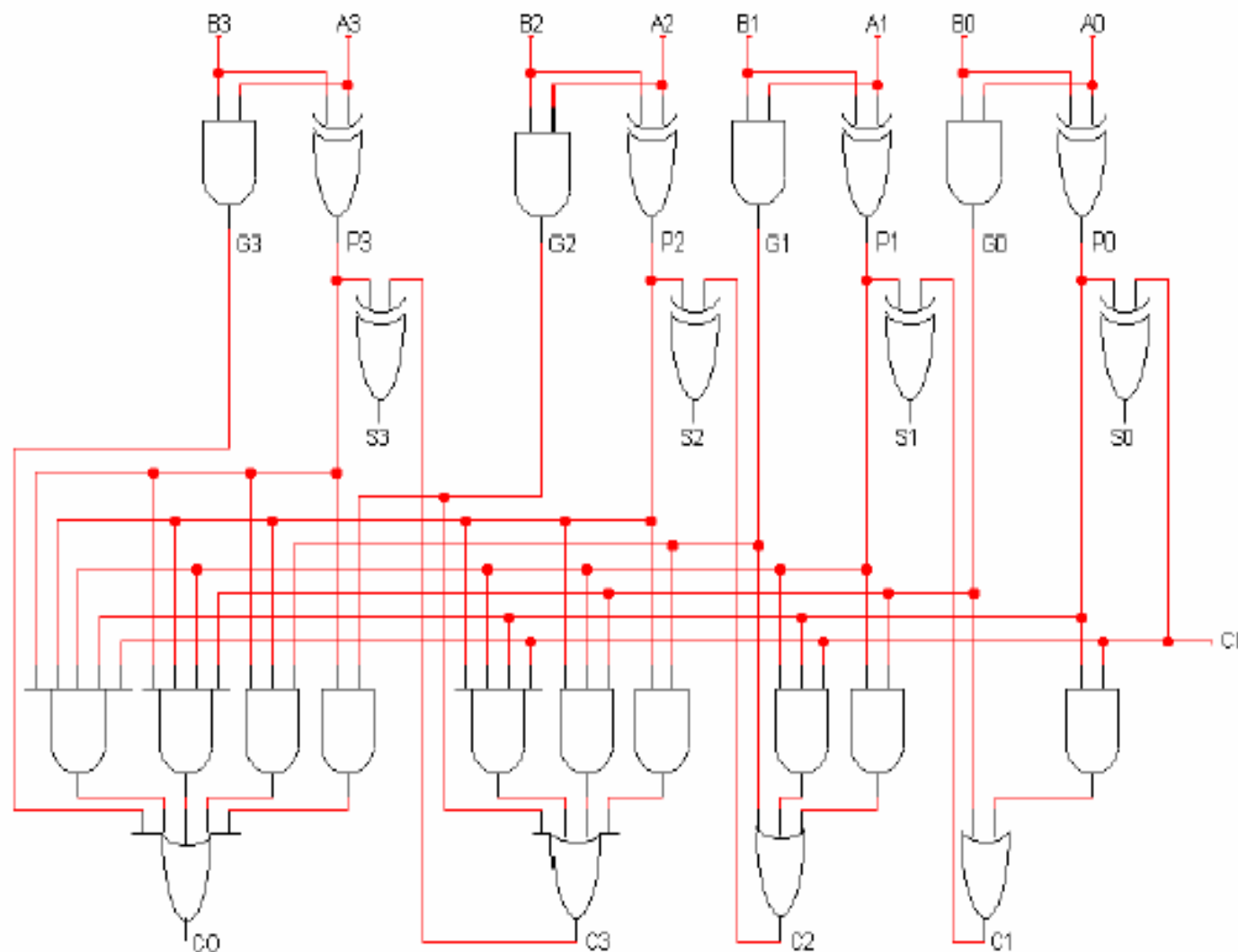

				1	1	0	1
			×	0	1	1	0
				0	0	0	0
			1	1	0	1	
		1	1	0	1		
+	0	0	0	0			
	1	0	0	1	1	1	0


Binary multiplication

				1	1	0	1	Multiplicand
				0	1	1	0	Multiplier
				0	0	0	0	} Partial products
			1	1	0	1		
		1	1	0	1			
+	0	0	0	0				
	1	0	0	1	1	1	0	Product


- Since we always multiply by either 0 or 1, the **partial products** are always either **0000** or the multiplicand (**1101** in this example).
- There are four partial products which are added to form the result.
 - We can add them in pairs, using three adders.
 - The product can have up to 8 bits, but we can use four-bit adders if we stagger them leftwards, like the partial products themselves.

A 2x2 binary multiplier


- Here is a circuit that multiplies the two-bit numbers A_1A_0 and B_1B_0 , resulting in the four-bit product P_3P_0 .
- For a 2x2 multiplier we can just use two half adders to sum the partial products. In general, though, we'll need full adders.
- The diagram on the next page shows how this can be extended to a four-bit multiplier, taking inputs A_3-A_0 and B_3-B_0 and outputting the product P_7-P_0 .

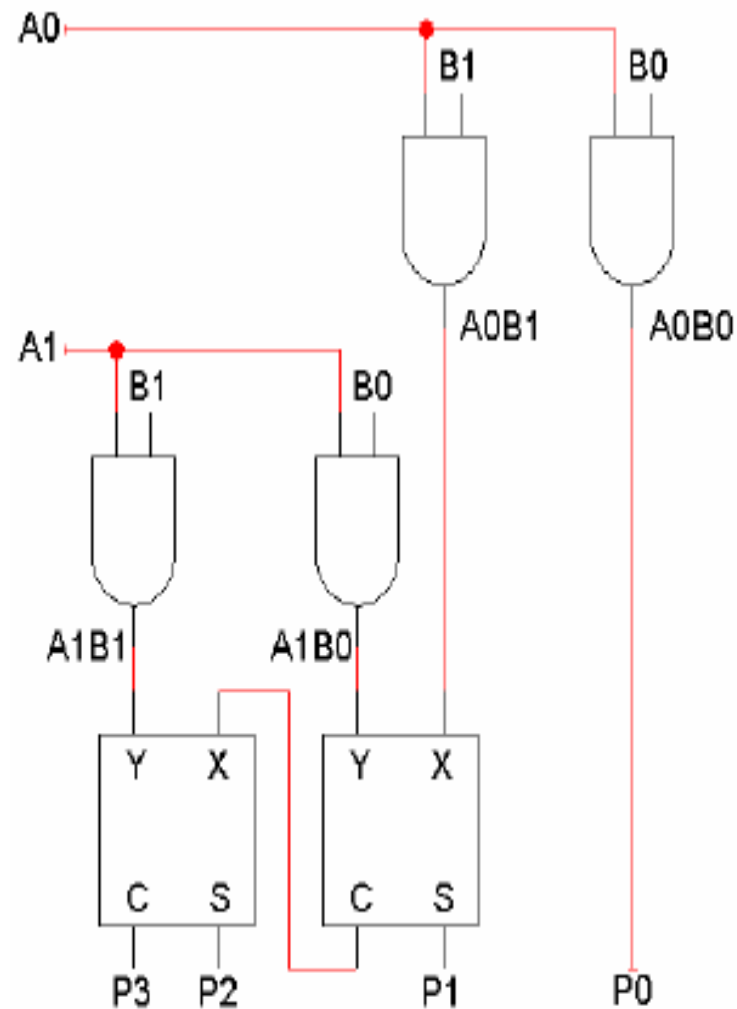

A 4x4 binary multiplier

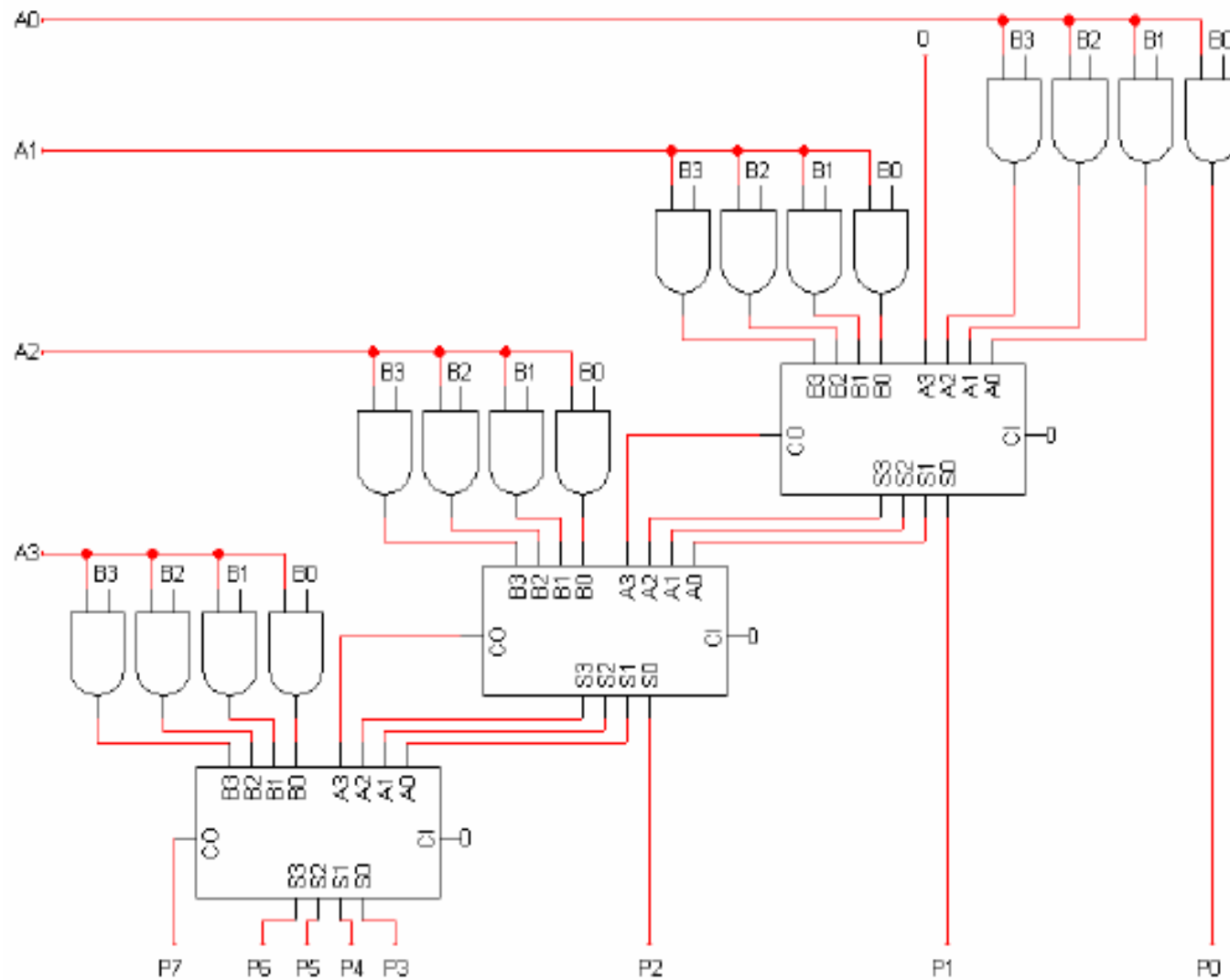

Complexity of multiplication circuits

 

- In general, when multiplying an m -bit number by an n -bit number:
 - There will be n partial products, one for each bit of the multiplier.
 - This requires $n-1$ adders, each of which can add m bits.
- The circuit for 32-bit or 64-bit multiplication would be huge!