

Algorithmic State Machines (ASM)

Binary information in Digital Systems:

Data

Control

➔ Data processing tasks:

Addition, decoding, counting etc

➔ Control information provides command signals monitoring data processing tasks.

Various modules are interconnected to form digital system

Logic Design consists of:

➔ Design of Data processing circuits

➔ Design of control circuits

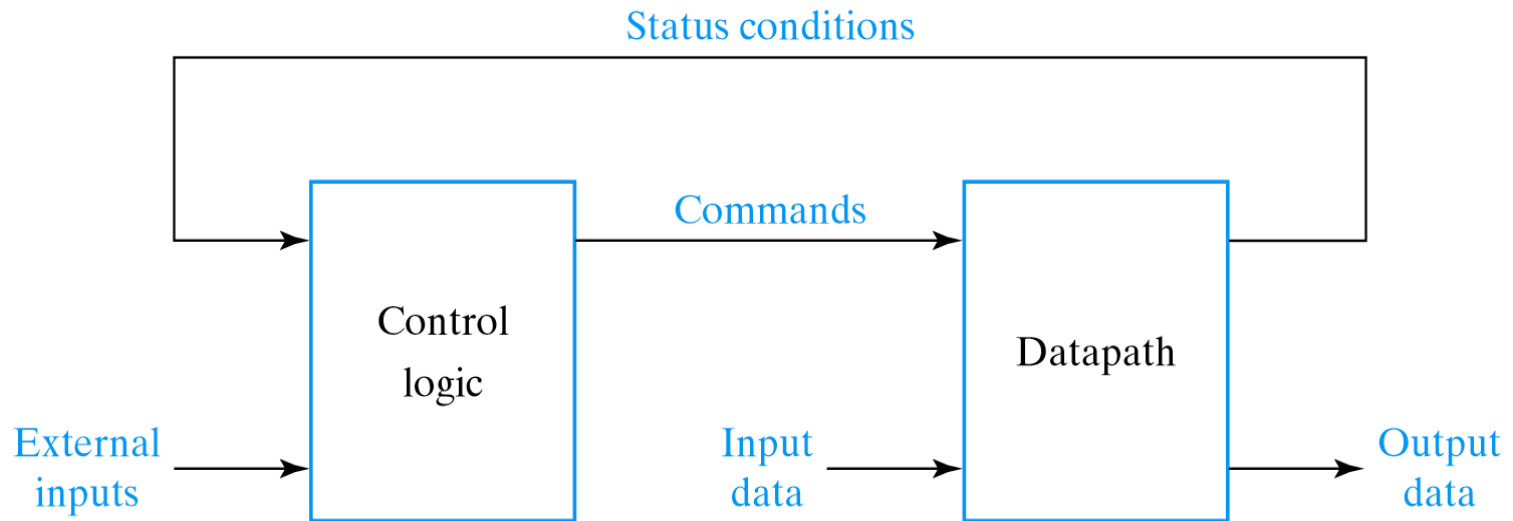


Fig. 8-2 Control and Datapath Interaction

**➔ Control sequence and data processing
Tasks are specified by means of Hardware
Algorithm.**

**➔ A Special Flowchart developed to design
Digital hardware algorithms is called
Algorithmic State Machines (ASM)**

➔ A conventional flowchart describes sequence of Procedural steps without concern for their time relationship

➔ An ASM chart describes the sequence of events *as well as* the timing relationship between states of sequential controller

ASM CHART

Composed of three basic elements

➔ The State box

➔ The decision box


➔ The conditional box

A state is indicated by the **state box within which
Register operations are written**


Or

**The output signal names that the control
generates while being in the state are written.**

 **➔ The state is given a symbolic name and a binary
code is assigned to state**



(a) General description

 

(b) Specific example

Fig. 8-3 State Box

‘START’ may indicate an output signal that starts an operation

➔ Decision box indicates the effect of an input on the control subsystem

➔ Input condition to be tested is written inside the box

➔ One exit path is taken if the condition is true and another if false

 


Fig. 8-4 Decision Box

➔ The conditional box is unique to ASM chart

➔ Input path to conditional box comes from one of exit paths of a decision box

➔ The register operations or outputs listed inside a conditional box are generated during a given State provided the input condition is satisfied.

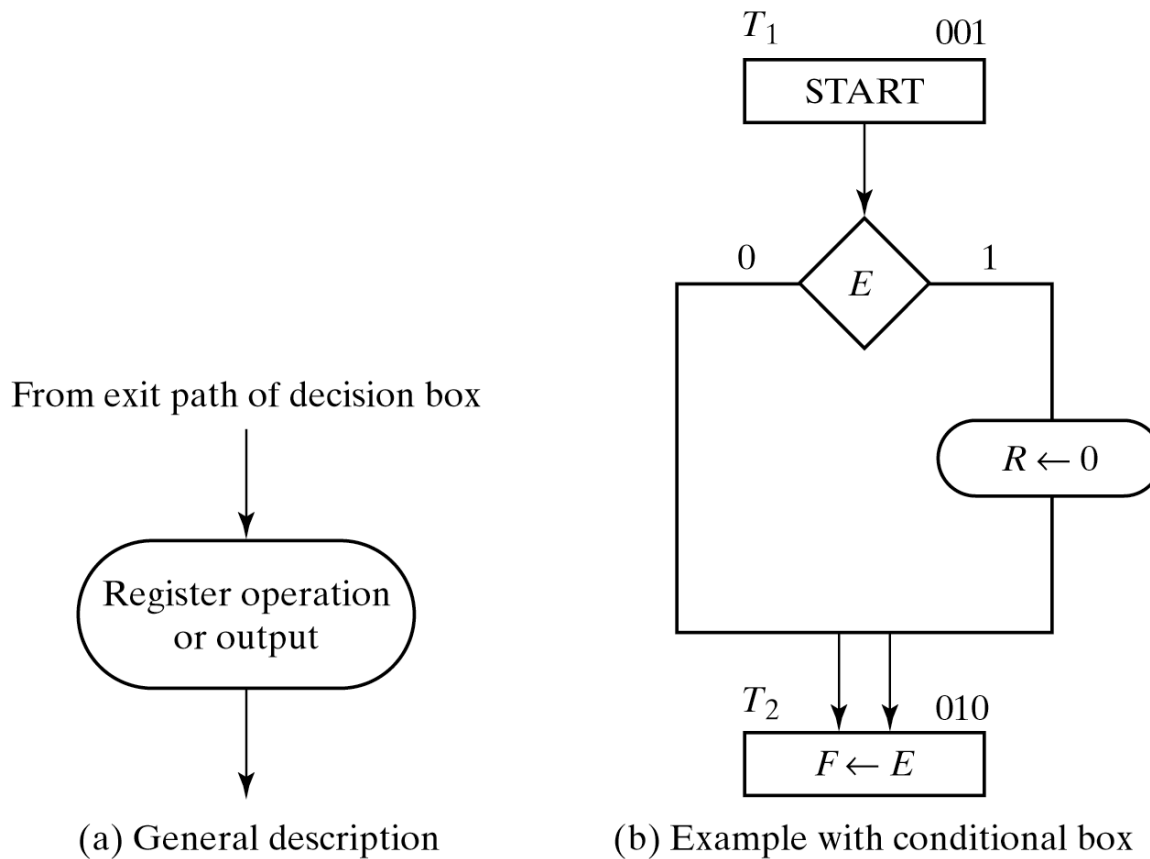


Fig. 8-5 Conditional Box

ASM Block

→ A structure consisting of one state box and all the decision and conditional boxes connected to its exit path.

→ An ASM block has one entrance and any number of exit paths represented by the structure of the decision boxes

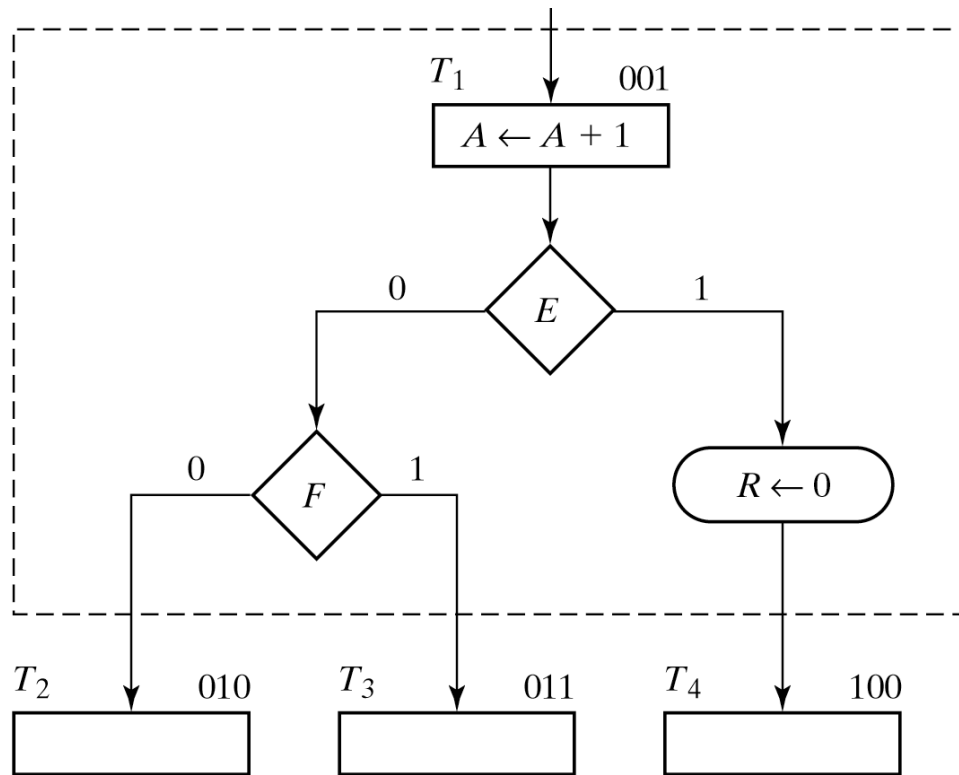


Fig. 8-6 ASM Block

- ➔ Each ASM block in the ASM chart describes the state of the system during one clock pulse interval
- ➔ The operations within the state and conditional boxes are executed with a common clock pulse while the system is in state T1.
- ➔ The same clock pulse also transfers the system controller to one of the next states.
- ➔ ASM chart is very similar to state diagram.

 


Fig. 8-7 State Diagram Equivalent to the ASM Chart of Fig. 8

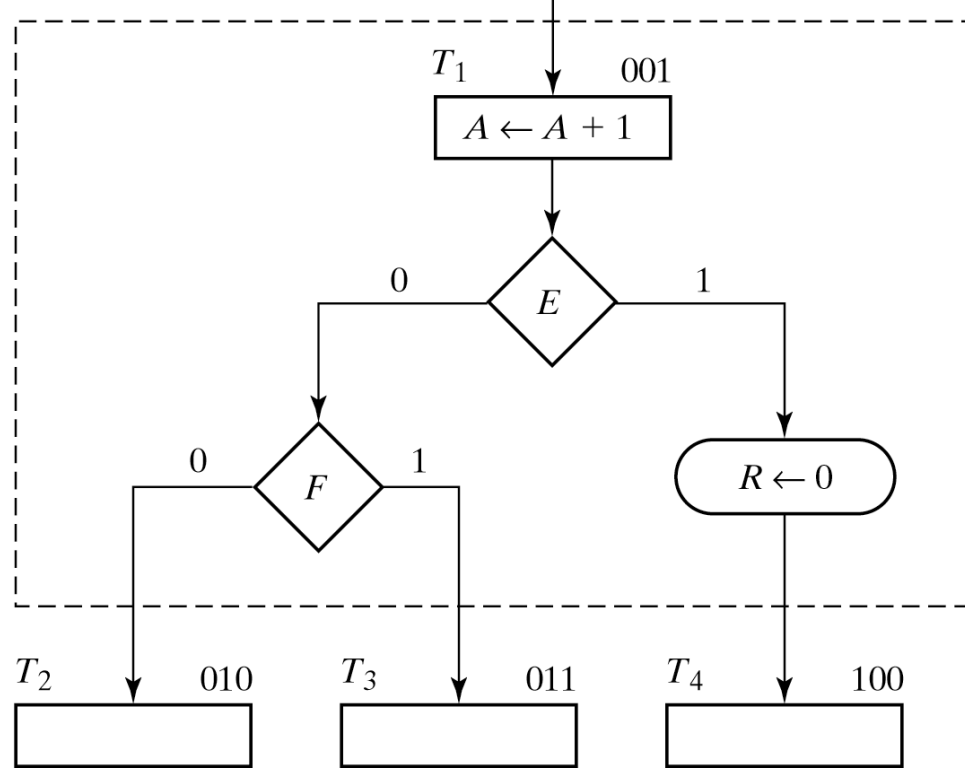


Fig. 8-6 ASM Block

- Major difference between a conventional flowchart and an ASM chart is interpreting the timing relations.
- In conventional flowchart the listed operations follow one after the other in time sequence.
- ASM chart consider the entire ASM block as one unit.
- All operations within a block must occur in synchronism during clock edge.

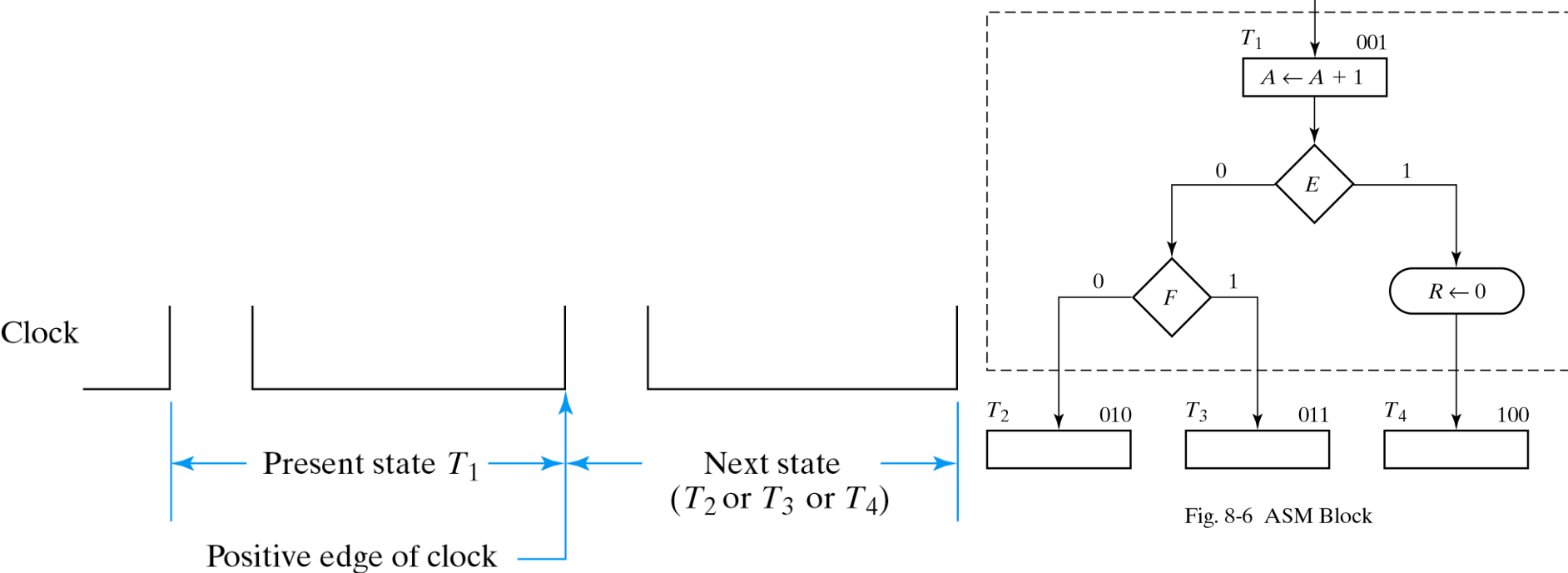


Fig. 8-8 Transition Between States

During transition

A is incremented, If $E = 1$, R is cleared

Depending on values of EF control transferred to T2 or T3 or T4

Design Example:

Design a Digital system with two FFs E and F, one 4-bit binary counter A ($A_4A_3A_2A_1$). A start signal S initiates the system operation by clearing counter A and flip-flop F. Counter incremented by one starting from next clock pulse, continues to increment until operations stop.

If $A_3 = 0$, E is cleared to 0 and count continues

If $A_3 = 1$, E set to 1; then if $A_4=0$, count continues, but if $A_4 = 1$, F set to 1 on *next clock pulse* and system stops counting. If $S = 0$ system remains in initial state, but if $S = 1$ operation cycle repeats.

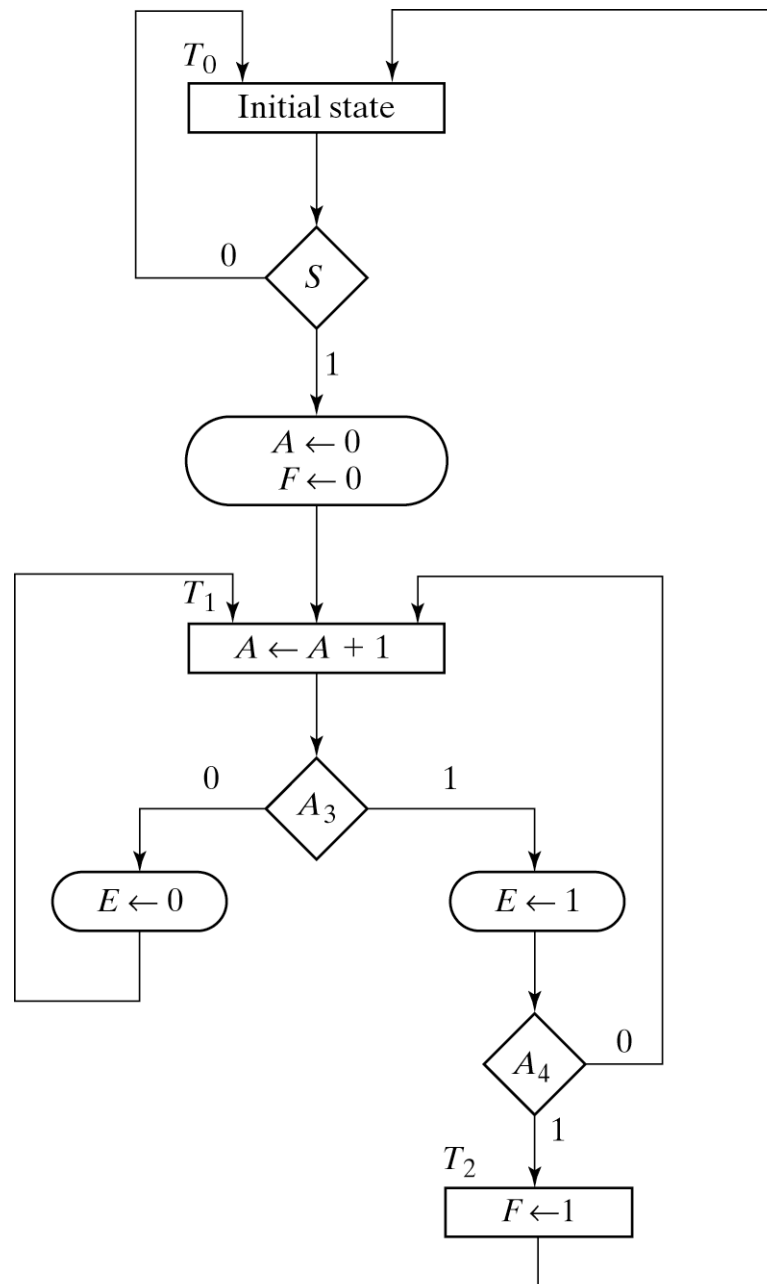


Fig. 8-9 ASM Chart for Design Example

→ When no operations the system in initial state T0 waiting for S

→ When input $S = 1$, counter A and flip-flop F cleared and Counter goes to state T1

→ Block with T1 has two decision and two conditional boxes

→ Counter incremented with every clock pulse, at the same time one of three operations occur during clock transition

**Either E cleared and control stays in T1 ($A_3 = 0$); or
E is set and control stays in T1 ($A_3A_4 = 10$); or
E is set and control goes to T2 ($A_3A_4 = 11$).**

→ When in T2 F is set and circuit goes to T0.

- Every block in the ASM chart specifies the operations performed during one common clock pulse.
- Operations specified within the state and conditional boxes in the block are performed in the **datapath section**.
- The change from one state to next is performed in the **control section**.

Counter				Flipflops		Conditions	State
A4	A3	A2	A1	E	F		
0	0	0	0	1	0	A3= 0, A4=0	T1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	A3=1, A4= 0	

Counter				Flipflops		Conditions	State
A4	A3	A2	A1	E	F		
0	1	0	0	0	0	A3=1, A4= 0	T1
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	A3=0, A4=1	

Counter				Flipflops		Conditions	State
A4	A3	A2	A1	E	F		
1	0	0	0	1	0	A3=0, A4=1	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	A3=1, A4 = 1	

Counter				Flipflops		Conditions	State
A4	A3	A2	A1	E	F		
1	1	0	0	0	0	A3=1, A4 = 1	
1	1	0	1	1	0		T2
1	1	0	1	1	1		T0

- The requirements of design of the datapath are specified inside the state and conditional boxes
- Control logic is determined by the decision boxes and required state transitions.

Data path consists of

- 4 bit binary counter**

- Two flip-flops**


- Gates**

Counter is incremented with every clock cycle when control is in state T1.

Cleared when control is in state T0 and S is equal to 1. → uses an AND gate

The other two conditional operations use two other AND gates for setting or clearing E.

F is set unconditionally during T2.

 

(a) State diagram for control

Register transfer operations:

T0: if (S=1) then $A \leftarrow 0$, $F \leftarrow 0$

T1: $A \leftarrow A + 1$

 if ($A3 = 1$) then $E \leftarrow 1$

 if ($A3 = 0$) then $E \leftarrow 0$

T2: $F \leftarrow 1$

State Table:

Present-State	Present State		Inputs			Next State		Outputs		
Symbol	G1	G0	S	A3	A4	G1	G0	T0	T1	T2
T0	0	0	0	X	X	0	0	1	0	0
T0	0	0	1	X	X	0	1	1	0	0
T1	0	1	X	0	X	0	1	0	1	0
T1	0	1	X	1	0	0	1	0	1	0
T1	0	1	X	1	1	1	1	0	1	0
T2	1	1	X	X	X	0	0	0	0	1

Design Using D FFs.

Flip-flop Inputs

$$\mathbf{DG1 = T1A3A4}$$

$$\mathbf{DG0 = T0S + T1}$$

Output Functions

$$\mathbf{T0 = G0'}$$

$$\mathbf{T1 = G1'G0}$$

$$\mathbf{T2 = G1}$$

 


Fig. 8-12 Logic Diagram of Control