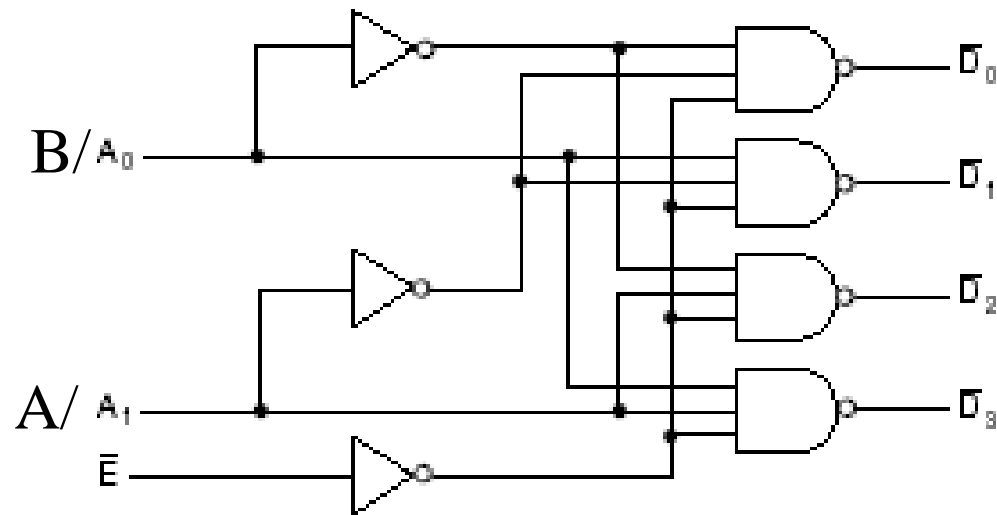

Back to HDL.....

2-to-4 Line Decoder



(a) Logic diagram

E	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$D_0 = \overline{E} \cdot \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{E} \cdot \overline{A_1} \cdot A_0$$

$$D_2 = \overline{E} \cdot A_1 \cdot \overline{A_0}$$

$$D_3 = \overline{E} \cdot A_1 \cdot A_0$$

(c) Logic Equations

Fig.3-14 A 2-to-4-Line Decoder

//Gate - level description of a 2-to-4 line decoder

module decoder_g1 (A,B,E,D);

input A, B, E;

output [0:3]D;

wire Anot, Bnot, Enot;

not

n1(Anot, A),

n2(Bnot, B),

n3(Enot, E);

nand


n4 (D[0], Anot, Bnot, Enot),

n5 (D[1], Anot, B, Enot),

n6 (D[2], A, Bnot, Enot),

n7 (D[3], A, B, Enot);

endmodule

 

(a) Logic diagram

E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$D_0 = \overline{E} \overline{A_1} \overline{A_0}$$

$$D_1 = \overline{E} \overline{A_1} A_0$$

$$D_2 = \overline{E} A_1 \overline{A_0}$$

$$D_3 = \overline{E} A_1 A_0$$

(c) Logic Equations

Fig.3-14 A 2-to-4-Line Decoder

```
module stimckt;
reg A,B,E;
wire [0:3]D;
  decoder_g1 dec (A, B, E, D);
  initial
  begin
    A = 1'b0; B = 1'b0; E = 1'b0;
    #100
    A = 1'b0; B = 1'b1; E = 1'b0;
    #100 $finish;
  end
endmodule
```

4-to-1 Multiplexer

 


Fig. 3-19 4-to-1-Line Multiplexer

4-to-1 Multiplexer

```
// 4-to-1 Line Multiplexer: Structural Verilog Description    // 1
// (See Figure 3-19 for logic diagram)                      // 2
module multiplexer_4_to_1_st_v(S, D, Y);                  // 3
    input [1:0] S;                                         // 4
    input [3:0] D;                                         // 5
    output Y;                                              // 6
```

```
    wire [1:0] not_S;
    wire [0:3] N;
```

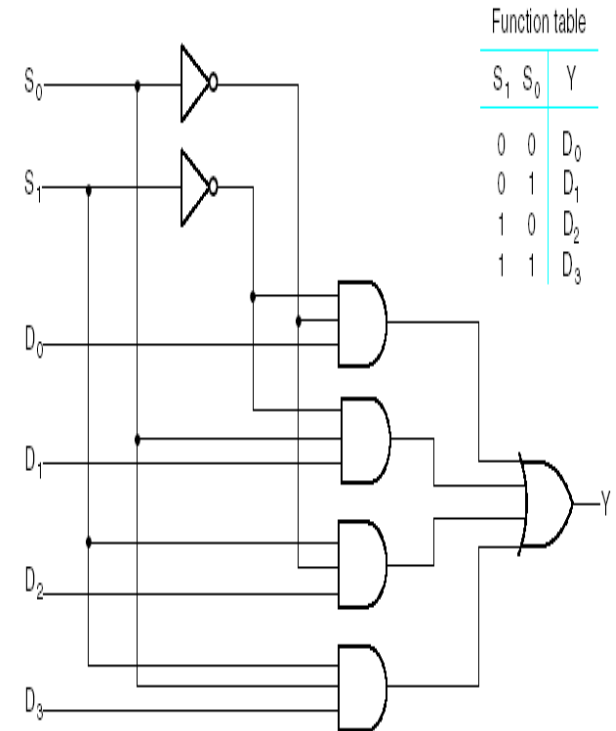


Fig. 3-19 4-to-1-Line Multiplexer

4-to-1 Multiplexer

```
// 4-to-1 Line Multiplexer: Structural Verilog Description    // 1
// (See Figure 3-19 for logic diagram)                      // 2
module multiplexer_4_to_1_st_v(S, D, Y);                  // 3
    input [1:0] S;                                         // 4
    input [3:0] D;                                         // 5
    output Y;                                              // 6

    wire [1:0] not_S;                                     // 7
    wire [0:3] N;                                         // 8
```

```
not
    gn0(not_S[0], S[0]),
    gn1(not_S[1], S[1]);
```

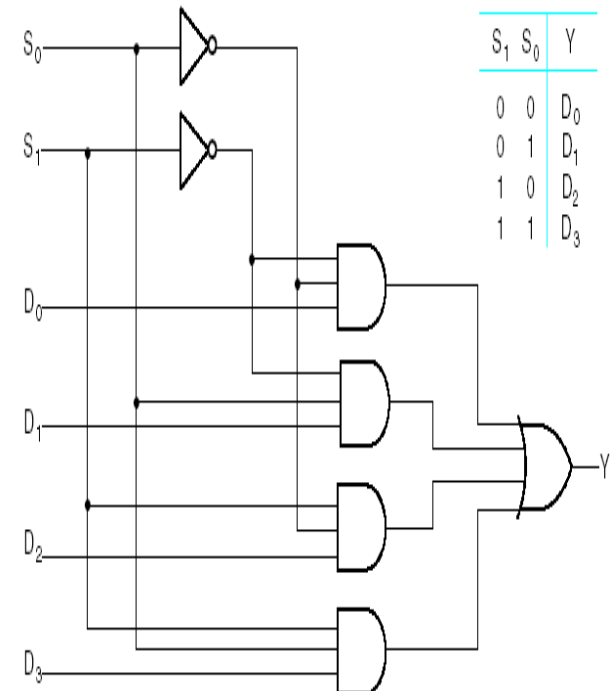


Fig. 3-19 4-to-1-Line Multiplexer

4-to-1 Multiplexer

```
// 4-to-1 Line Multiplexer: Structural Verilog Description // 1
// (See Figure 3-19 for logic diagram) // 2
module multiplexer_4_to_1_st_v(S, D, Y); // 3
    input [1:0] S; // 4
    input [3:0] D; // 5
    output Y; // 6
```

```
    wire [1:0] not_S;
    wire [0:3] N;

    not
        gn0(not_S[0], S[0]),
        gn1(not_S[1], S[1]);

    and
        g0(N[0], not_S[1], not_S[0], D[0]),
        g1(N[1], not_S[1], S[0], D[1]),
        g2(N[2], S[1], not_S[0], D[2]),
        g3(N[3], S[1], S[0], D[3]);

    or go(Y, N[0], N[1], N[2], N[3]);

endmodule
```

 


Fig. 3-19 4-to-1-Line Multiplexer

DATA FLOW MODELLING

Dataflow modelling

- Another level of abstraction is to model dataflow.
- Dataflow modeling uses a number of operators that act on operands to produce desired results.
- Verilog HDL provides about 30 operator types.
- In dataflow models, signals are continuously assigned values using the **assign** keyword.

Dataflow Modeling

- For ex: assign $Y = (A \&B) \mid (C \&D)$
- **assign** can be used with Boolean expressions.
 - Verilog uses **&** (and), **|** (or), **^** (xor) and **~** (not)
- Logic expressions and binary arithmetic are also possible.

Simple Circuit Boolean Expression

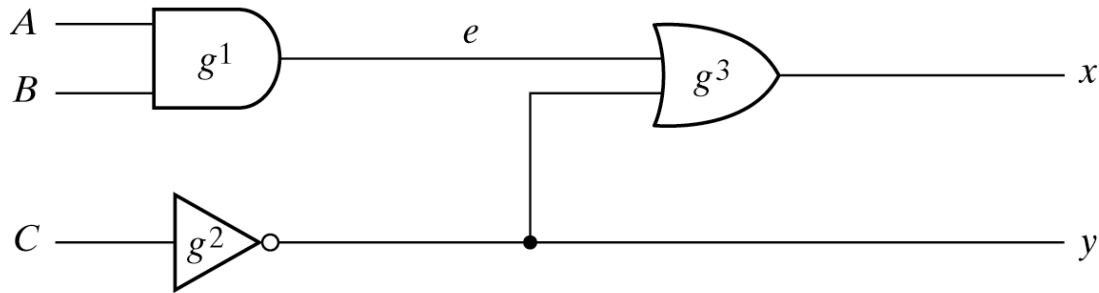


Fig. 3-37 Circuit to Demonstrate HDL

$$x = A.B + \bar{C}$$


$$y = \bar{C}$$

Boolean Expressions

//Circuit specified with Boolean equations

```
module circuit_bln (A,B,C,x,y);  
    input A,B,C;  
    output x,y;  
    assign x = (A & B) | (~C);  
    assign y = ~C ;  
endmodule
```

2-to-4 Line Decoder

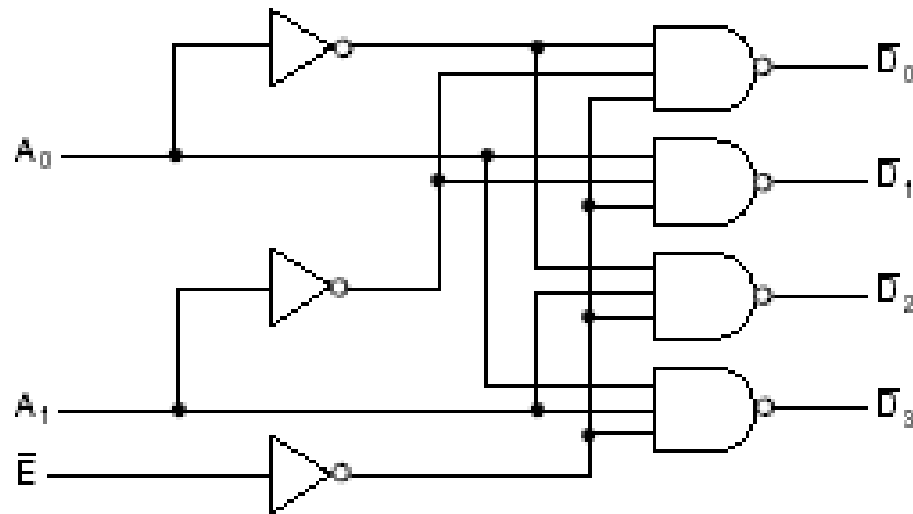

(a) Logic diagram

E	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$D_0 = \overline{E} \cdot \overline{A_1} \cdot \overline{A_0}$$

$$D_1 = \overline{E} \cdot \overline{A_1} \cdot A_0$$

$$D_2 = \overline{E} \cdot A_1 \cdot \overline{A_0}$$

$$D_3 = \overline{E} \cdot A_1 \cdot A_0$$

(c) Logic Equations

Dataflow Modeling

//Dataflow description of a 2-to-4-line decoder

```
module decoder_df (A,B,E,D);
```

```
    input A,B,E;
```

```
    output [0:3] D;
```


```
    assign D[0] = ~(~A & ~B & ~E),
```

```
           D[1] = ~(~A & B & ~E),
```

```
           D[2] = ~(A & ~B & ~E),
```

```
           D[3] = ~(A & B & ~E);
```

```
endmodule
```

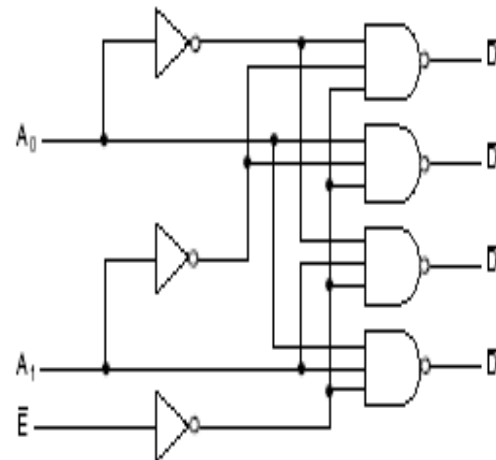

(a) Logic diagram

E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\overline{D_0} = \overline{E} \overline{A_1} \overline{A_0}$$

$$\overline{D_1} = \overline{E} \overline{A_1} A_0$$

$$\overline{D_2} = \overline{E} A_1 \overline{A_0}$$

$$\overline{D_3} = \overline{E} A_1 A_0$$

(c) Logic Equations

Fig.3-14 A 2-to-4-Line Decoder

4 bit Full Adder

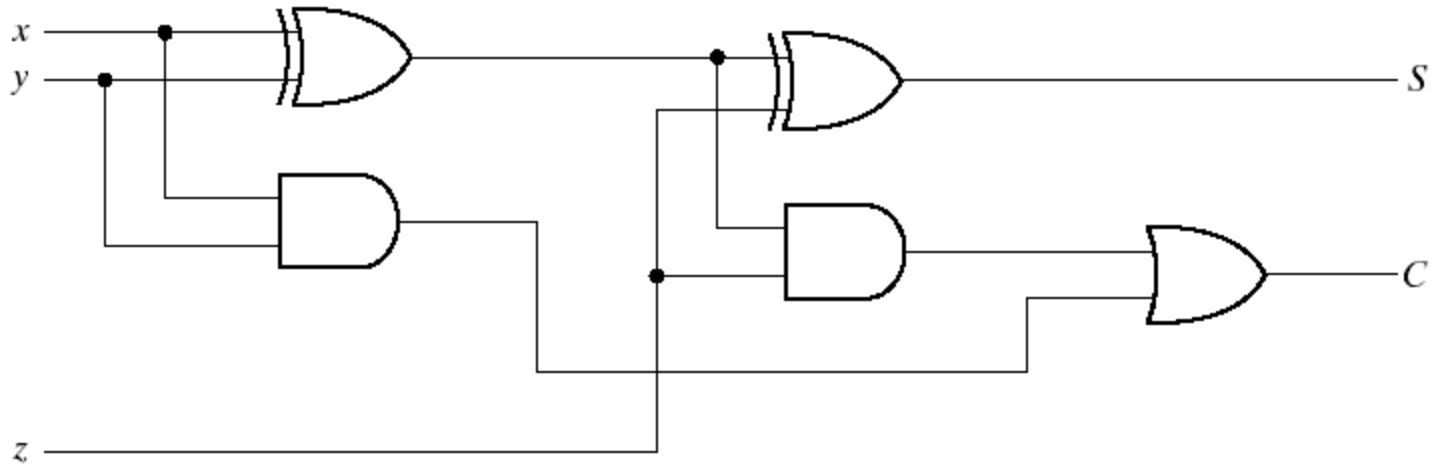


FIG. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

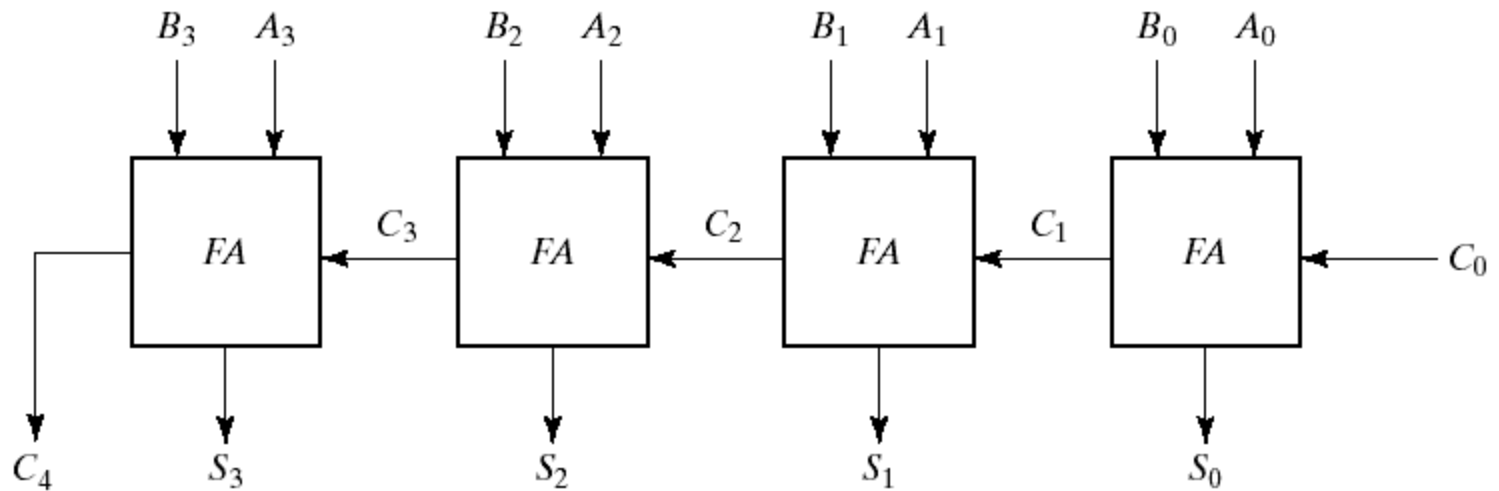


Fig. 4-9 4-Bit Adder

Dataflow Modeling

```
//Dataflow description of 4-bit adder  
module binary_adder (A,B,Cin,SUM,Cout);  
    input [3:0] A,B;  
    input Cin;  
    output [3:0] SUM;  
    output Cout;  
    assign {Cout,SUM} = A + B + Cin;  
endmodule
```

Dataflow Modeling

- The addition logic of 4 bit adder is described by a single statement using the operators of **addition** and **concatenation**.
- The plus symbol (+) specifies the binary addition of the 4 bits of A with the 4 bits of B and the one bit of Cin .
- The target output is the concatenation of the output carry $Cout$ and the four bits of SUM .
- Concatenation of operands is expressed within braces and a comma separating the operands. Thus, $\{Cout, SUM\}$ represents the 5-bit result of the addition operation.


- Dataflow modelling provides means of describing combinational circuit by function rather than gate structure.
- A verilog HDL Synthesis tool can accept this module as input and can provide a netlist of a circuit equivalent.

Dataflow Modeling

```
//Dataflow description of a 4-bit comparator.  
module magcomp (A,B,ALTB,AGTB,AEQB);  
    input [3:0] A,B;  
    output ALTB,AGTB,AEQB;  
    assign ALTB = (A < B),  
           AGTB = (A > B),  
           AEQB = (A == B);  
endmodule
```


Multiplexer

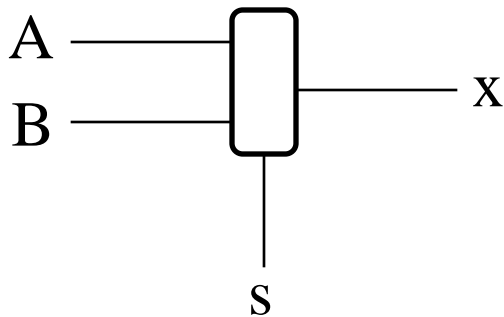- Multiplexer is a combinational circuit where an input is chosen by a select signal.
 - Two input mux
 - output = A if select = 1
 - output = B if select = 0



Two Input Multiplexor

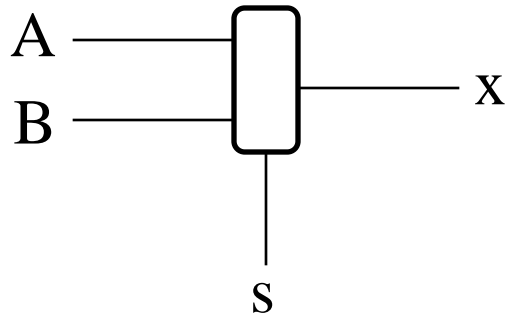- A two-input mux is actually a three input device.



$$X = A.s + B.\bar{s}$$

s	A	B	x
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Dataflow description of 2-input Mux

- Conditional operator `?`: takes three operands:
`condition? true_expression : false_expression`

```
module mux2x1_df (A,B,select,x);  
    input A,B,select;  
    output x;  
    assign x = select ? A : B;  
endmodule
```